

Embedded Hardware Design and Development

Unit 2-3

Dr. Dhanashri H. Gawali

Analog Circuit Design:

Transistors




Transistor --
Transfer Varistor


Two types –
NPN and PNP

Three terminals --
Emitter (E),
Base (B),
Collector (C)

It is current-
controlled device

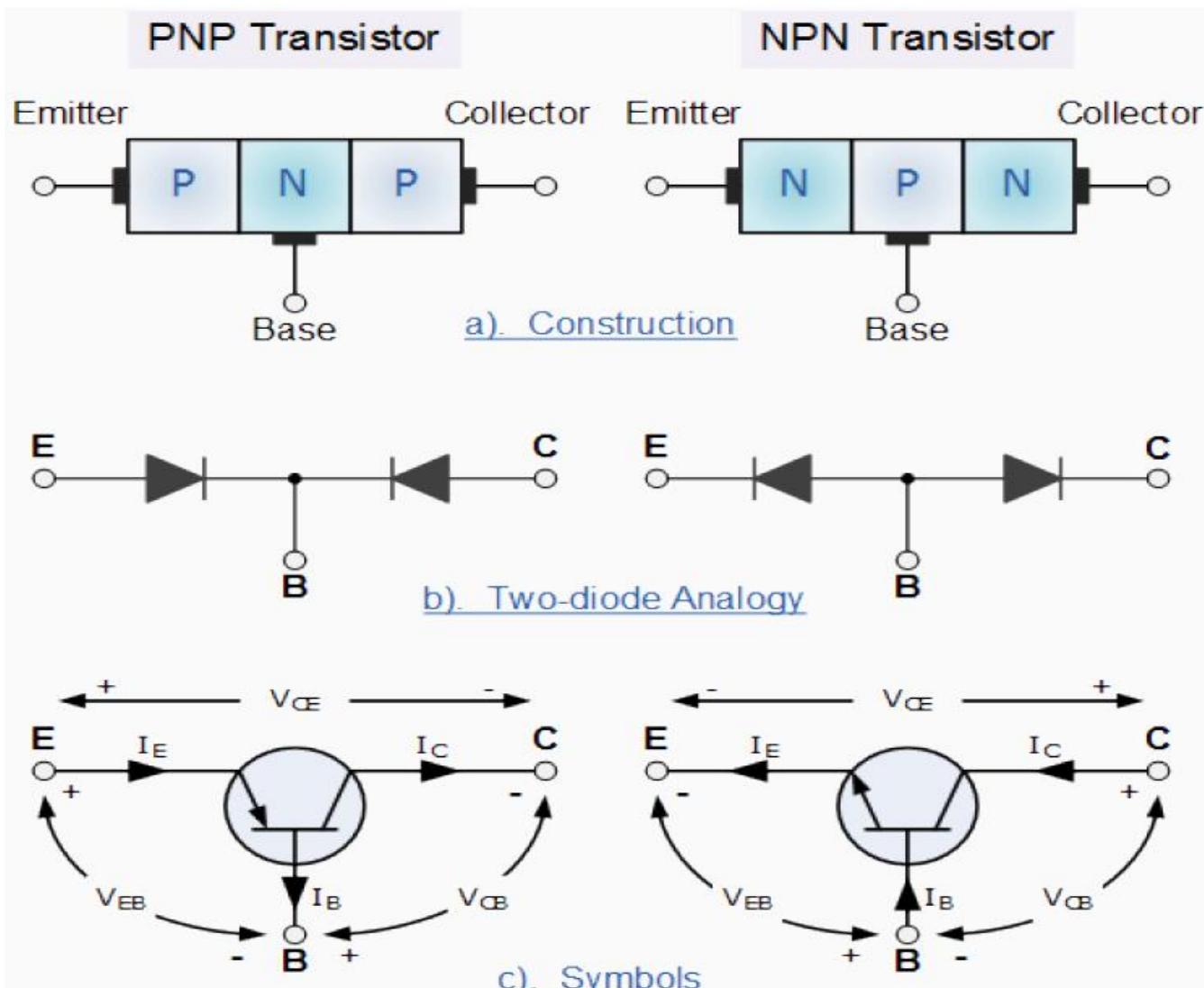


Transistors : BJT

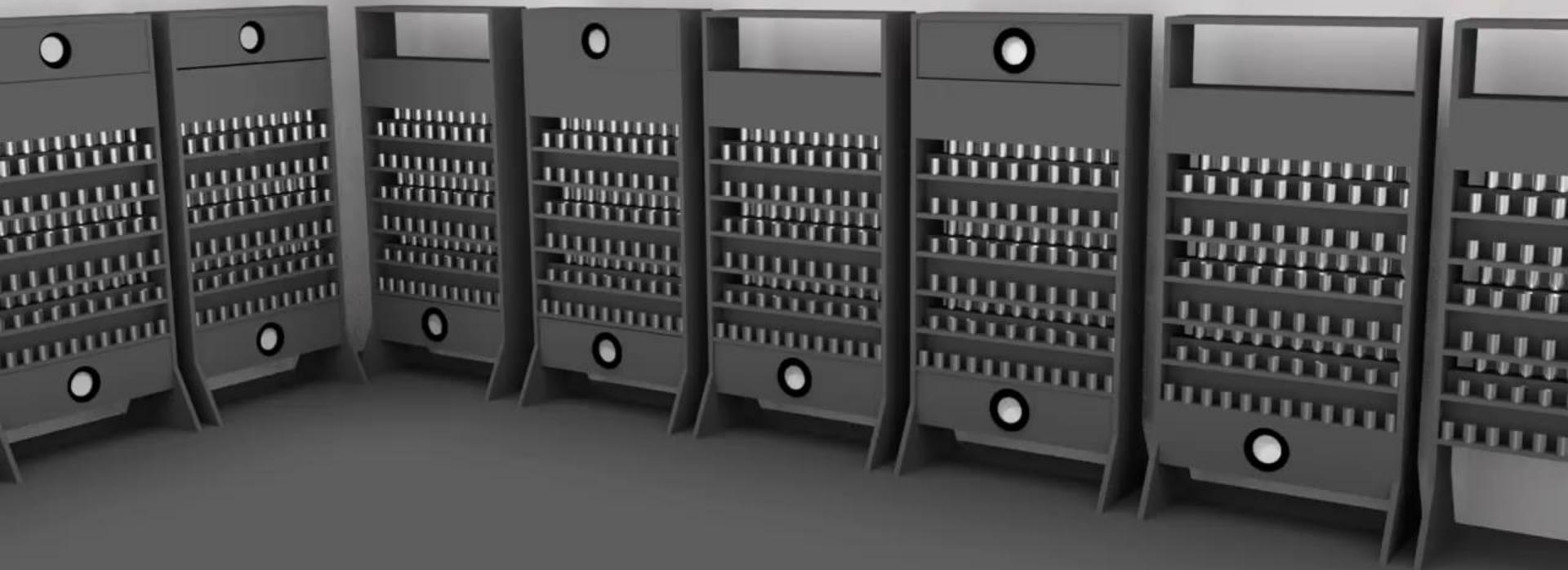

SPECIAL THANKS
JOSE JOJI
WESTGHATS TECHNOLOGIES PVT LTD

Transistor biasing

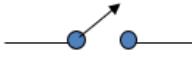Sr. No.	Region of operation	Base emitter junction	Collector base junction	application
1	Cutoff region	Reverse biased	Reverse biased	
2	Saturation region	Forward biased	Forward biased	
3	Active region	Forward biased	Reverse biased	Amplifier

Bipolar Transistor Configurations

- 1. Common Base Configuration - has Voltage Gain but no Current Gain.
-
- 2. Common Emitter Configuration - has both Current and Voltage Gain.
-
- 3. Common Collector Configuration - has Current Gain but no Voltage Gain.

Characteristics of a transistor in CB configuration

- **The characteristics of a transistor help us to understand its behavior.**
- **The transistor characteristics are of three types :**

Characteristics of a transistor in CB configuration

- **The characteristics of a transistor help us to understand its behavior.**
- **The transistor characteristics are of three types :**
- **Input characteristics**

Characteristics of a transistor in CB configuration



- The characteristics of a transistor help us to understand its behavior.
- The transistor characteristics are of three types :
- **Input characteristics**
- **Output characteristics**

Characteristics of a transistor in CB configuration

- **The characteristics of a transistor help us to understand its behavior.**
- **The transistor characteristics are of three types :**
- **Input characteristics**
- **Output characteristics**
- **Transfer characteristics**


Characteristics of a transistor in CB configuration

Input characteristics

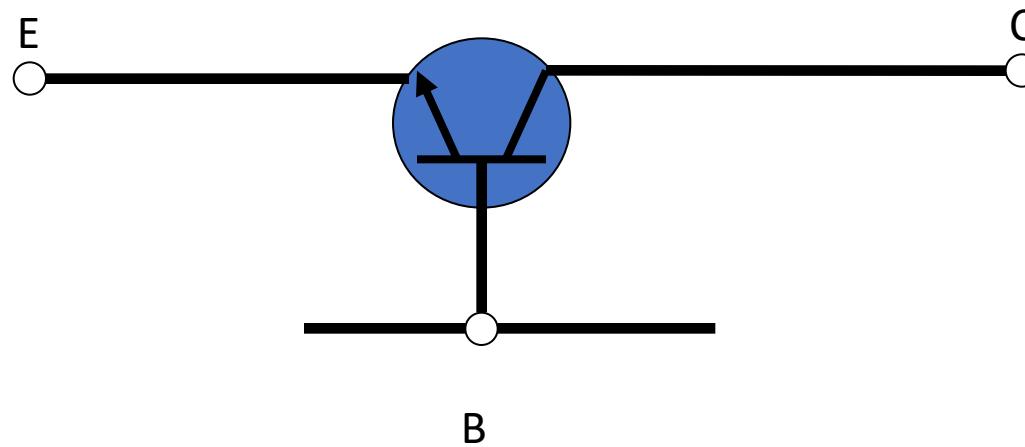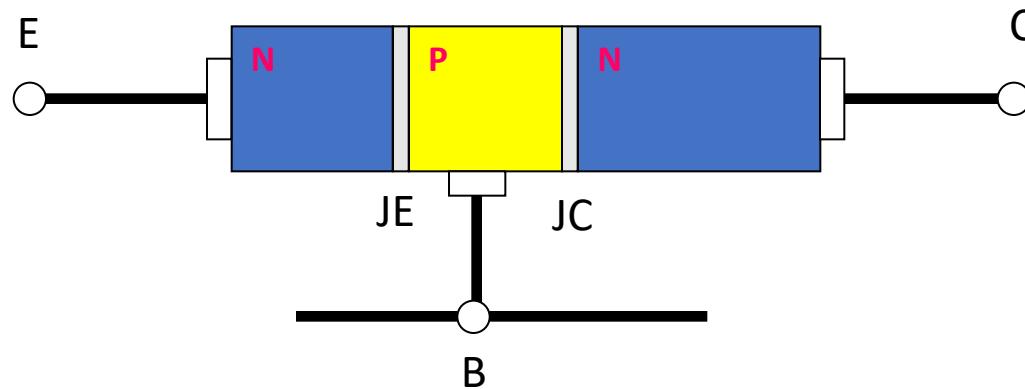


Characteristics of a transistor in CB configuration

Input characteristics



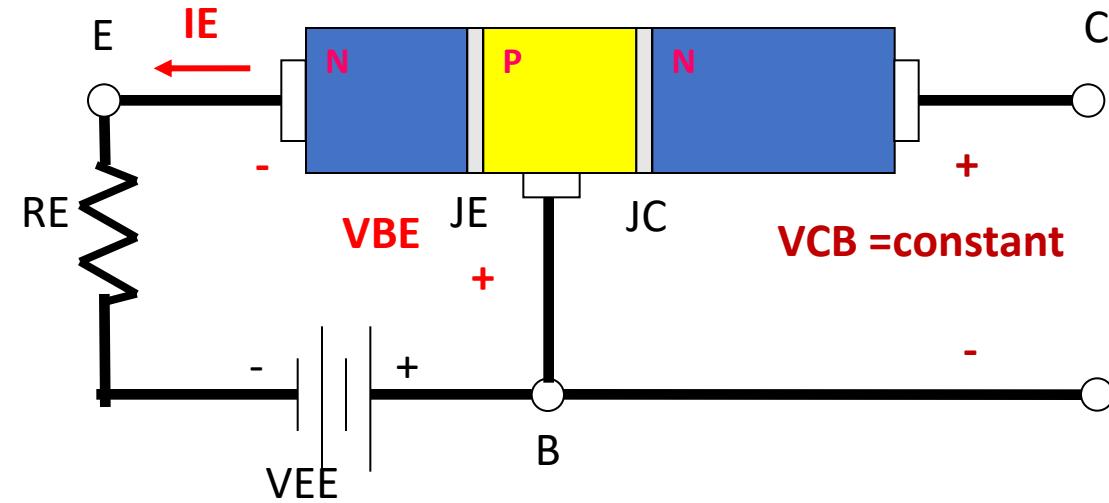


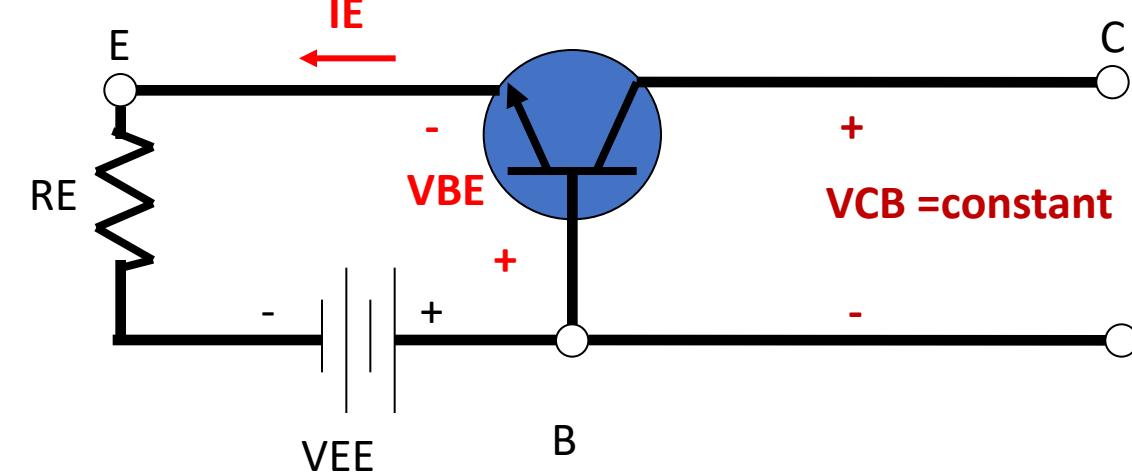- Input characteristics is always A graph of input current versus Input voltage.
- For the CB configuration, input Current is I_E and input voltage Is the emitter to base voltage V_{BE}
- Input characteristics is plotted at a constant output voltage V_{CB}






Characteristics of a transistor in CB configuration

Input characteristics

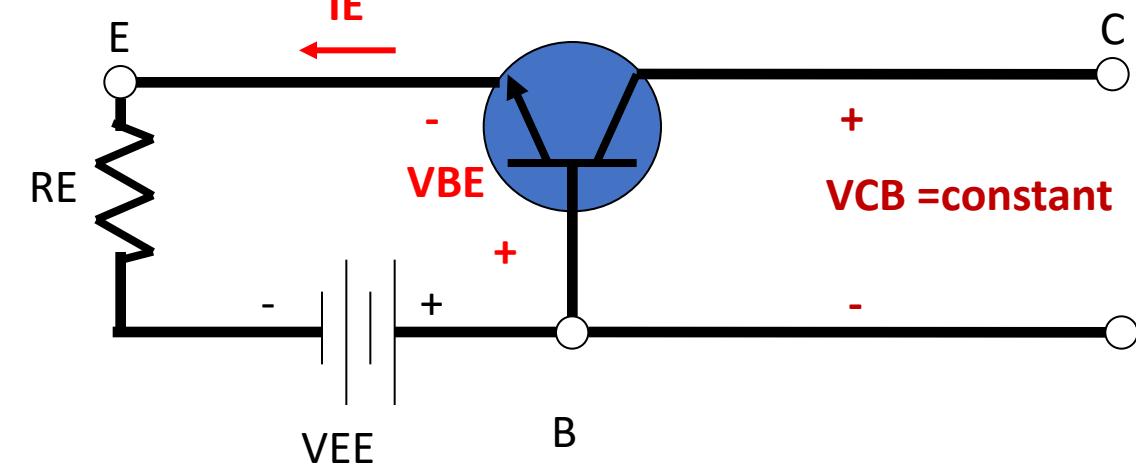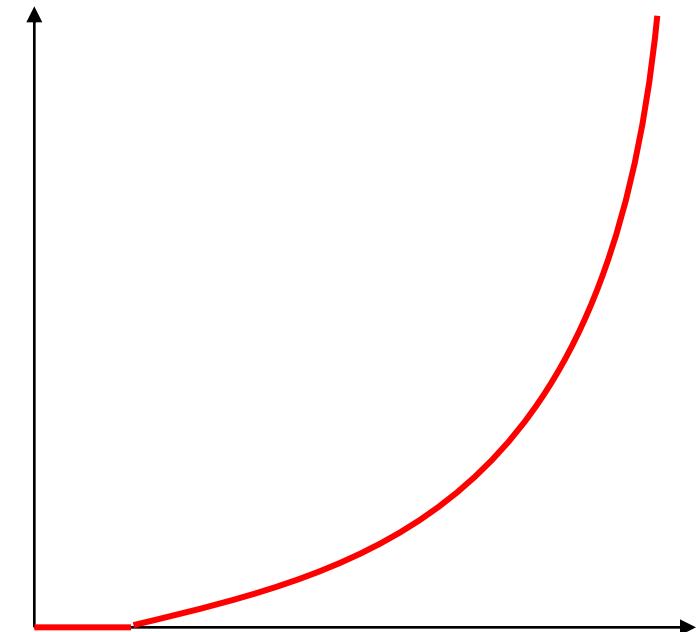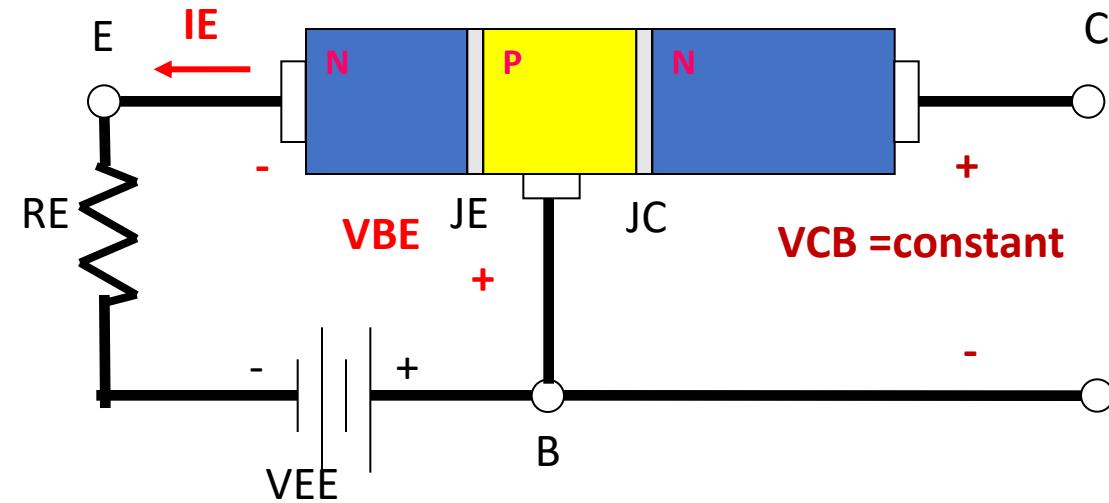

Characteristics of a transistor in CB configuration




Input characteristics

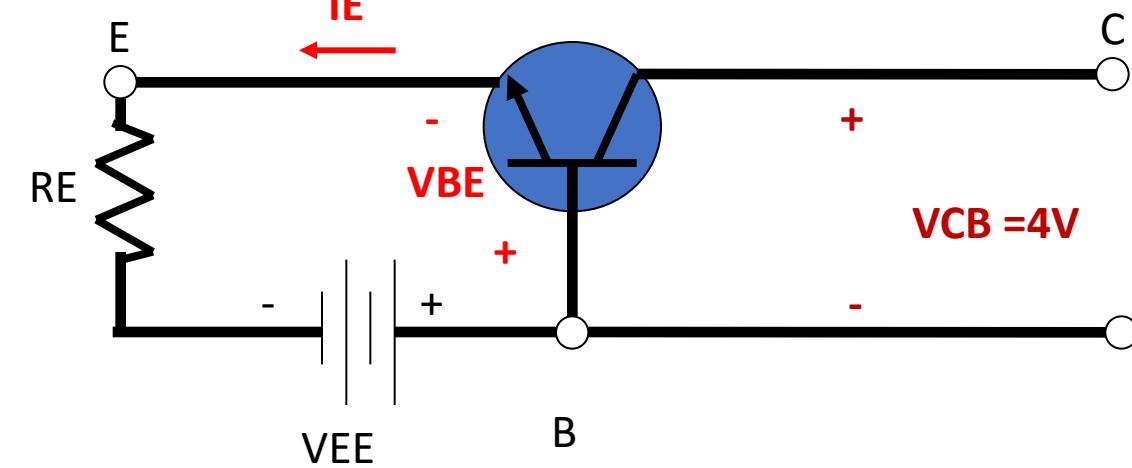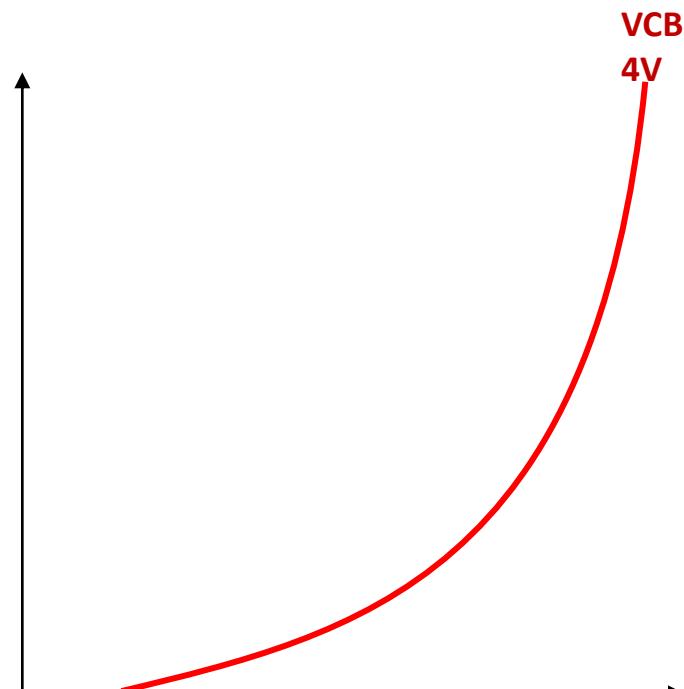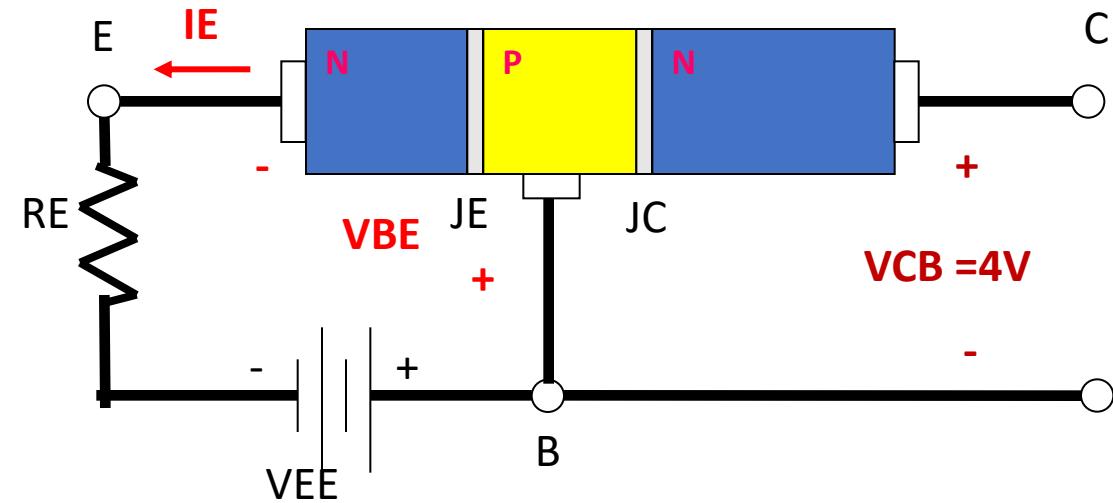

V_{BE}




Characteristics of a transistor in CB configuration

Input characteristics

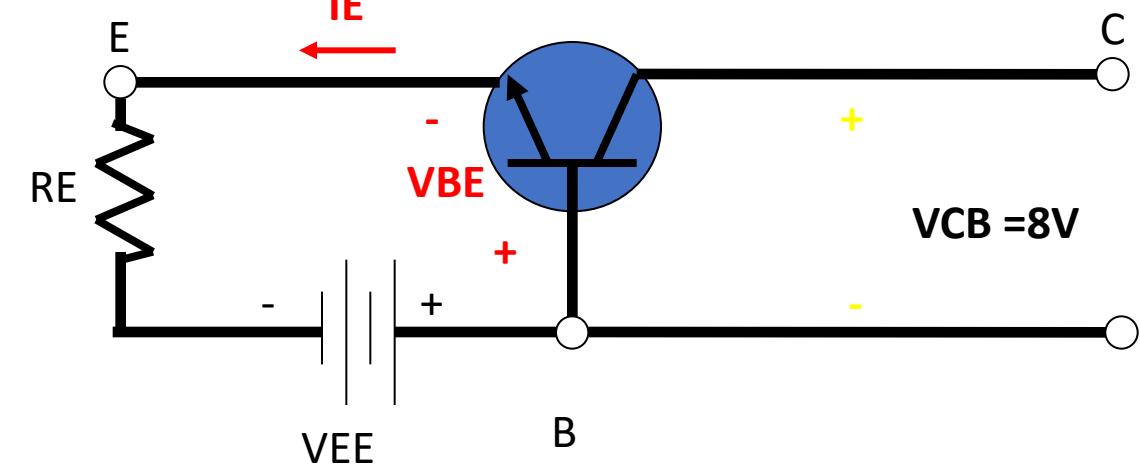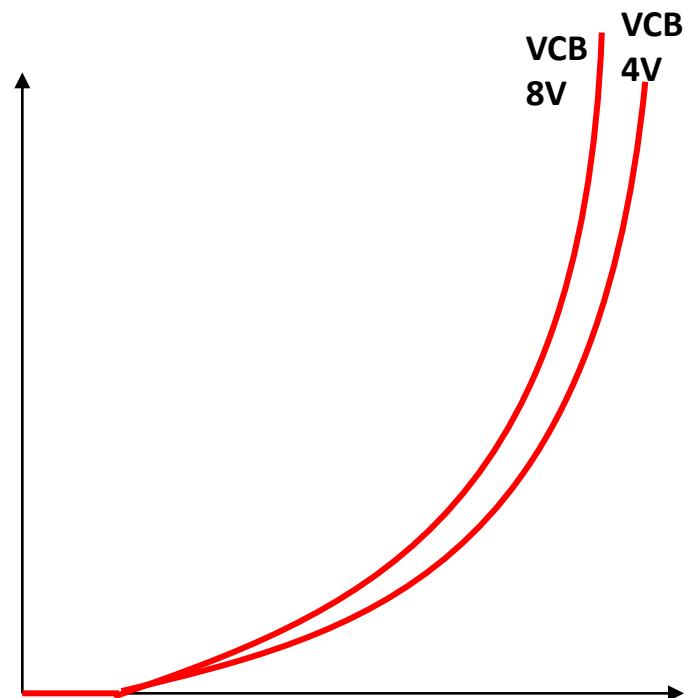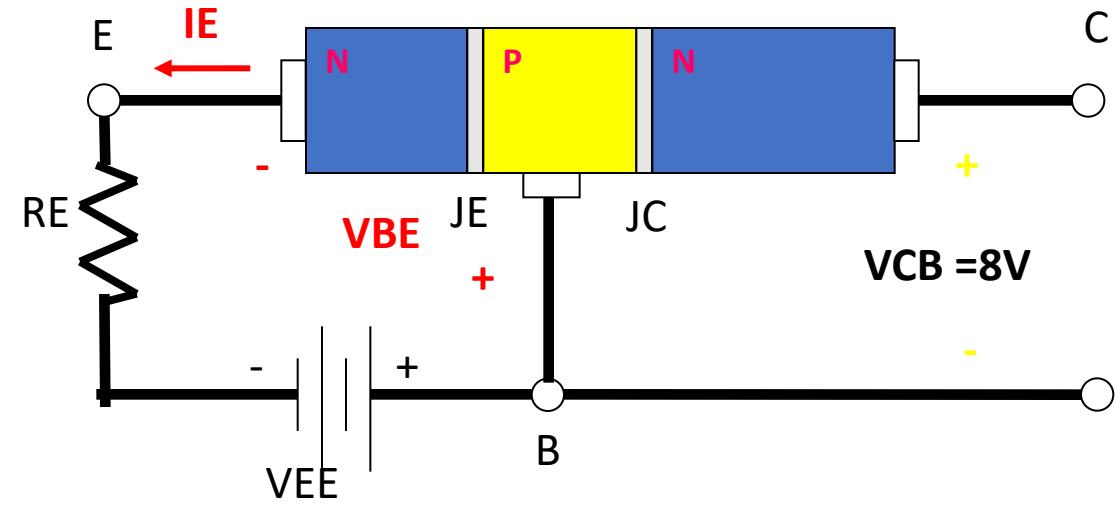




Characteristics of a transistor in CB configuration

Input characteristics

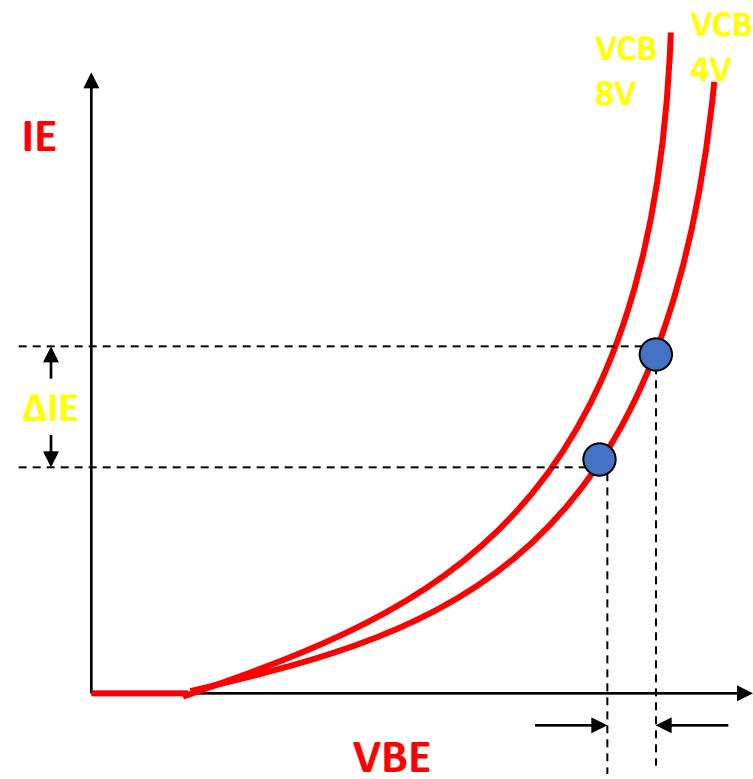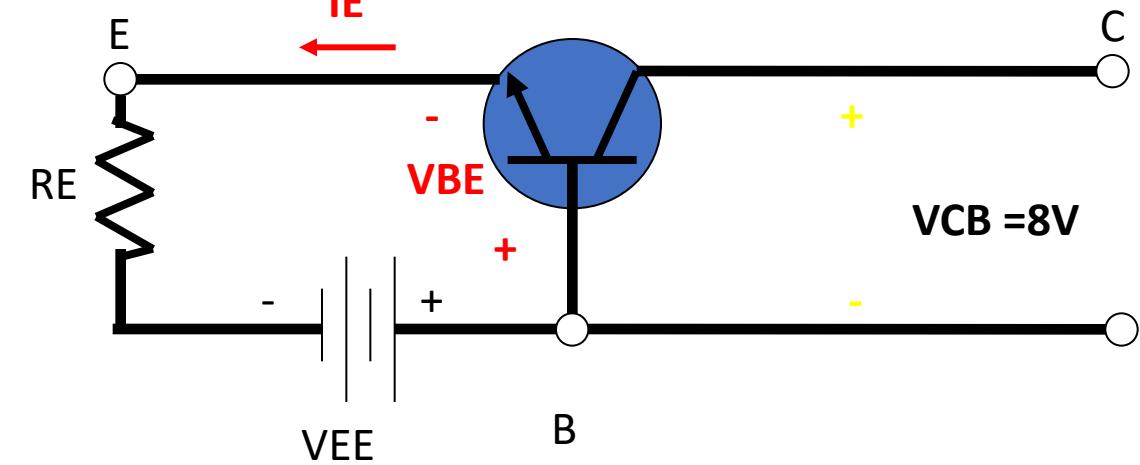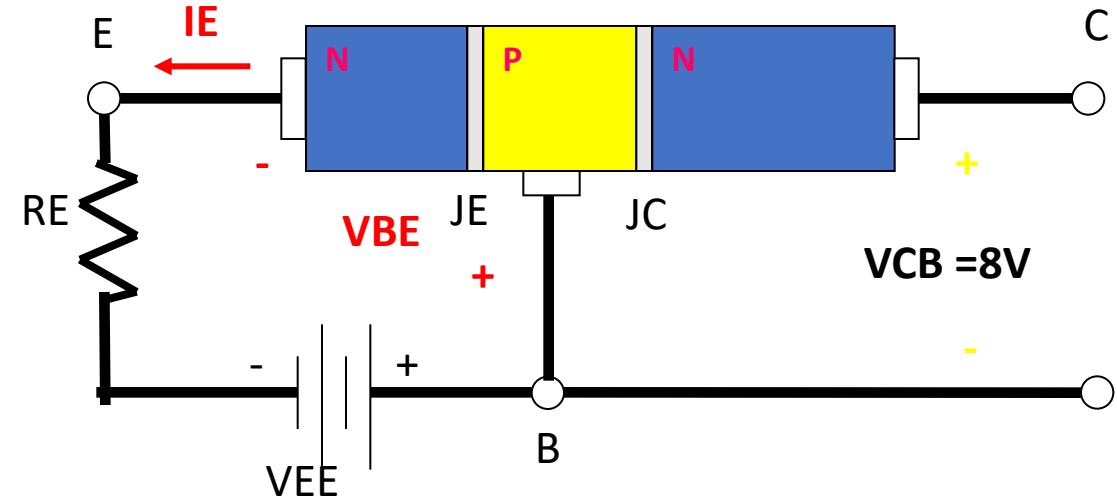

Characteristics of a transistor in CB configuration

Input characteristics

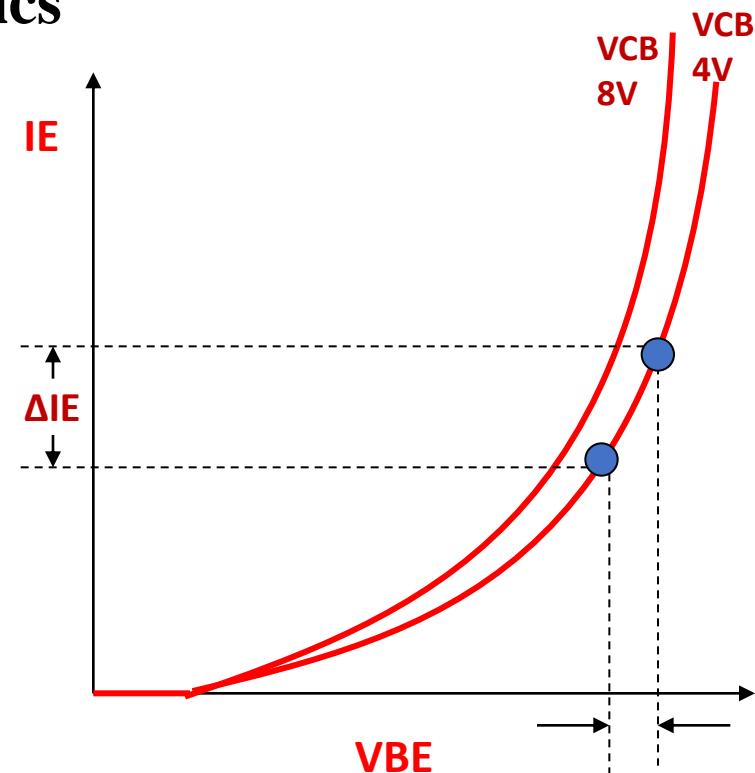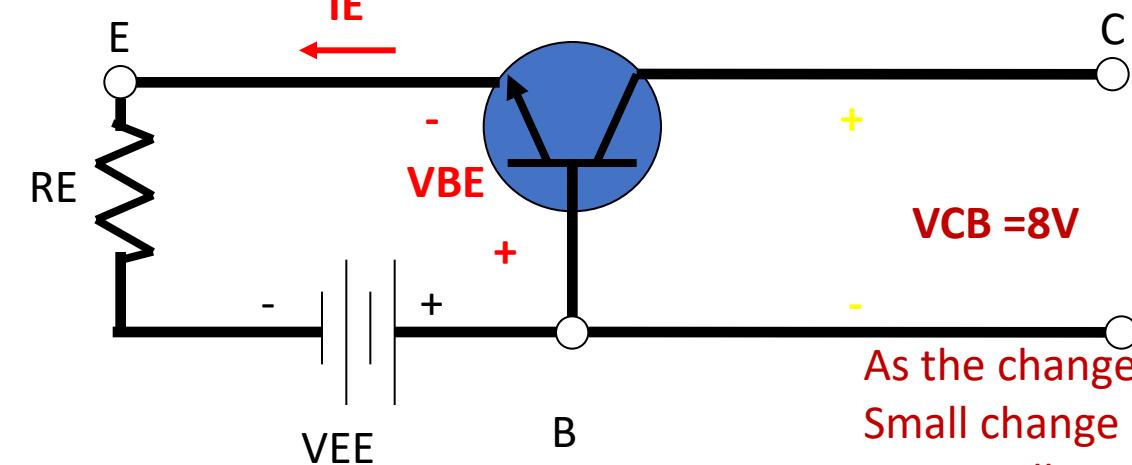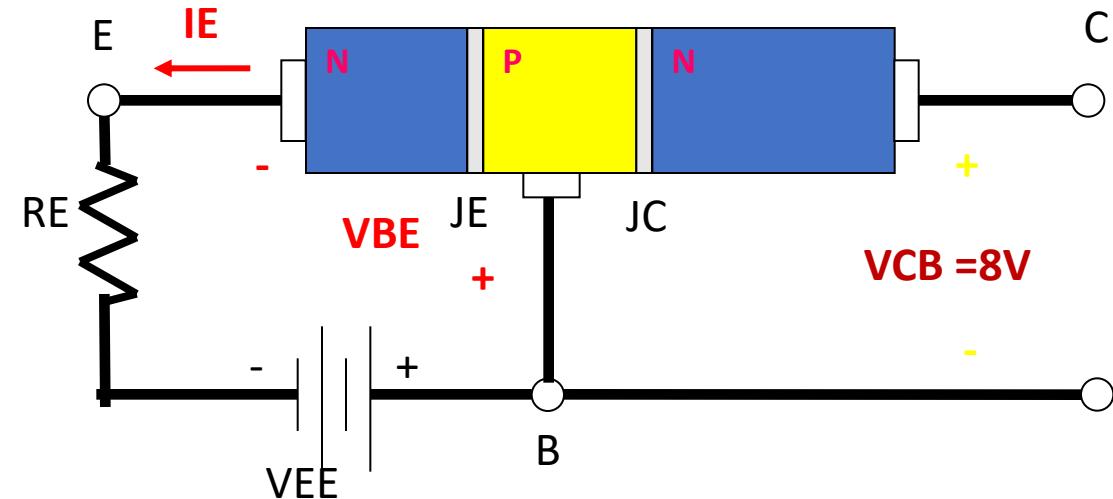

$$\text{Input resistance } R_i = \frac{\Delta V_{BE}}{\Delta I_E}$$


at constant V_{CB}

As the change in emitter current is very large for a small change in input voltage, the input resistance R_i is small

Characteristics of a transistor in CB configuration

Output characteristics

Constant

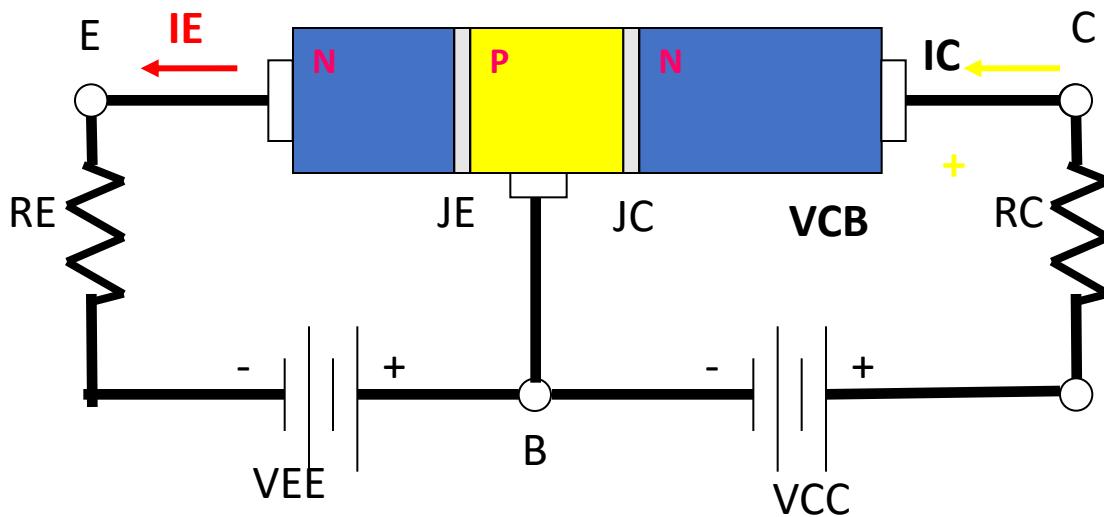


- output characteristics is always
A graph of output current versus
output voltage.

- For the CB configuration, output
Current is I_C and output voltage
Is the collector to base voltage V_{CB}




- Input characteristics is plotted at
a constant input current I_E

Constant I_E

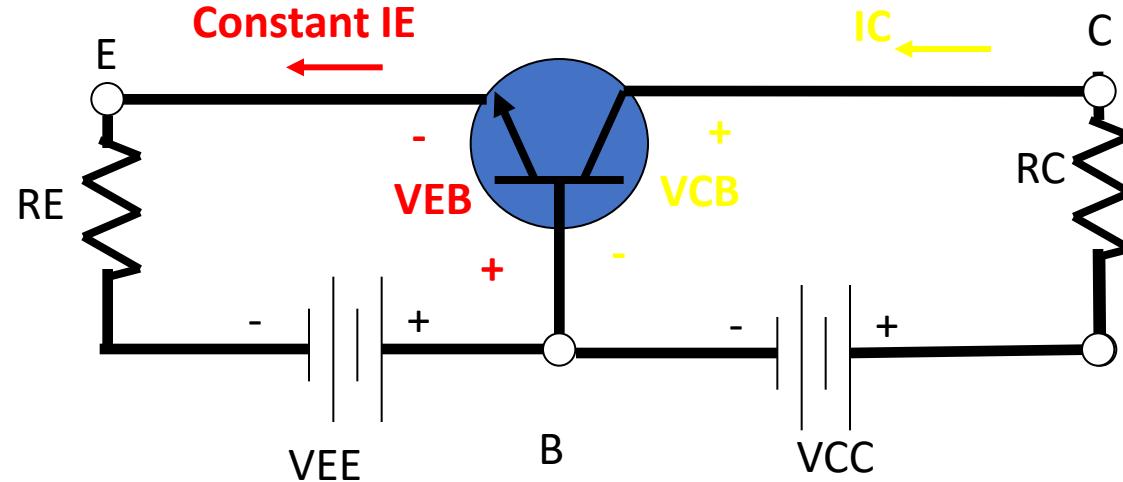




Characteristics of a transistor in CB configuration

Output characteristics

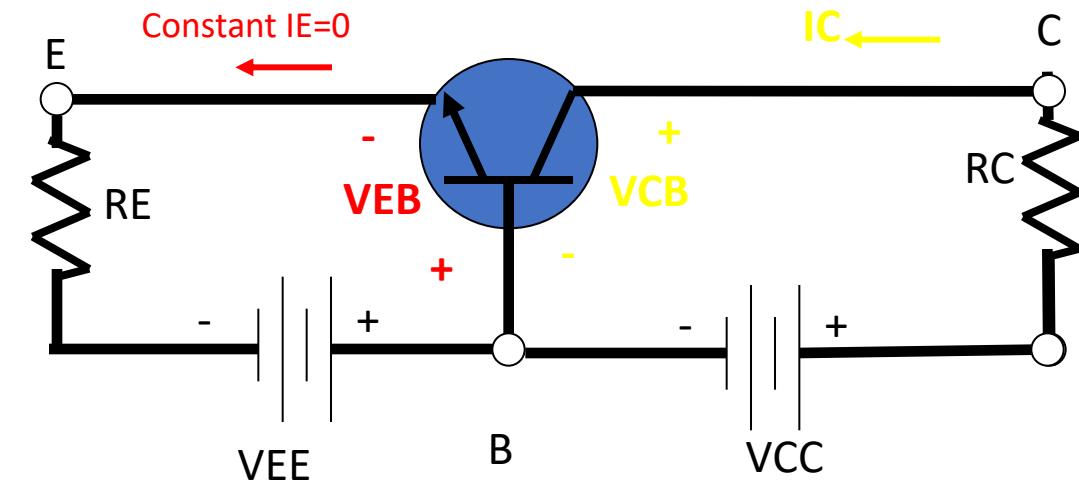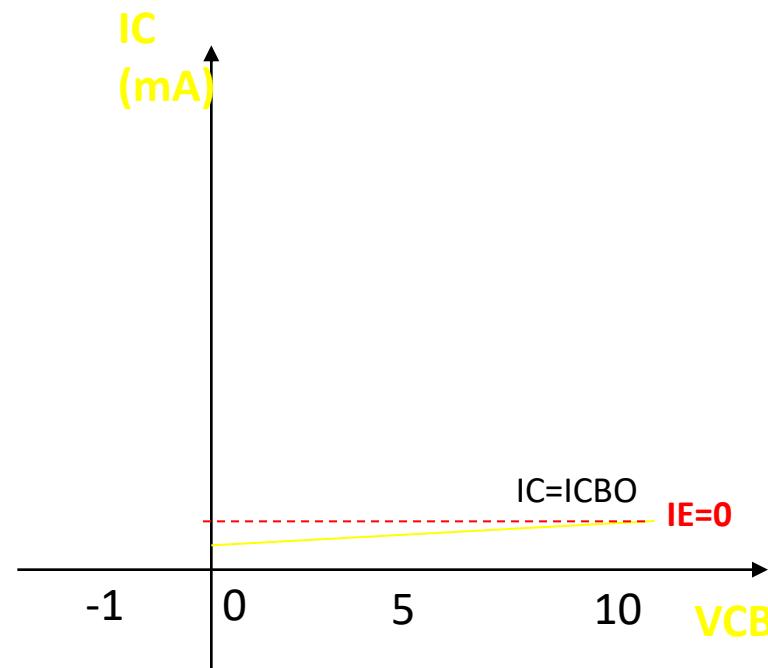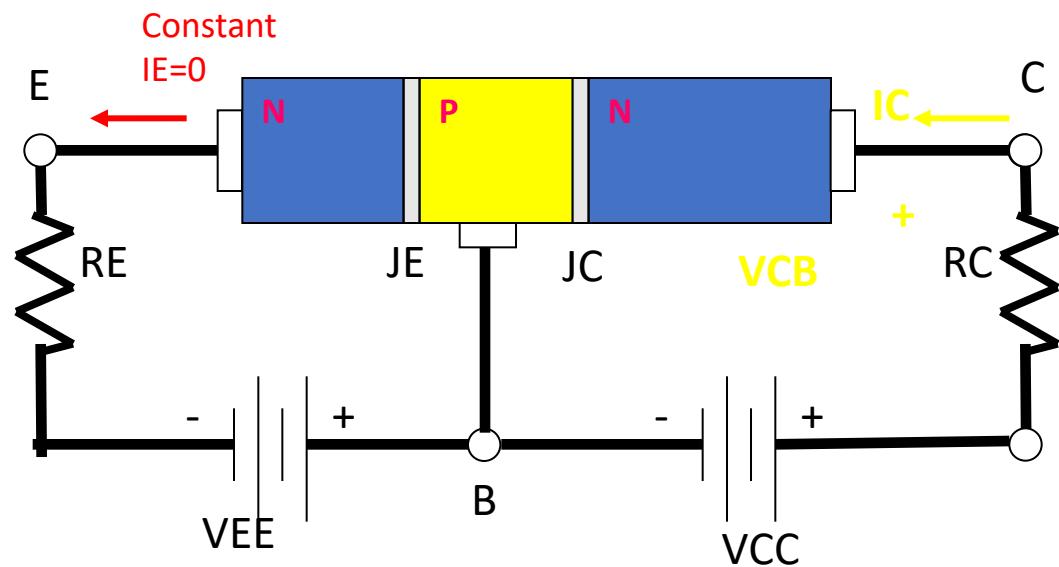

Characteristics of a transistor in CB configuration




Output characteristics

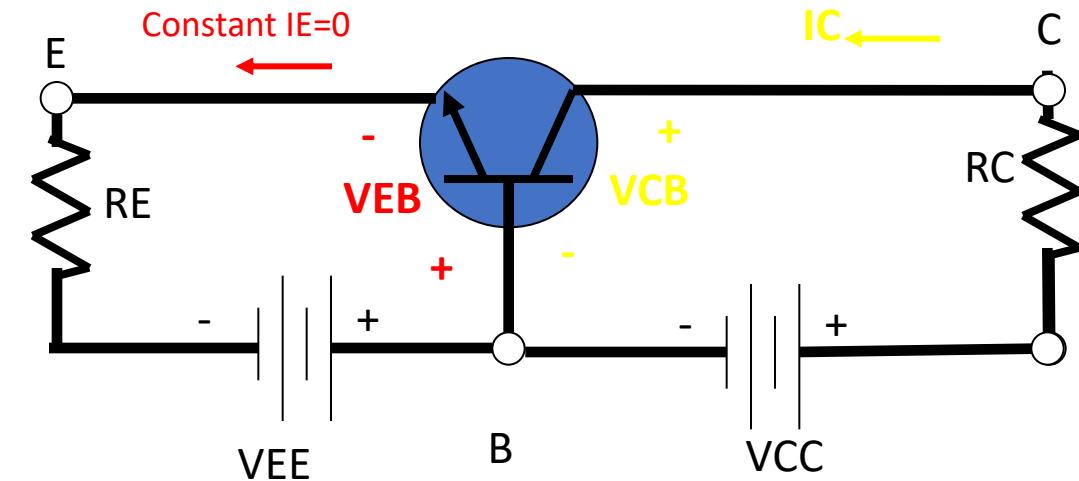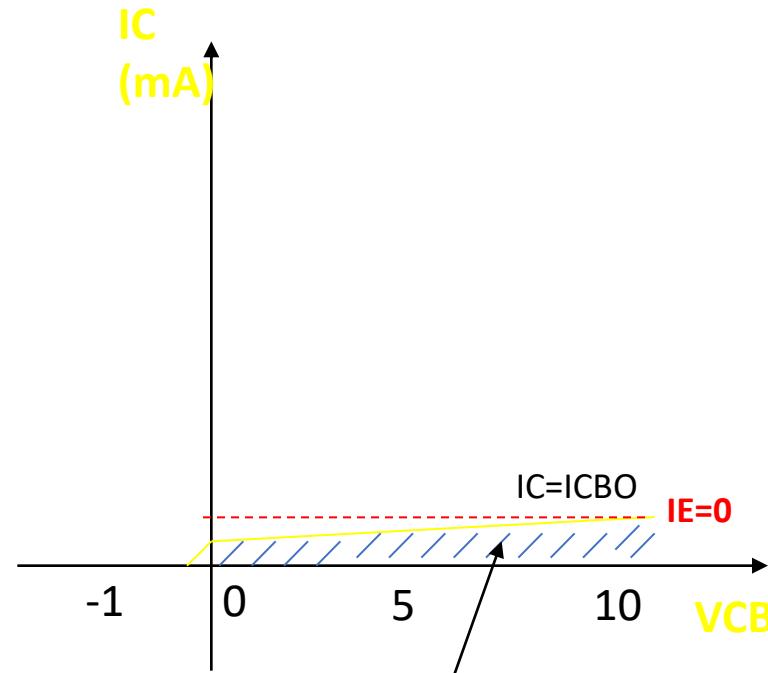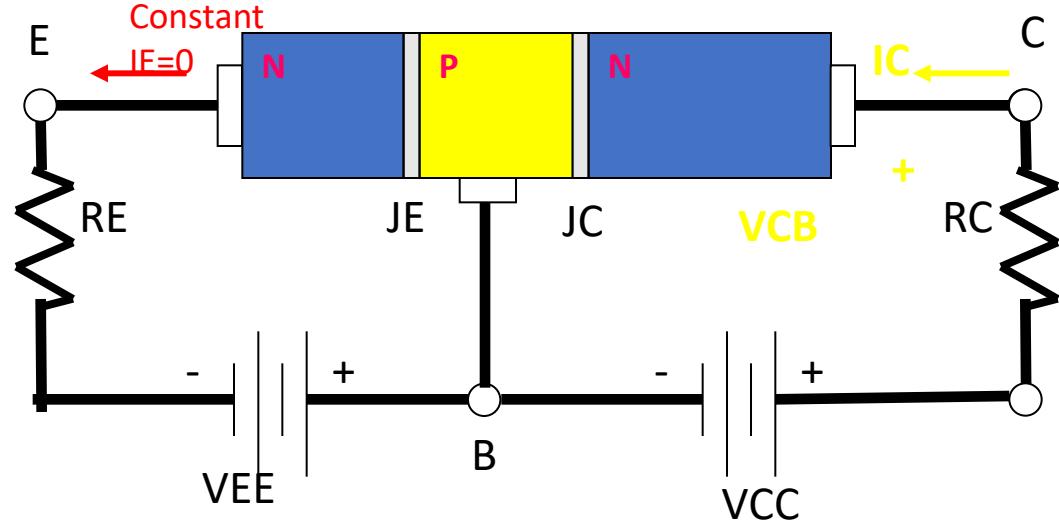

Cutoff region
Both the junction
Becomes reverse bias

Characteristics of a transistor in CB configuration




Output characteristics

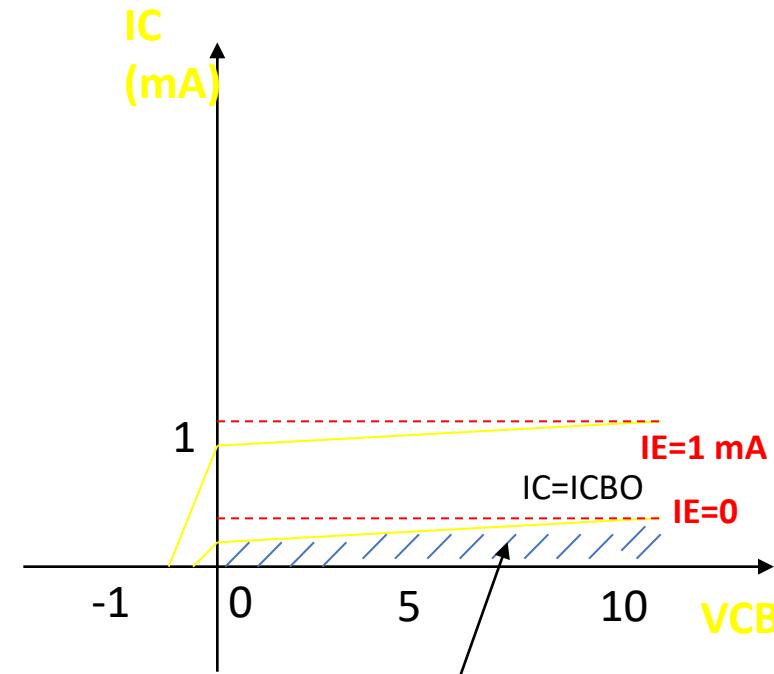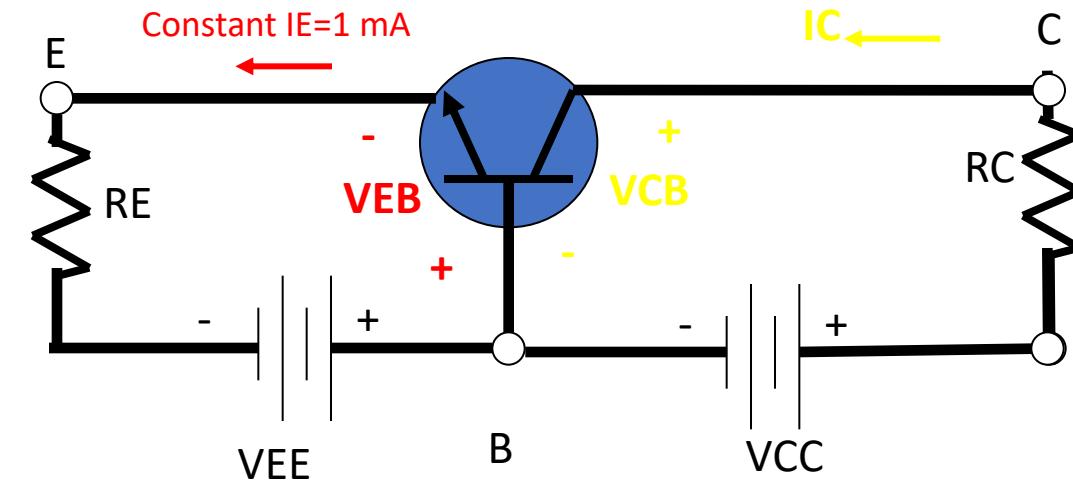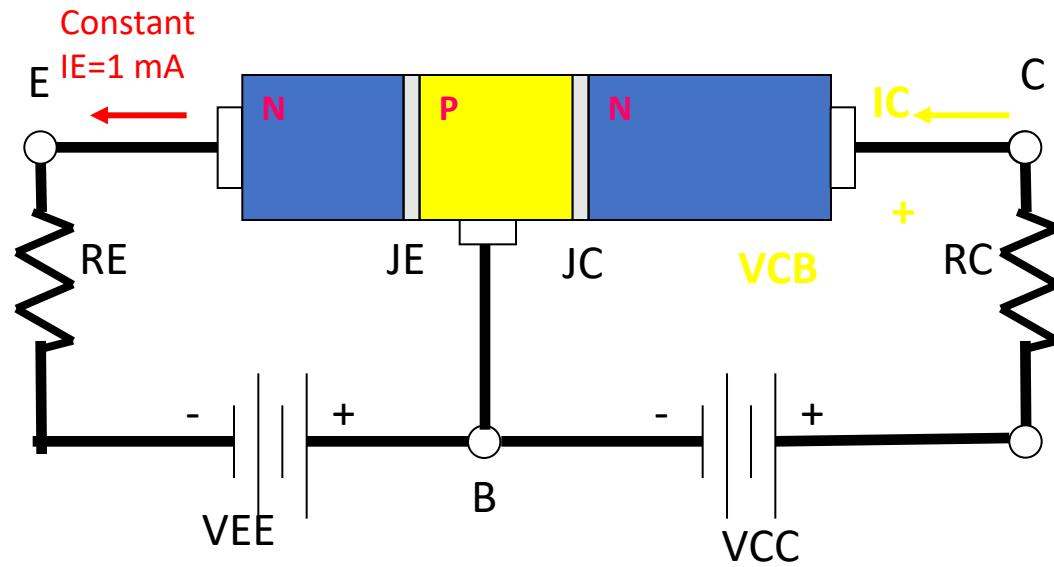

Cutoff region
Both the junction
Becomes reverse bias

Characteristics of a transistor in CB configuration




Output characteristics

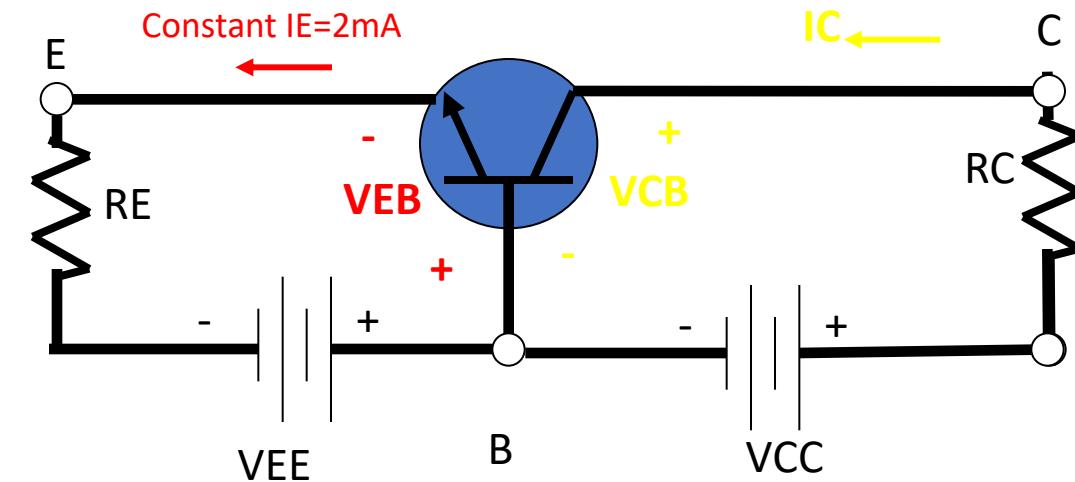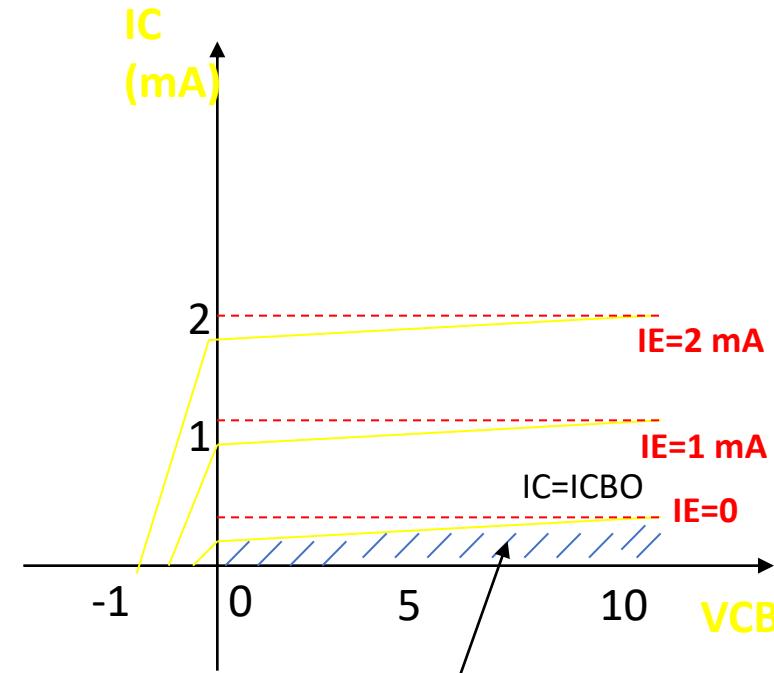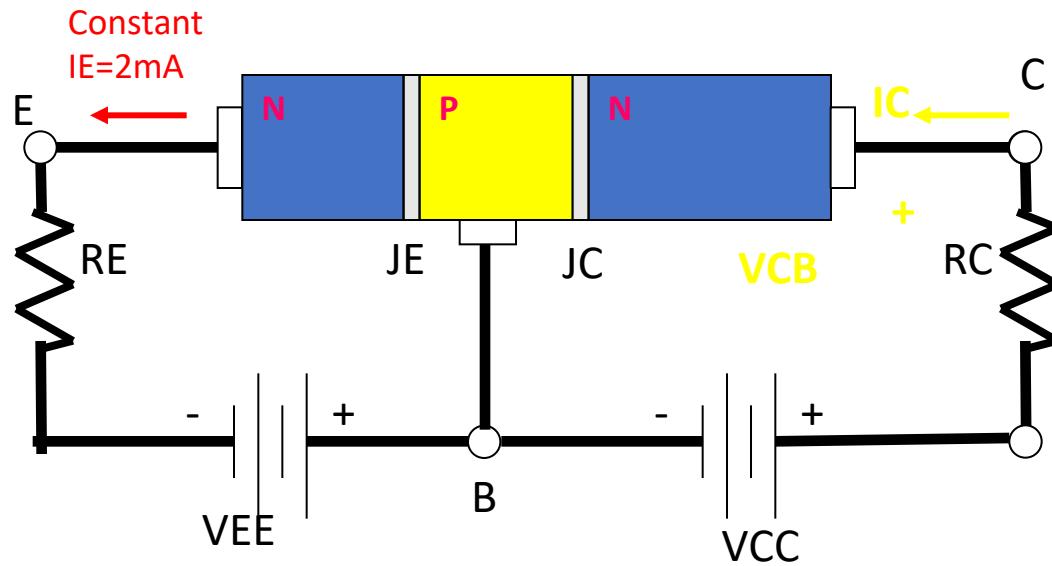

Cutoff region
Both the junction
Becomes reverse bias

Characteristics of a transistor in CB configuration




Output characteristics

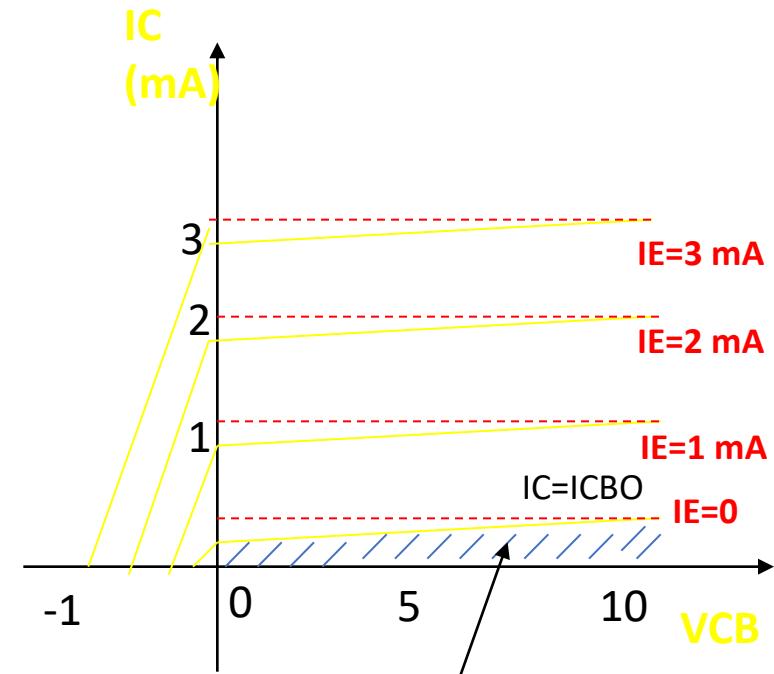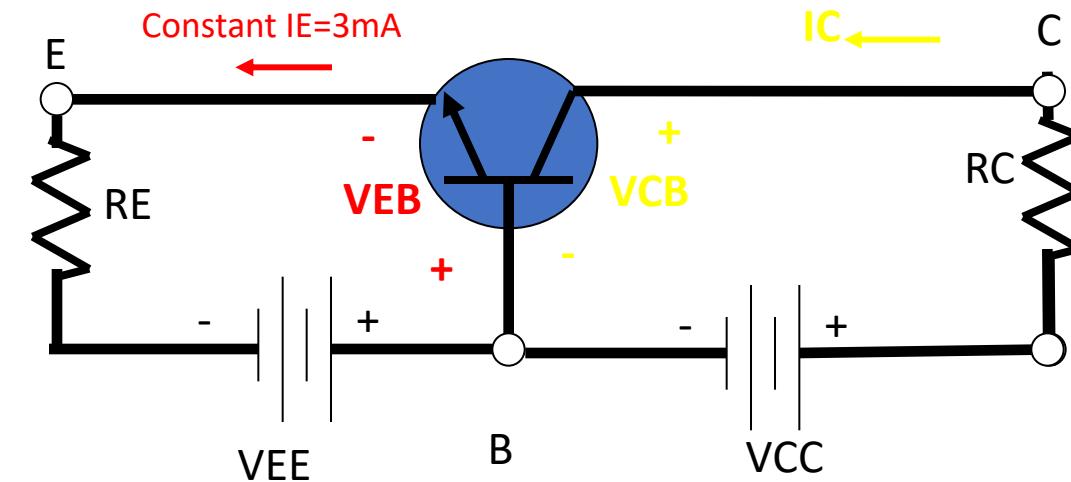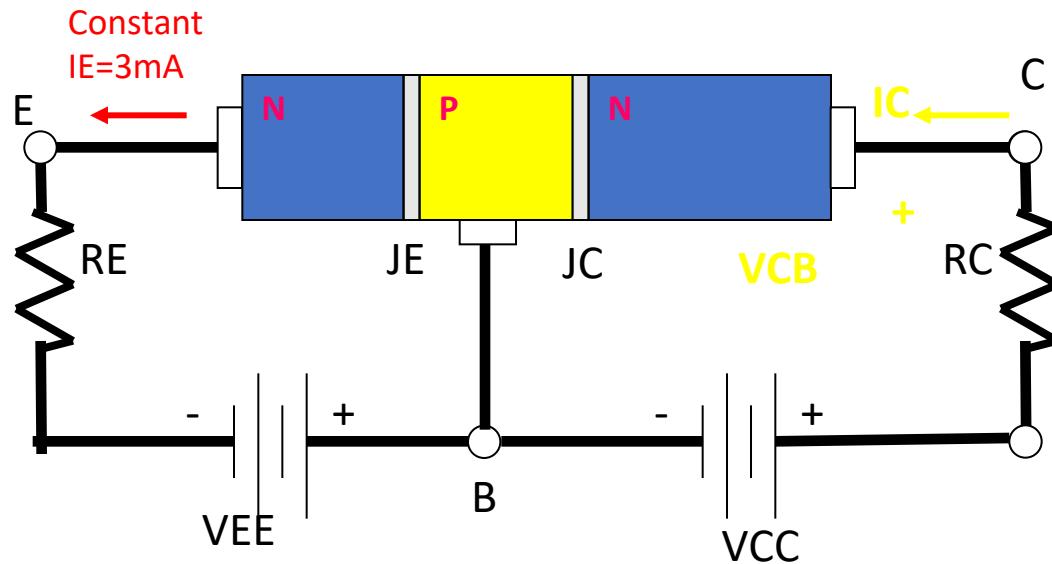

Cutoff region
Both the junction
Becomes reverse bias

Characteristics of a transistor in CB configuration




Output characteristics

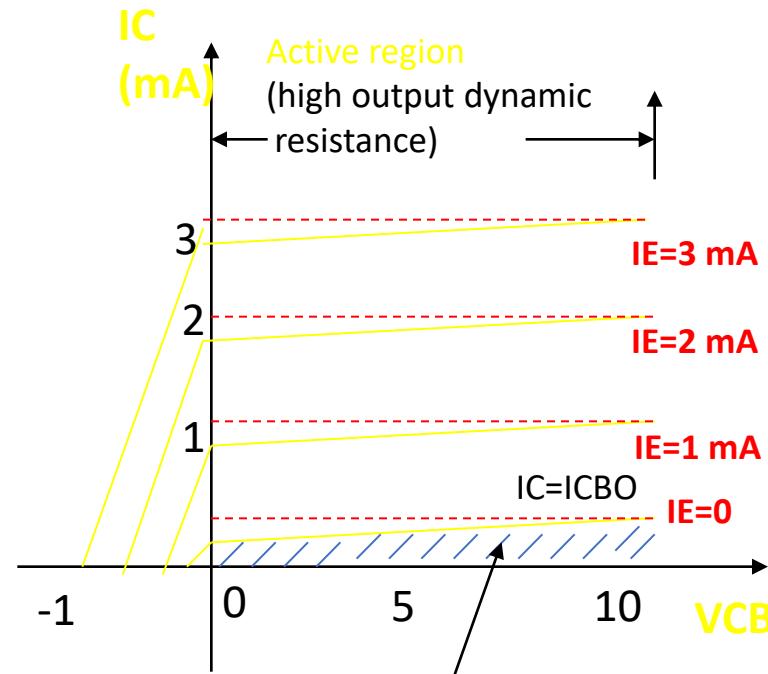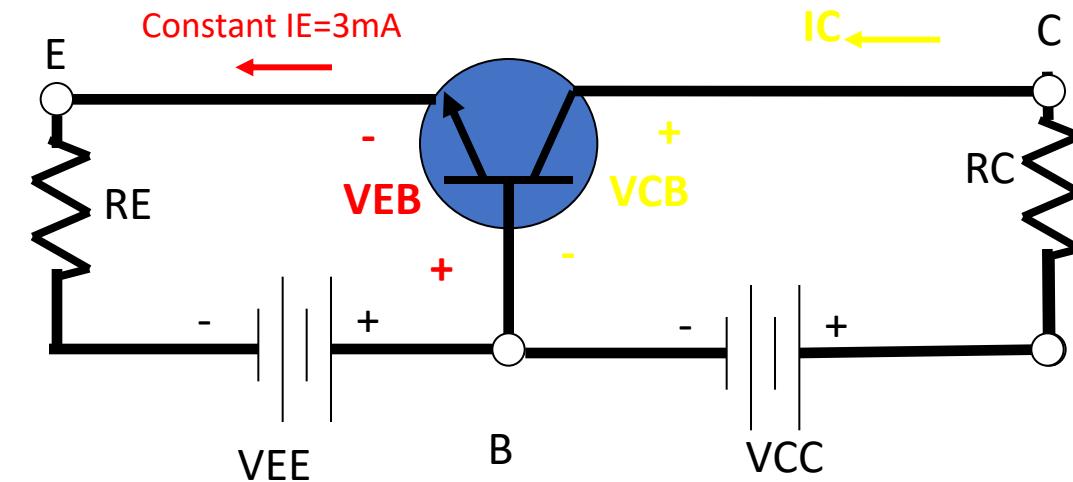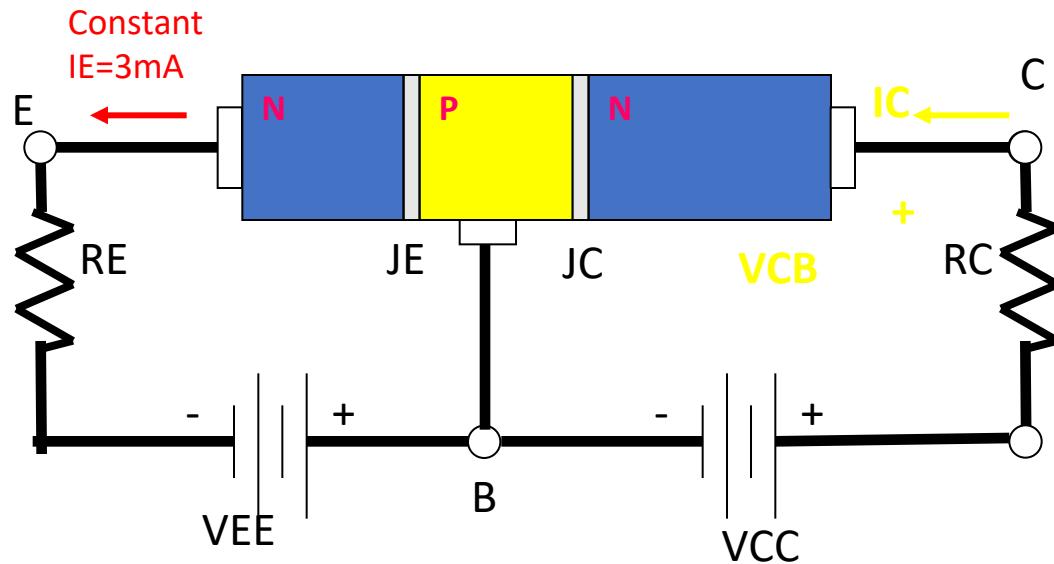

Cutoff region
Both the junction
Becomes reverse bias

Characteristics of a transistor in CB configuration

Output characteristics

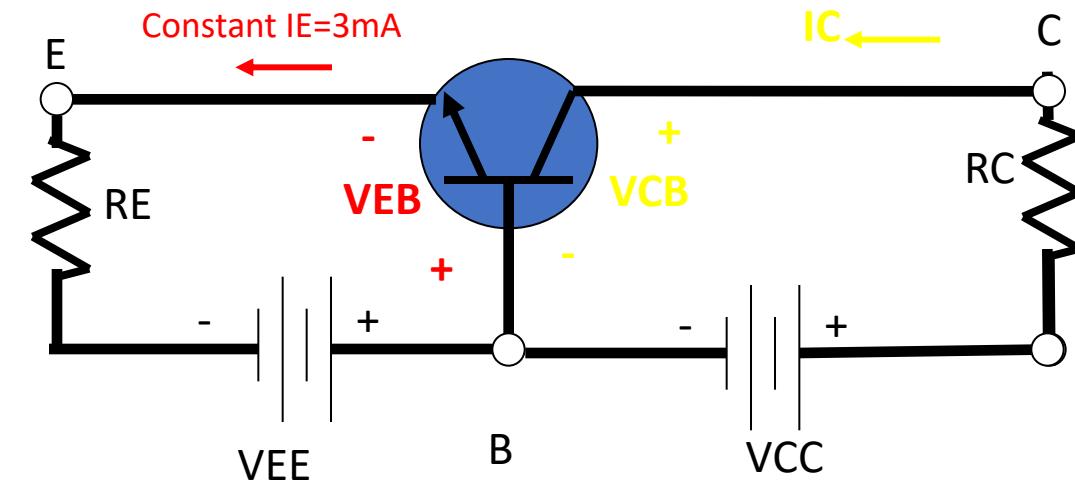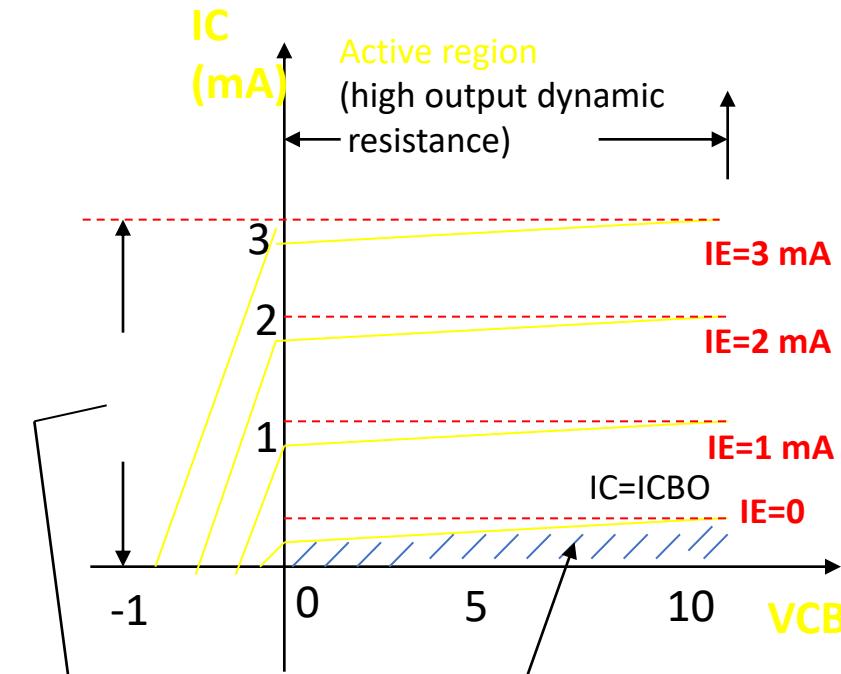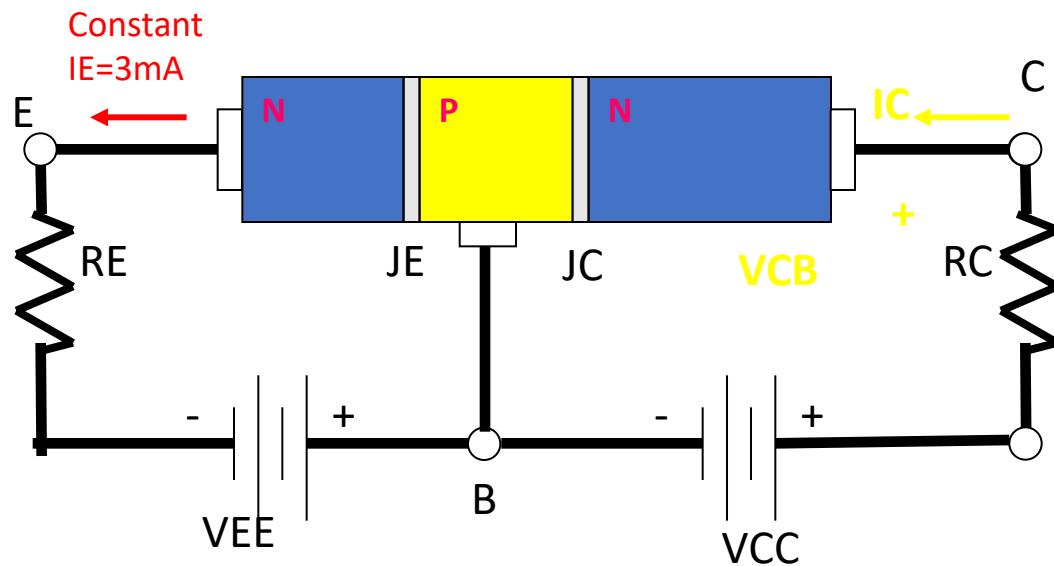

Active region
(high output dynamic resistance)

$IE=3\text{ mA}$

$IE=2\text{ mA}$

$IE=1\text{ mA}$

$IC=IC_{BO}$

$IE=0$

Cutoff region
Both the junction
Becomes reverse bias

saturation region
Both the junction
Becomes forward bias

Characteristics of a transistor in CB configuration

Output characteristics


Dynamic output resistance of the transistor :

$$R_o = \Delta V_{CB} / \Delta I_C \quad \dots \dots \dots \text{for } I_E \text{ constant}$$

- This is nothing but the reciprocal of the output characteristics in the active region.
- Slope of the output characteristics in the active region is very small.
- Therefore the dynamic resistance R_o in the active region is high.
- That's why the voltage drop across the transistor is very large in active region

Characteristics of a transistor in CB configuration


Output characteristics

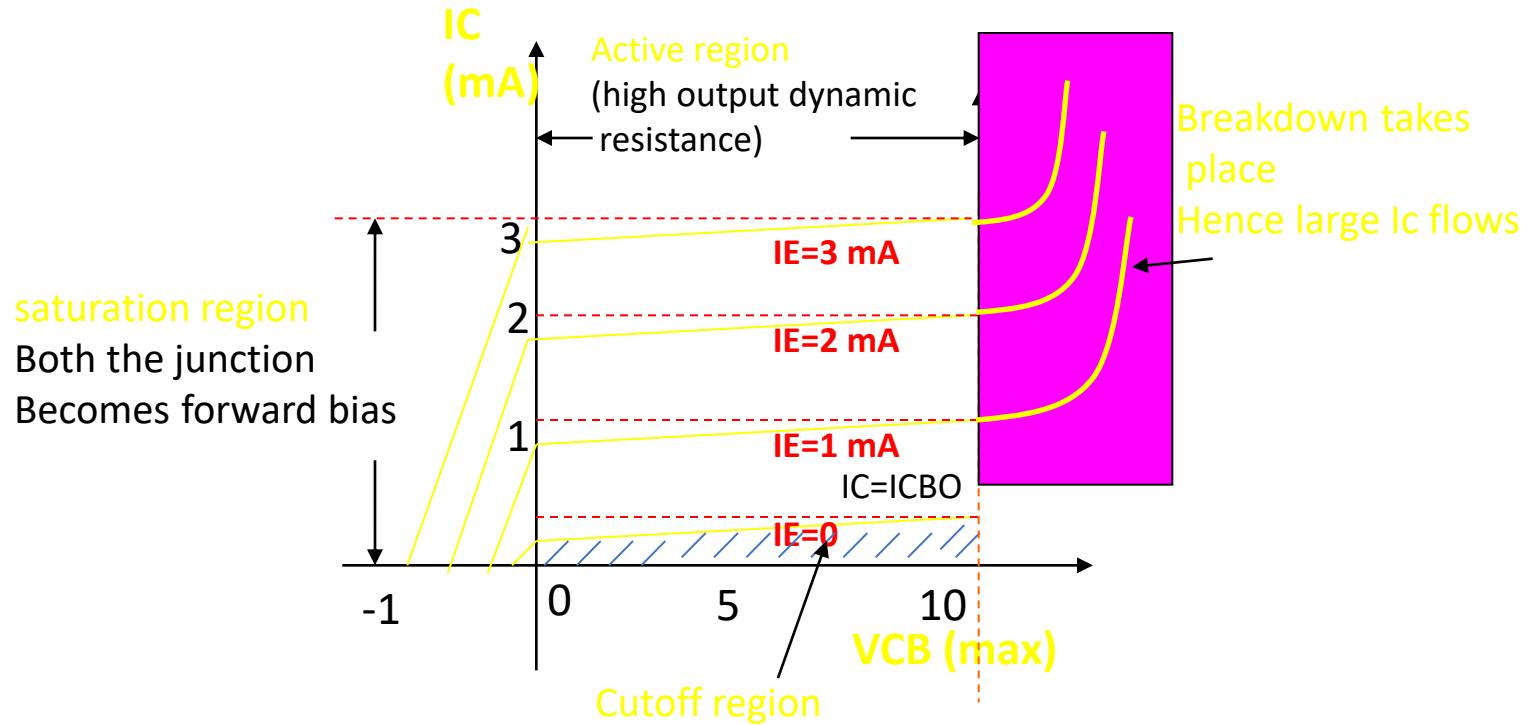

- Due to excessive heat produced by this current, the transistor may get damaged. The type of breakdown is **avalanche breakdown**.

Characteristics of a transistor in CB configuration



Transfer characteristics

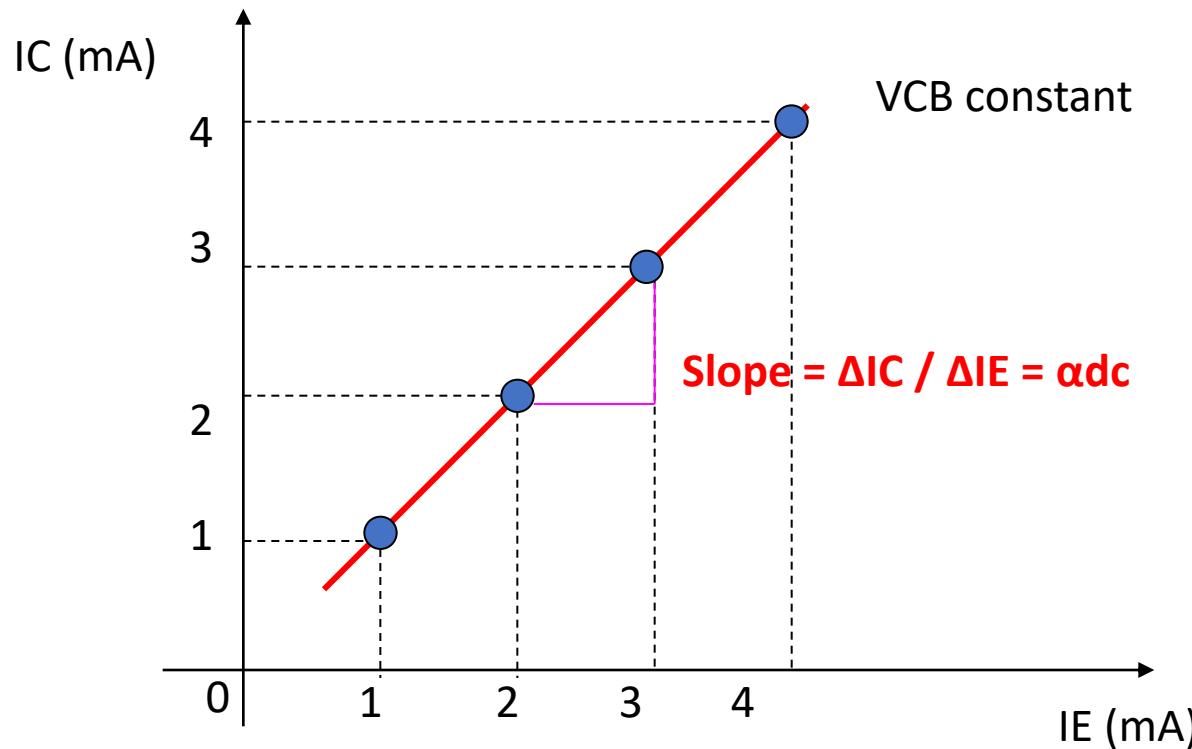

$$\alpha_{dc} = \Delta I_C / \Delta I_E$$

Characteristics of a transistor in CE configuration

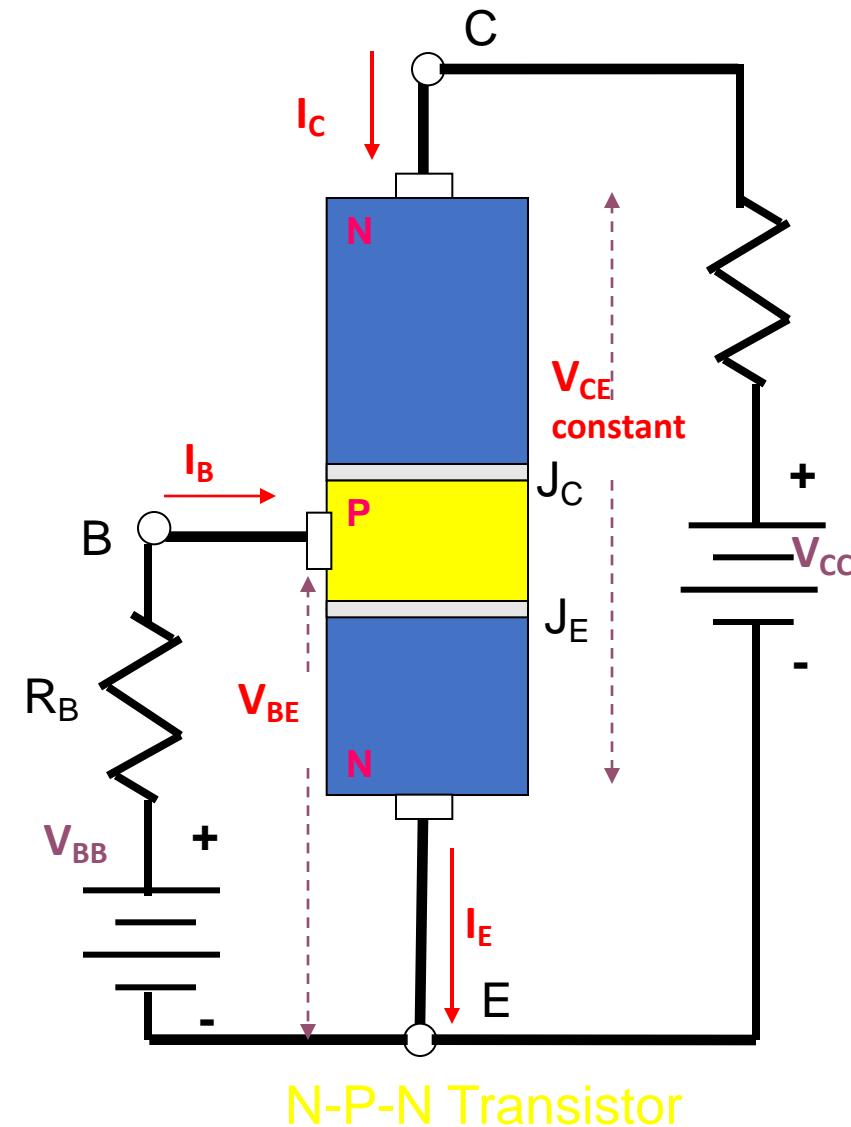
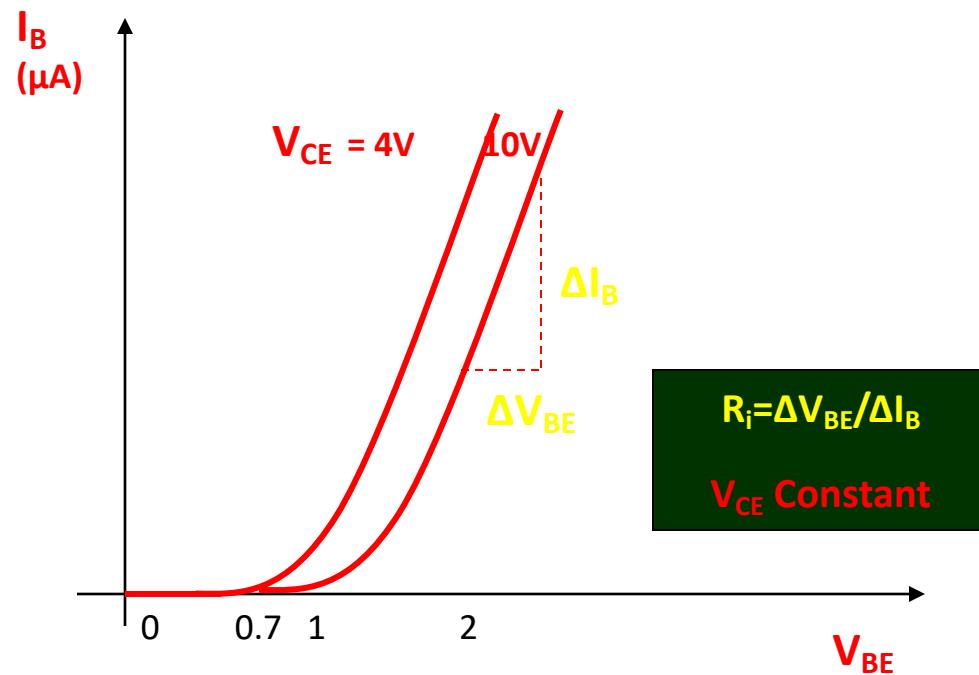
- Input characteristics:
- It is a graph of input current (I_B) versus input voltage (V_{BE}) at a constant output voltage (V_{CE}).



The value of dynamic input resistance “ R_i ” is low for CE


Characteristics of a transistor in CE configuration

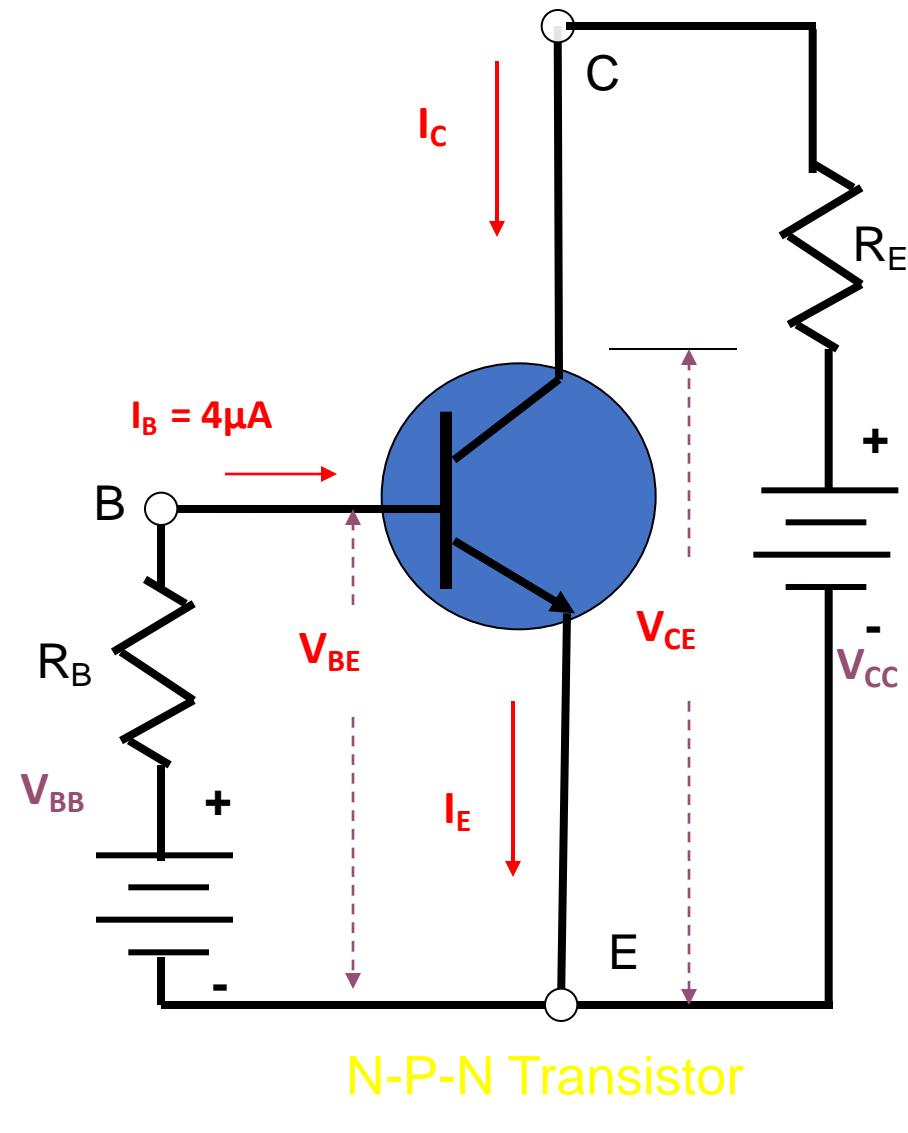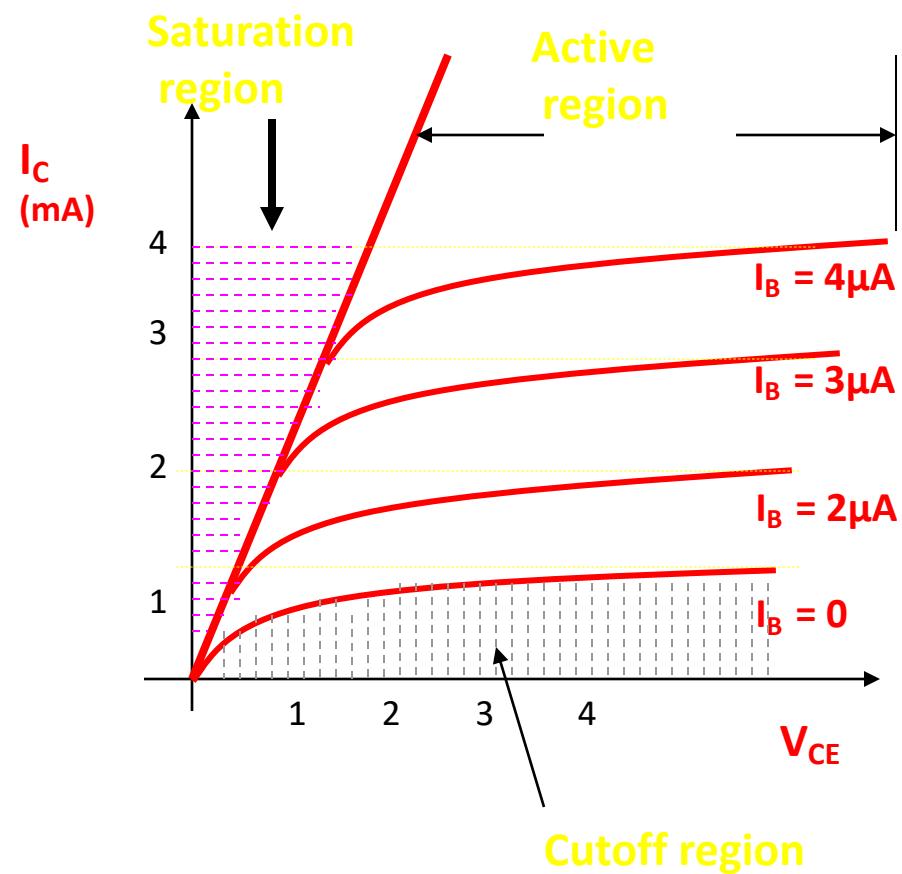- Output characteristics:
- It is a graph of output current (I_c) versus output voltage (V_{CE}) at a constant input current (I_B)



Characteristics of a transistor in CE configuration

Transfer characteristics

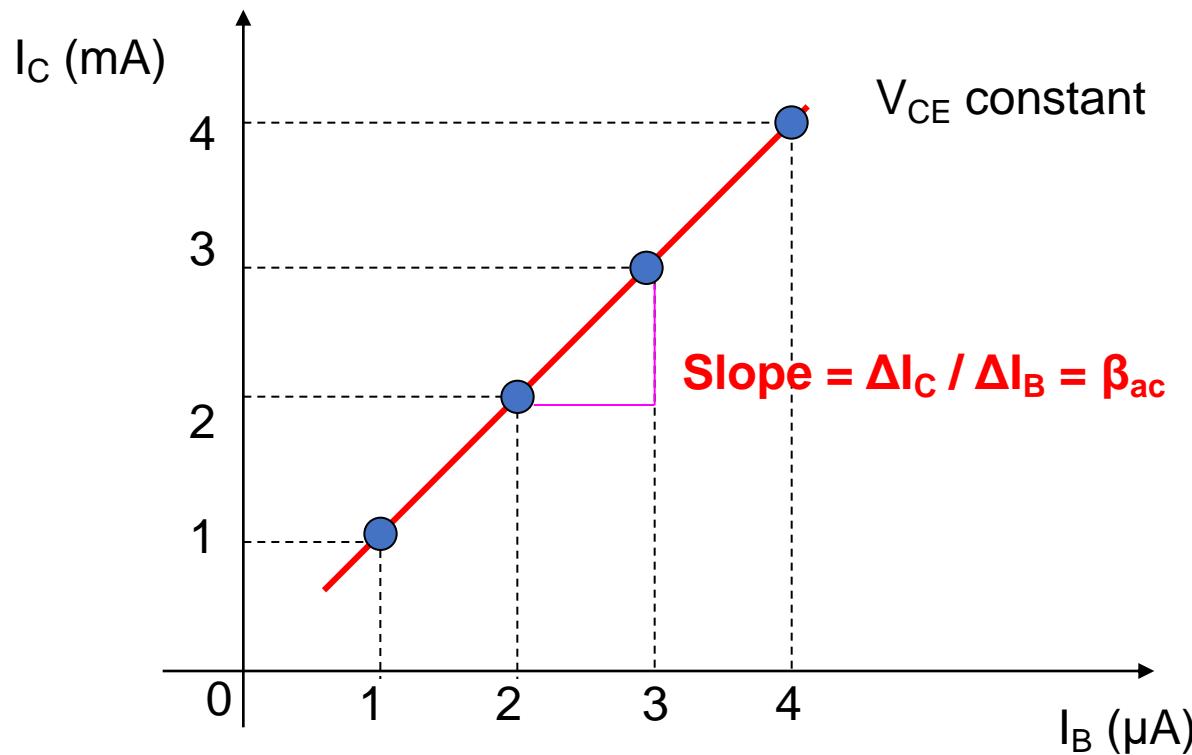

$$\beta_{ac} = \Delta I_C / \Delta I_B$$

$$\beta_{dc} = I_C / I_B$$

V_{CE} constant

Relationship between DC Currents and Gains

$$I_E = I_B + I_C$$

$$\alpha = \frac{I_C}{I_E} = \frac{\beta}{1+\beta}$$

$$I_C = I_E - I_B$$

$$I_B = I_E - I_C \quad \beta = \frac{I_C}{I_B} = \frac{\alpha}{1-\alpha}$$

$$I_B = \frac{I_C}{\beta} = \frac{I_E}{1+\beta} = I_E(1-\alpha)$$

$$I_C = \beta I_B = \alpha I_E$$


$$I_E = \frac{I_C}{\alpha} = I_B(1+\beta)$$

Relationship between DC Currents and Gains

If NPN transistor $I_B = 50\mu A$ and $\alpha = 0.99$ then $I_E = ??$

In a transistor, $I_C = 100mA$ & $I_E = 100.5mA$. The value of $\beta_{DC} = ??$

Bipolar Transistor Configurations

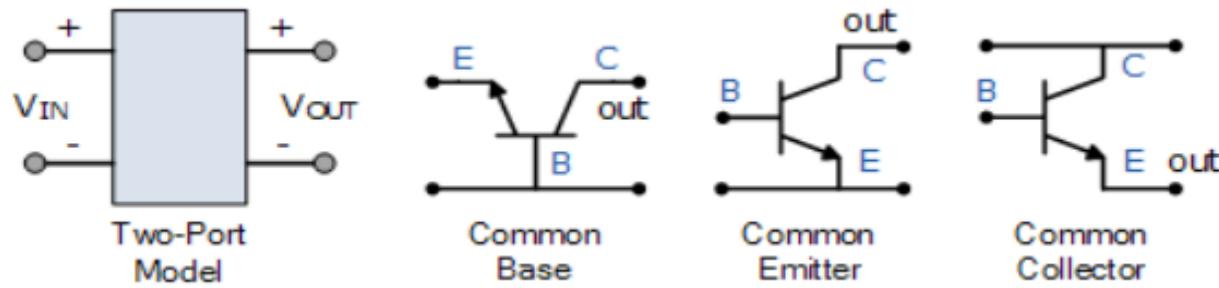


S.No	Characteristics	CB	CE	CC
1	Input impedance	Low	Medium	High
2	Output impedance	High	medium	low
3	Current gain	Low	High	High
4	Voltage gain	High	High	Unity
5	Power gain	Medium	High	Low
6	Phase reversal	No	Yes	No
7	application	AF amplifiers	Voltage & power amplifiers	Impedance matching


DC Load Line

For a transistor circuit to amplify it must be properly biased with dc voltages. The dc operating point between saturation and cutoff is called the **Q-point**. The goal is to set the Q-point such that it does not go into saturation or cutoff when an ac signal is applied.

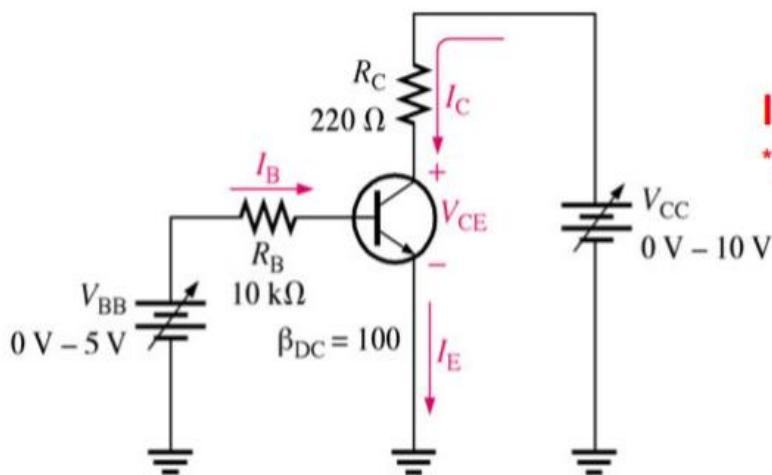
$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = -\left(\frac{1}{R_C}\right)V_{CE} + \frac{V_{CC}}{R_C}$$




(a) DC biased circuit

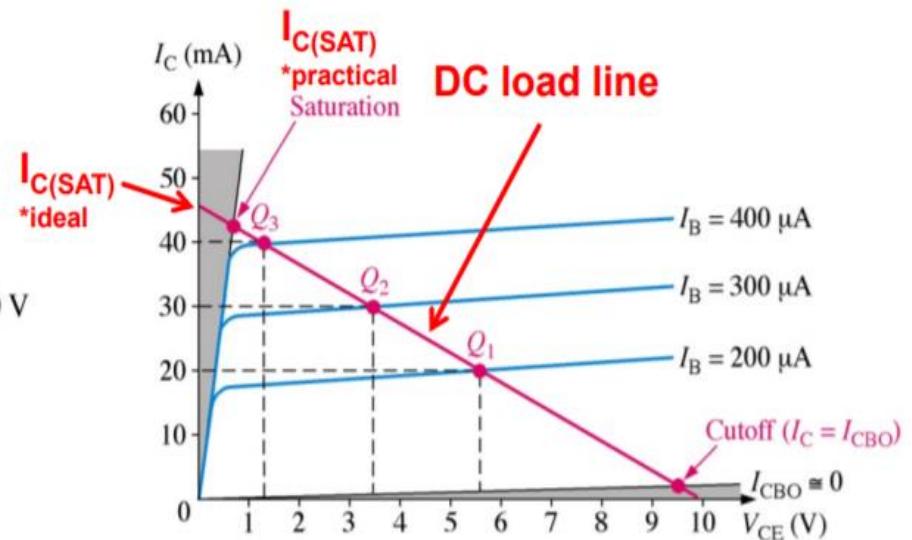


Single stage RC coupled CE amplifier

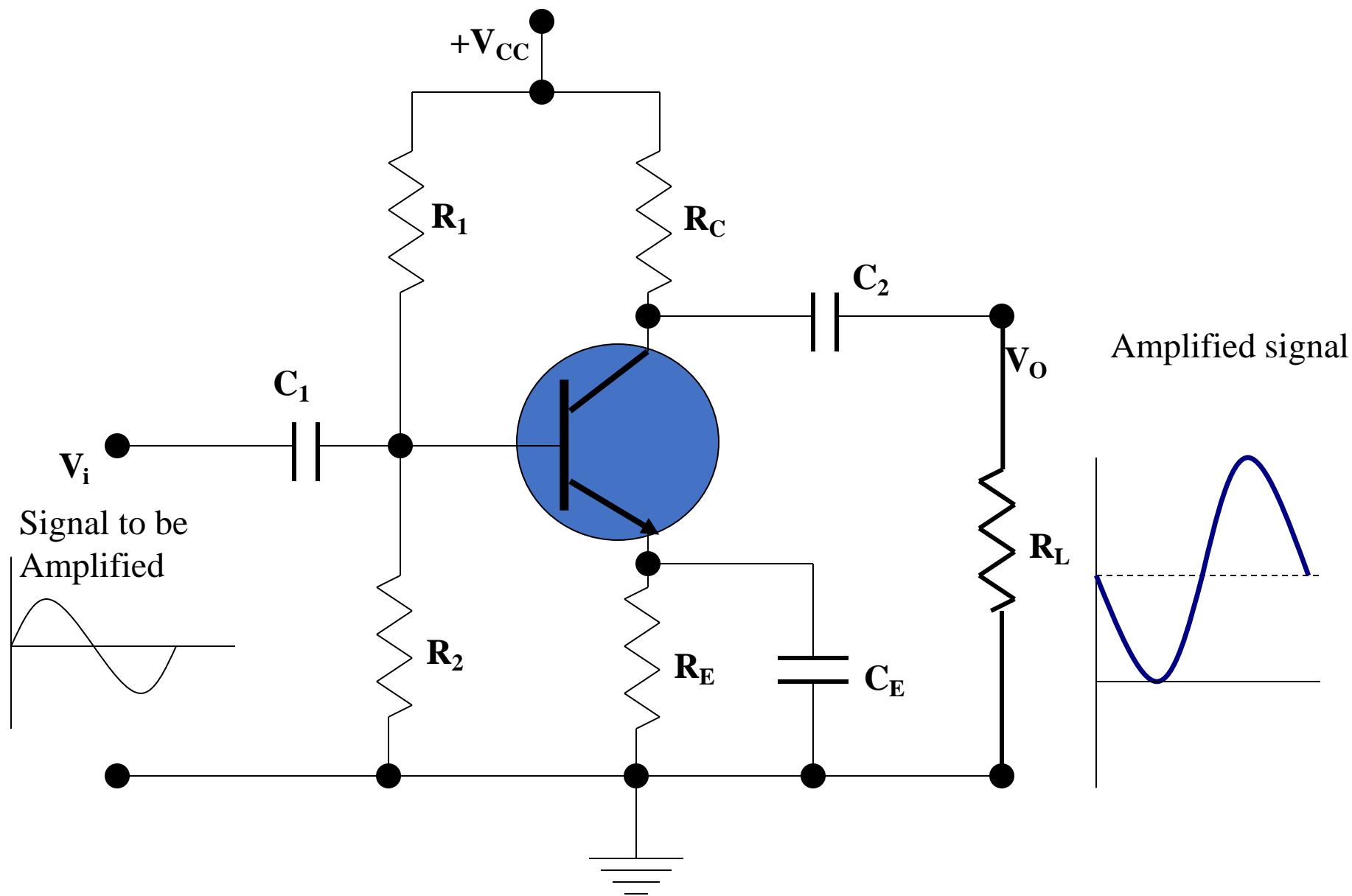


Q- point at the center of DC load line

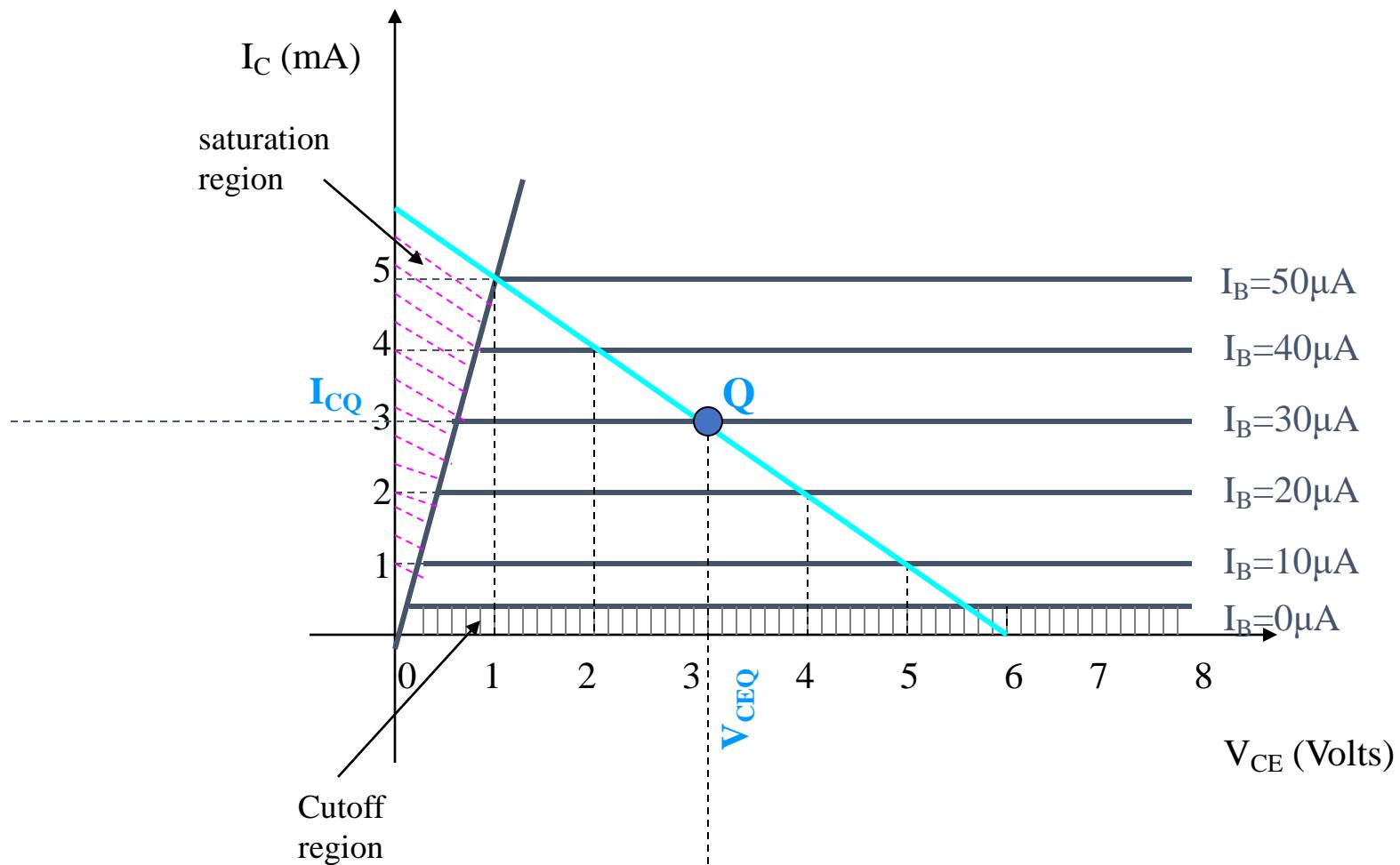


Q- point at the center of DC load line

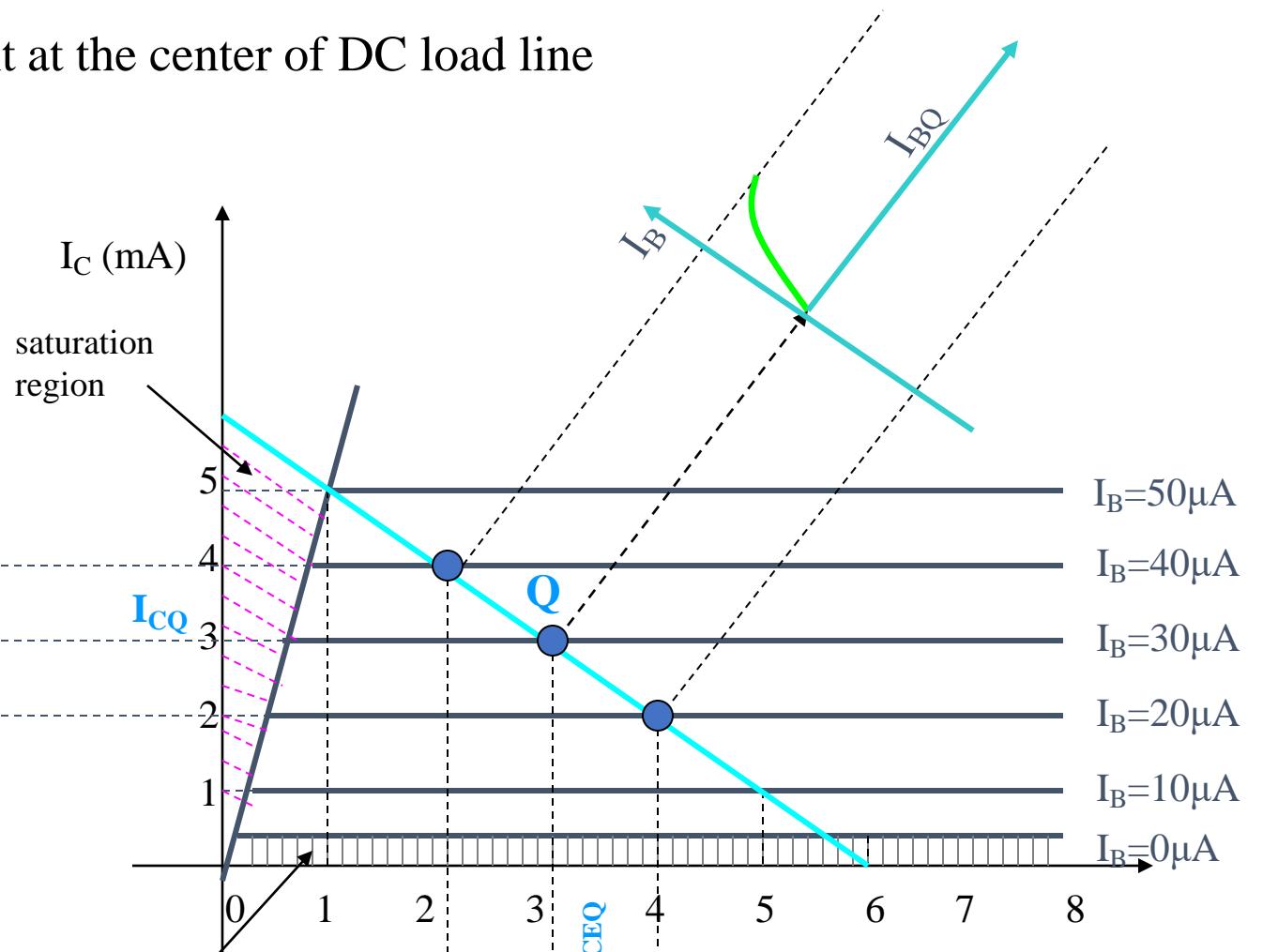


Q- point at the center of DC load line

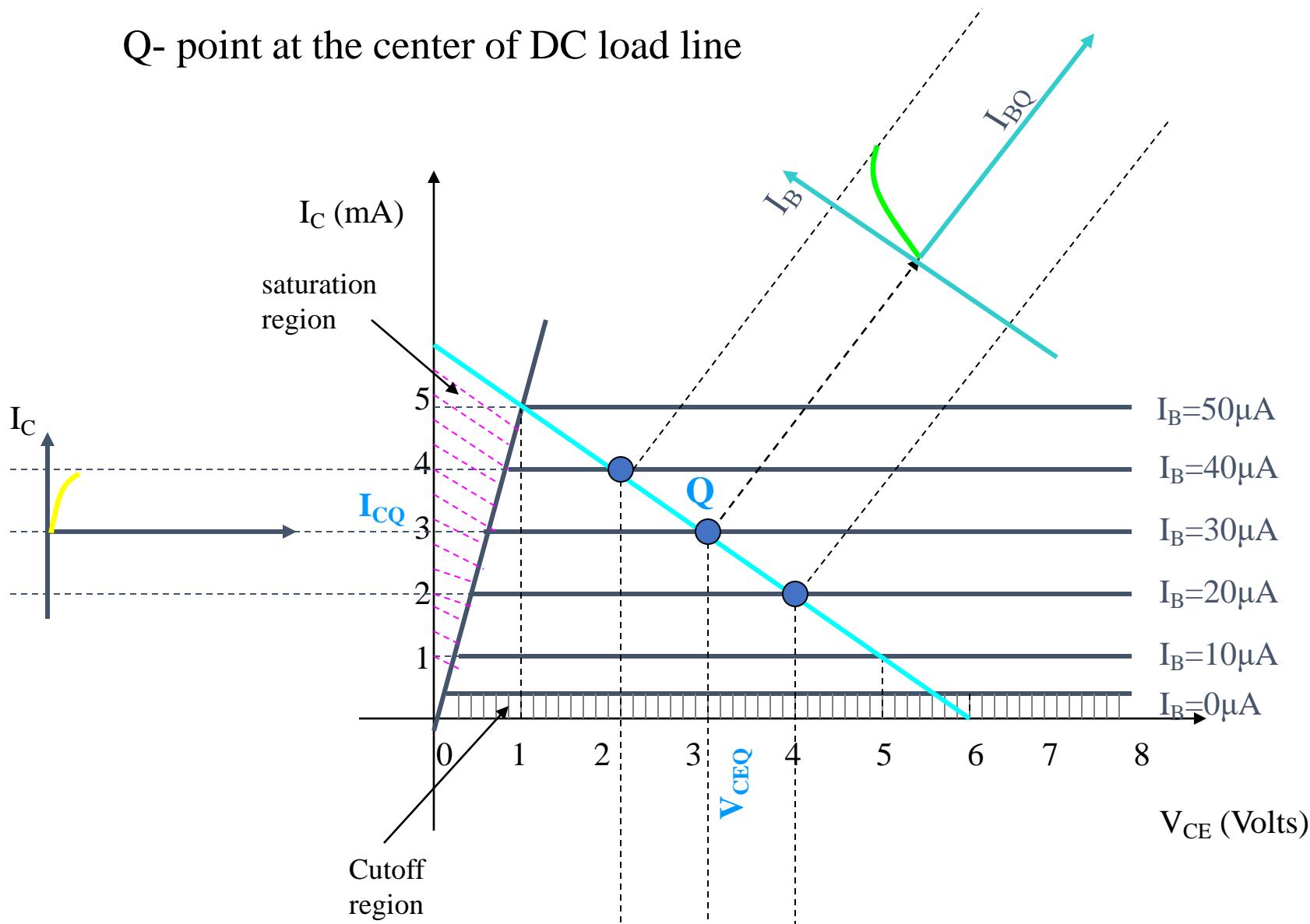


Q- point at the center of DC load line

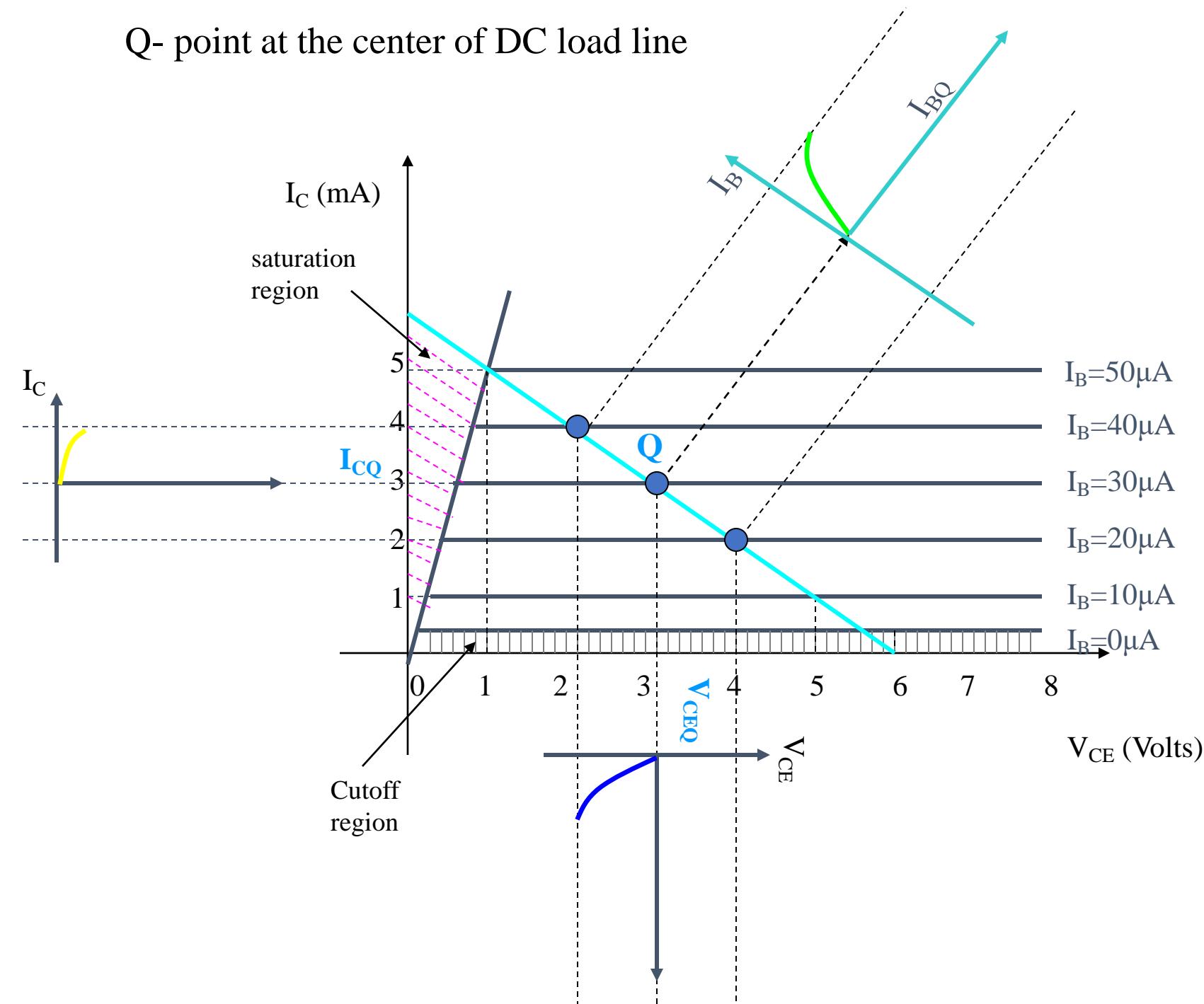


Q- point at the center of DC load line

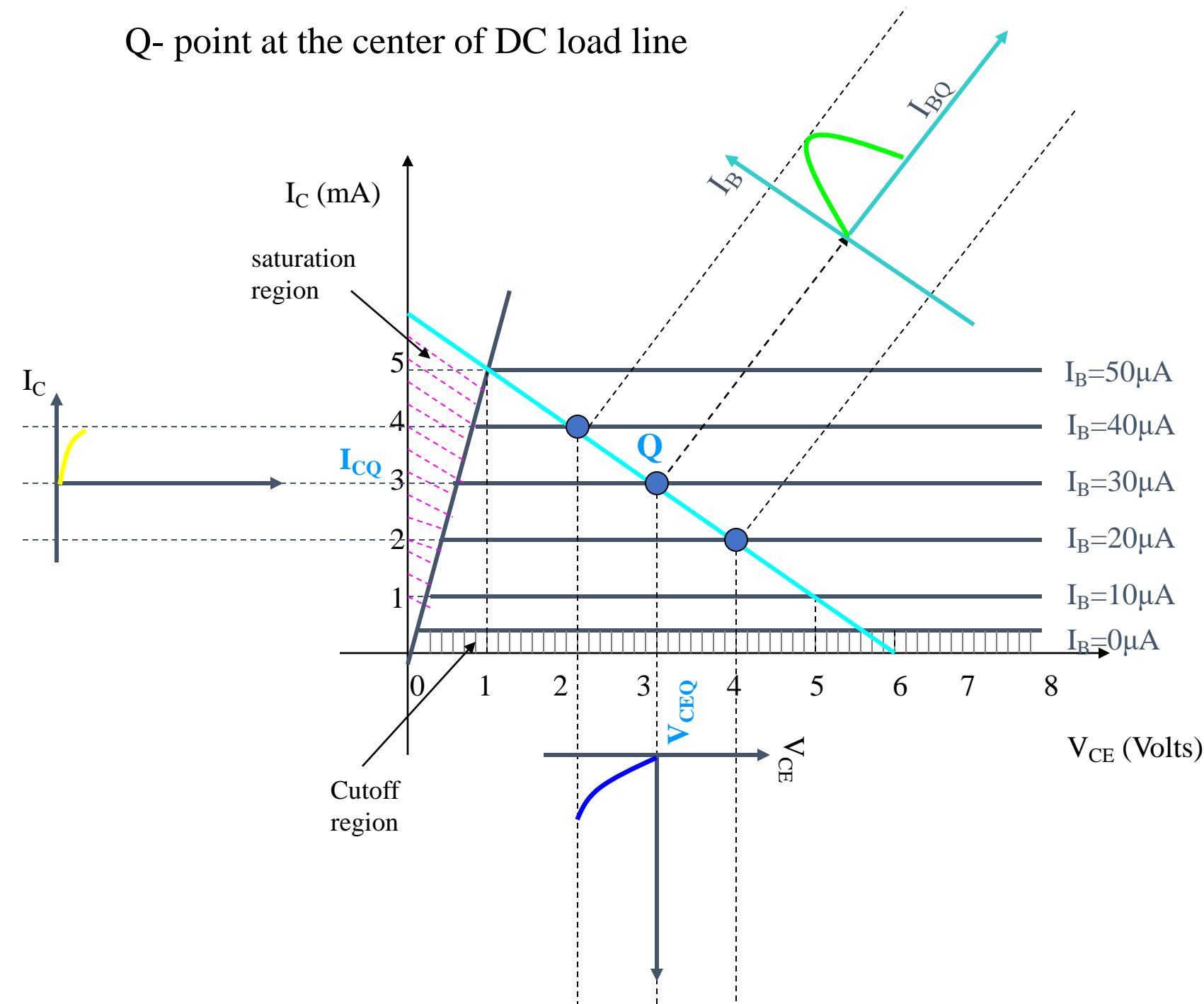


Q-point at the center of DC load line

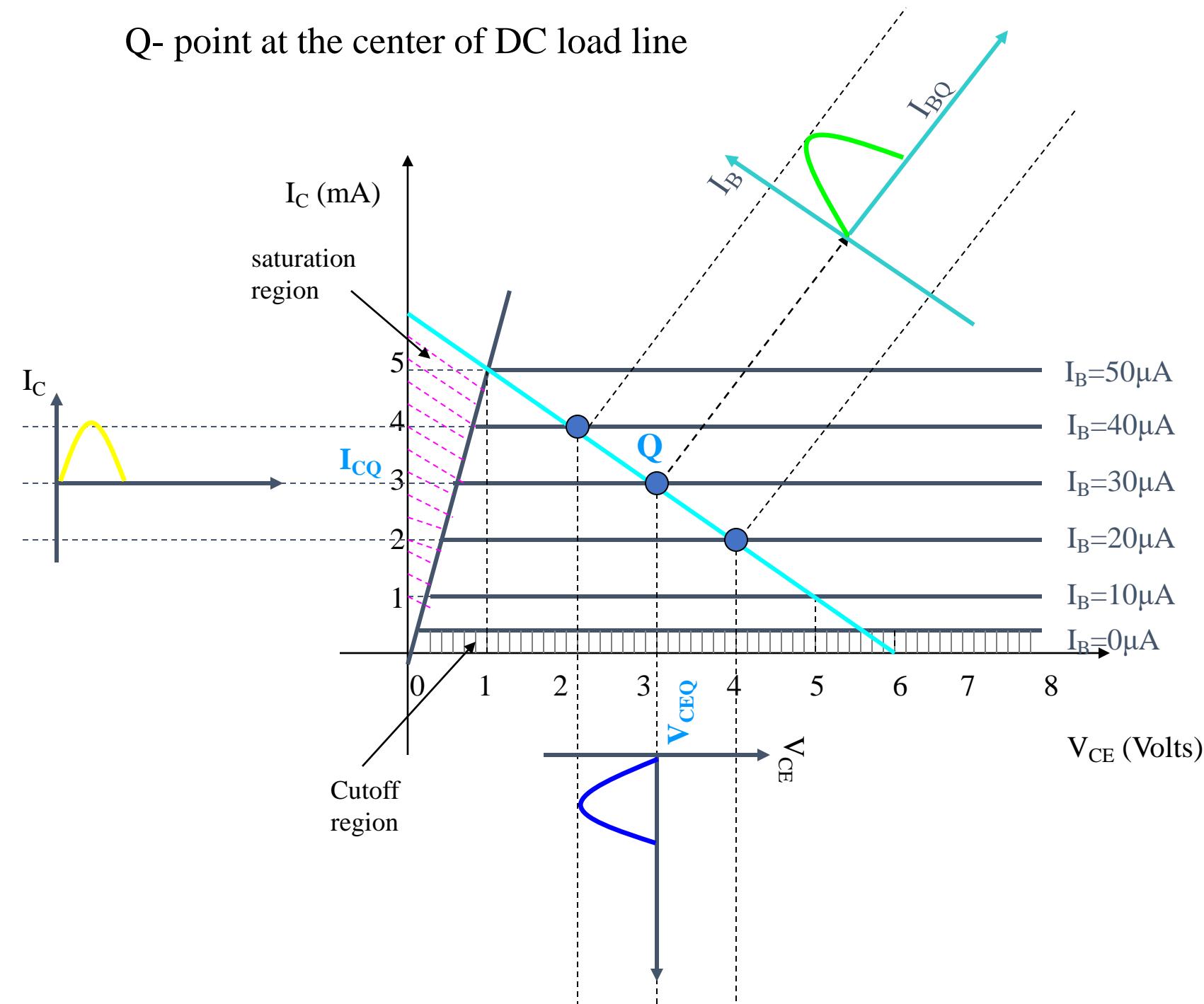


Q- point at the center of DC load line

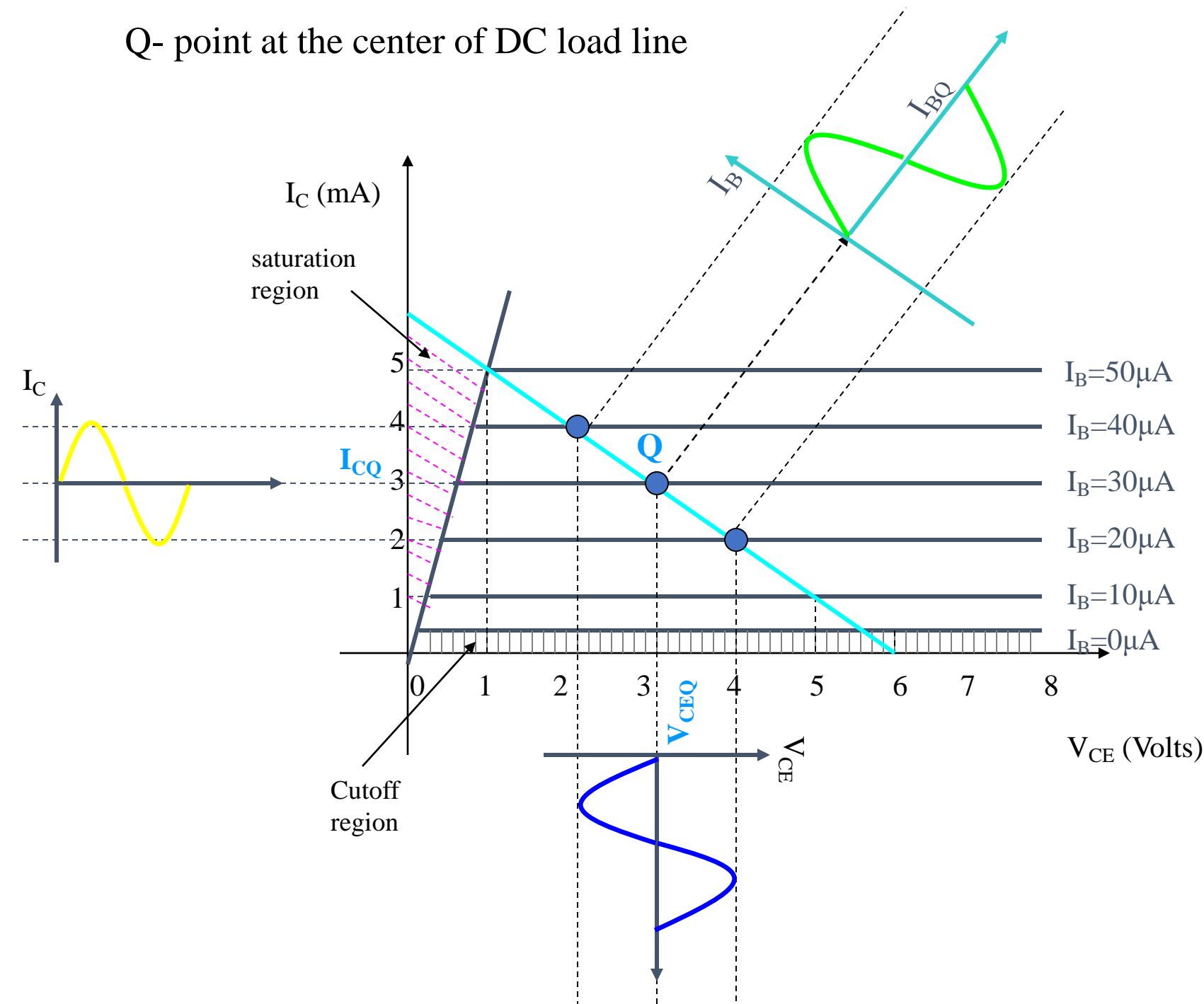

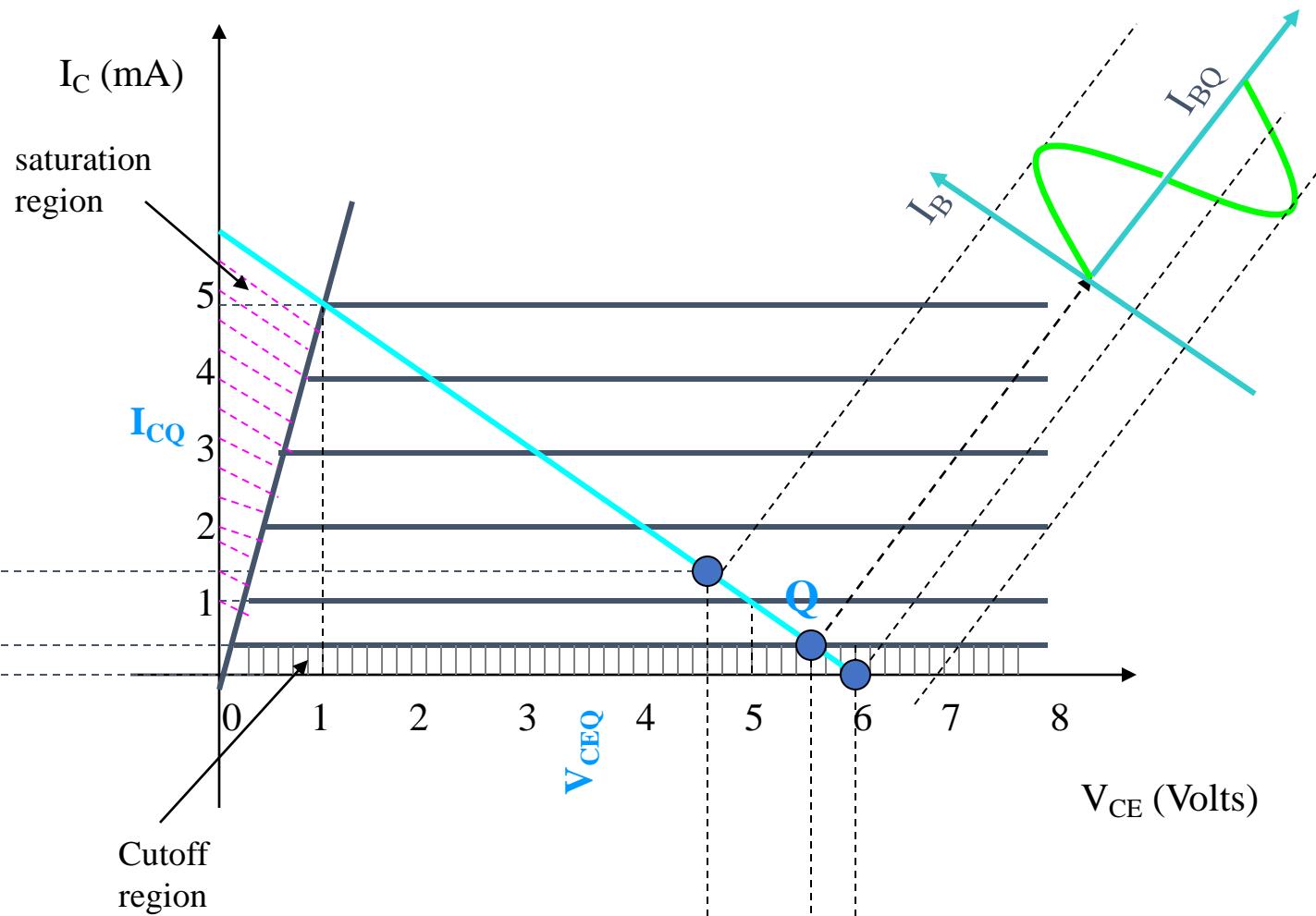
Effect of Q- point close to cutoff region



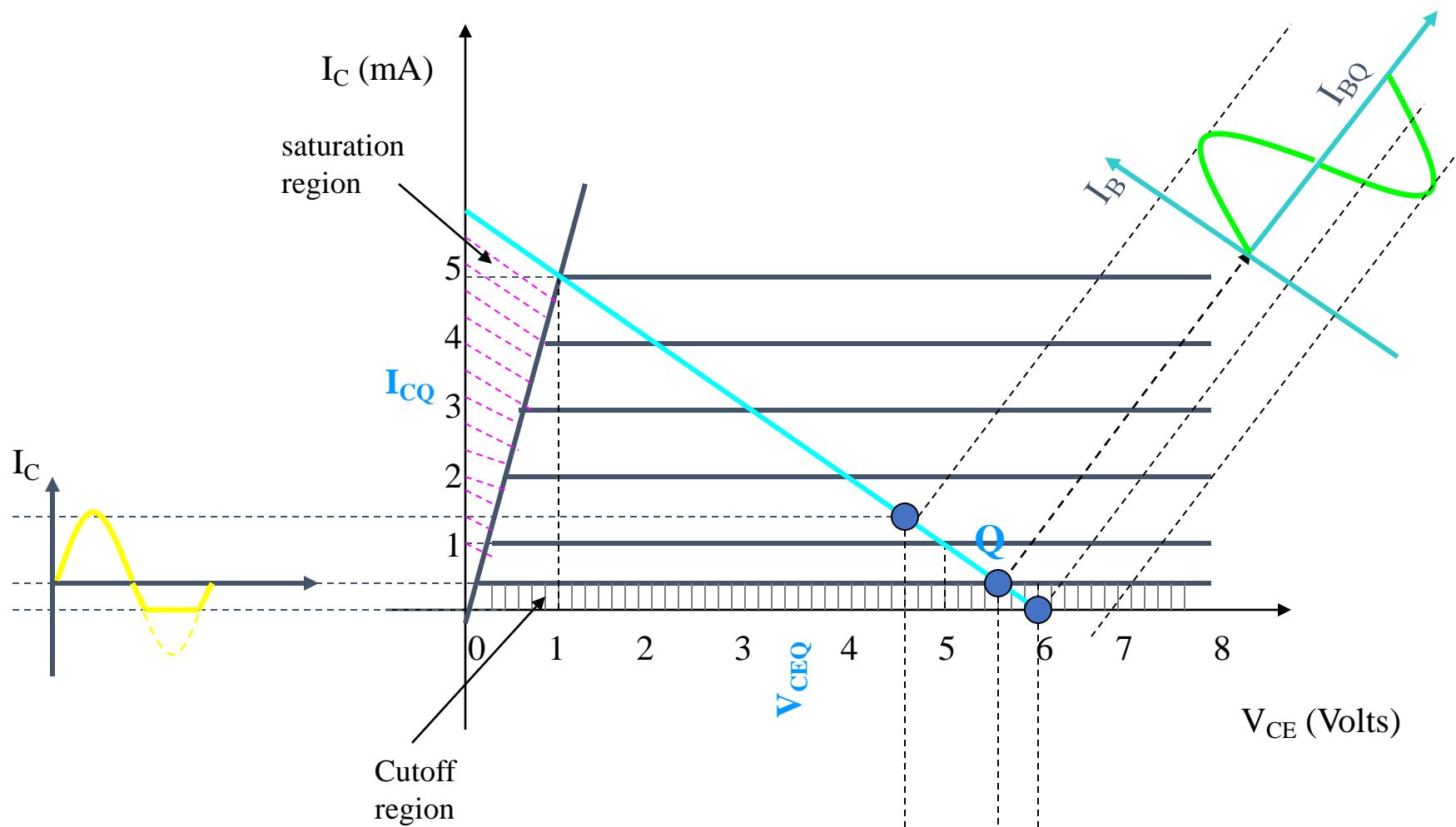
Effect of Q- point close to cutoff region



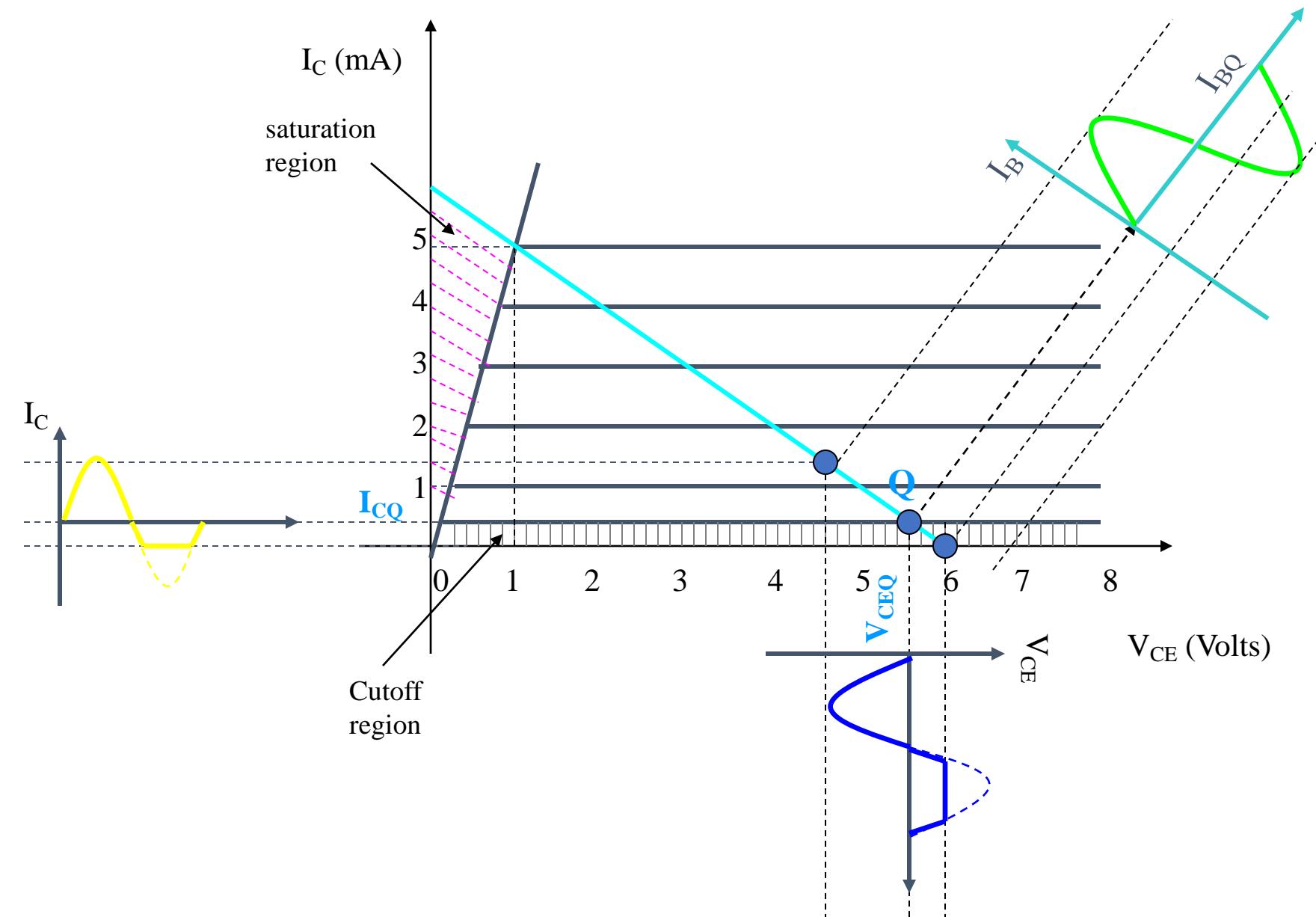
Effect of Q- point close to cutoff region



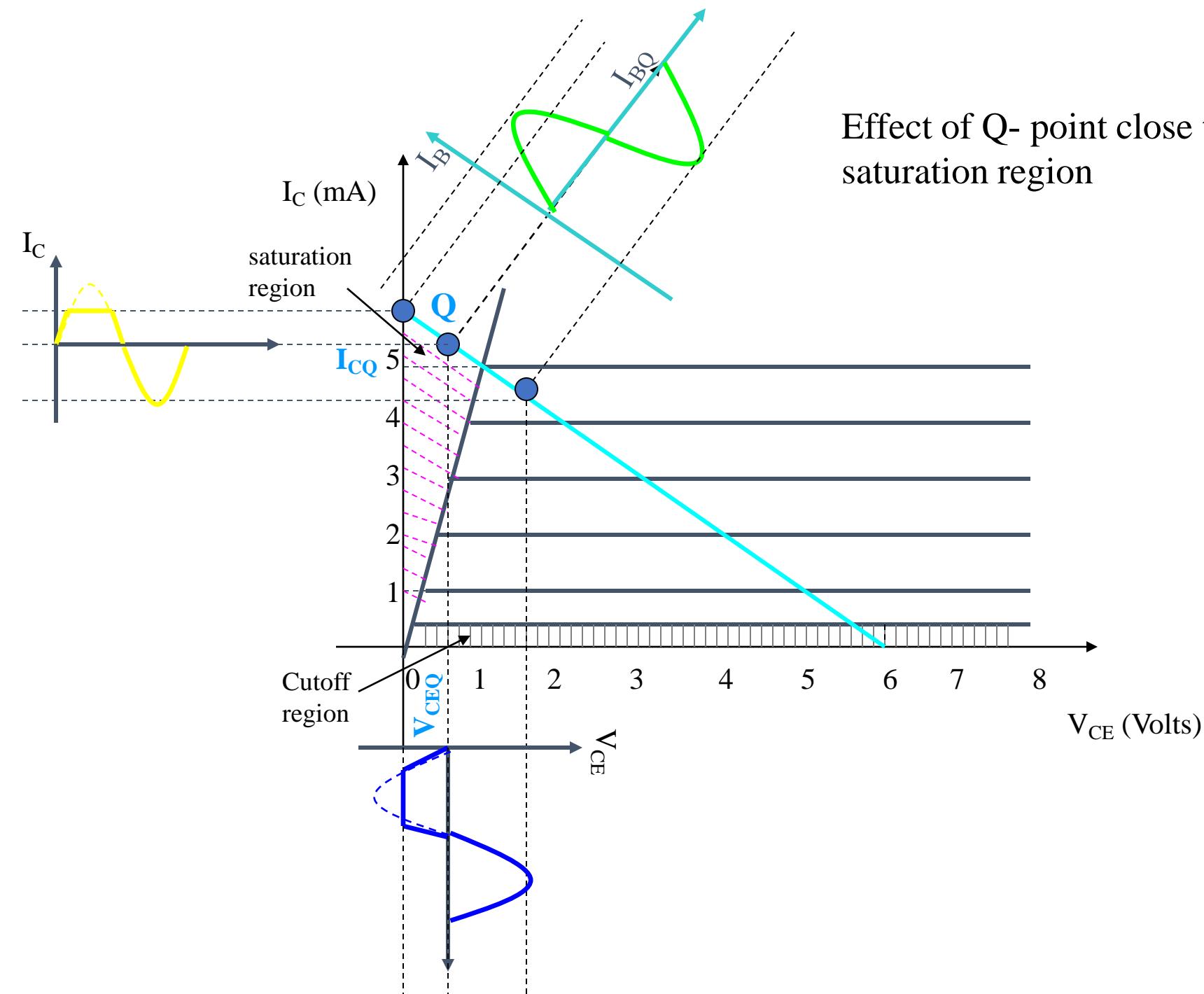
Effect of Q- point close to saturation region




Q- point at the center of DC load line

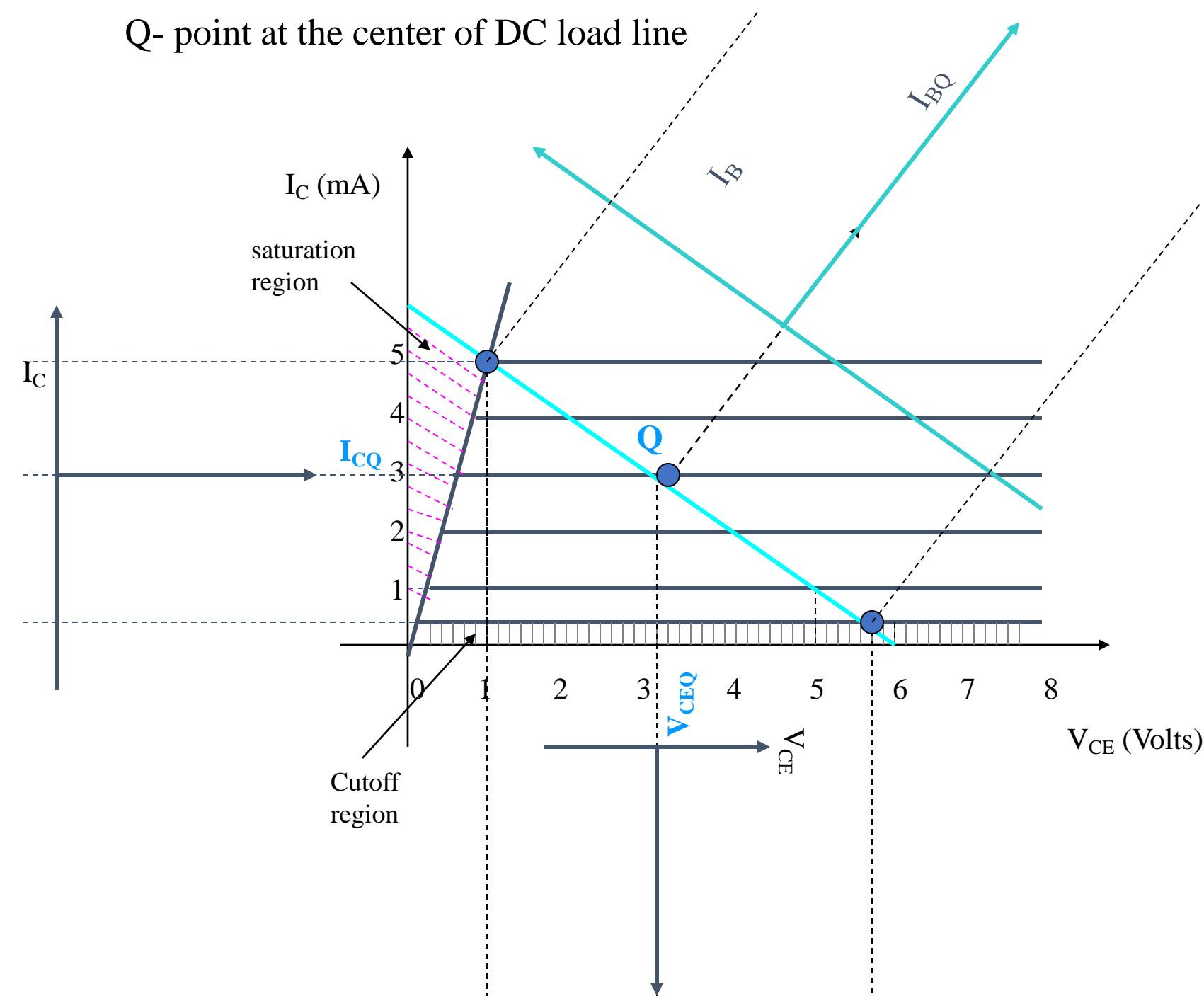


Q- point at the center of DC load line

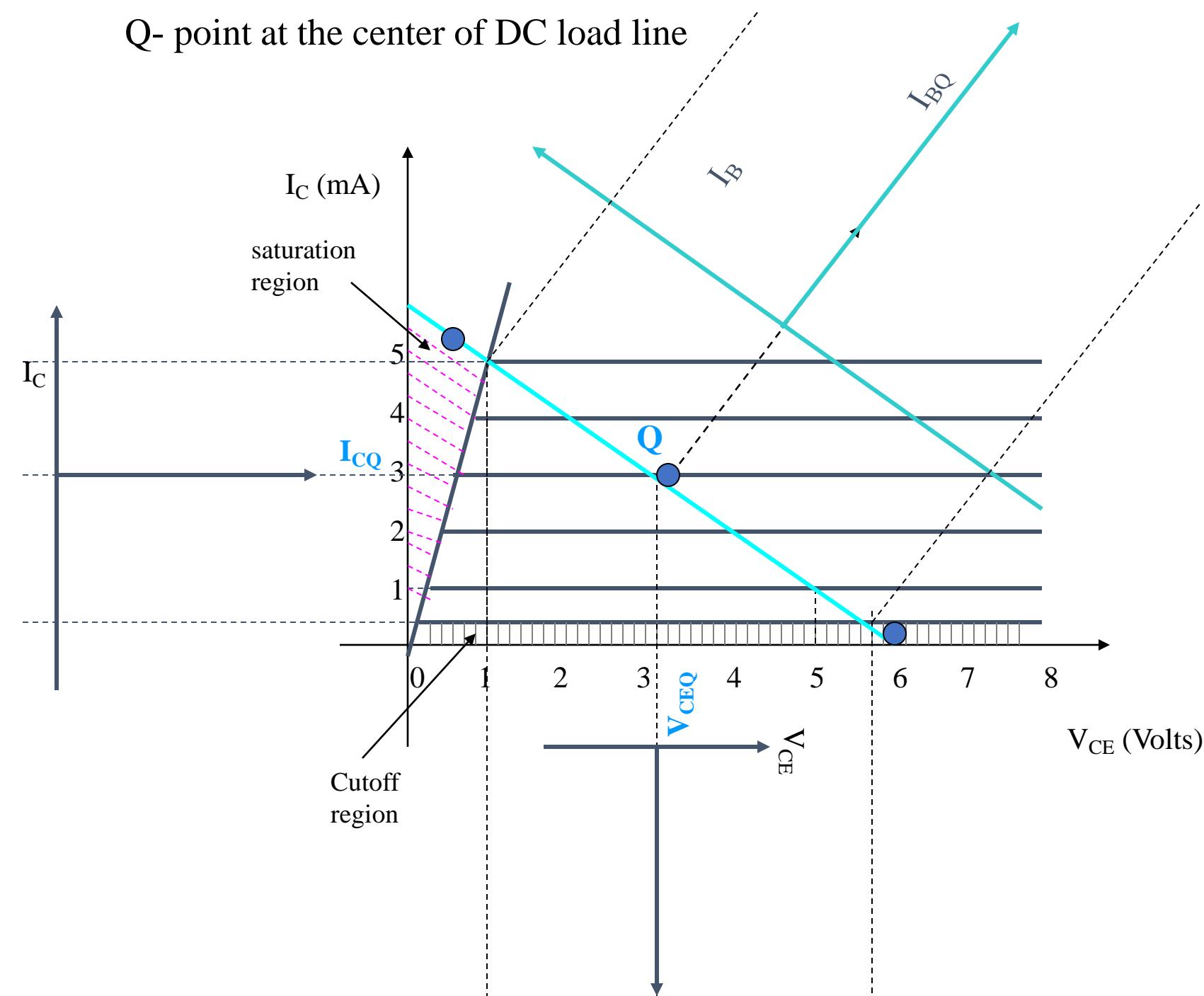


Q- point at the center of DC load line

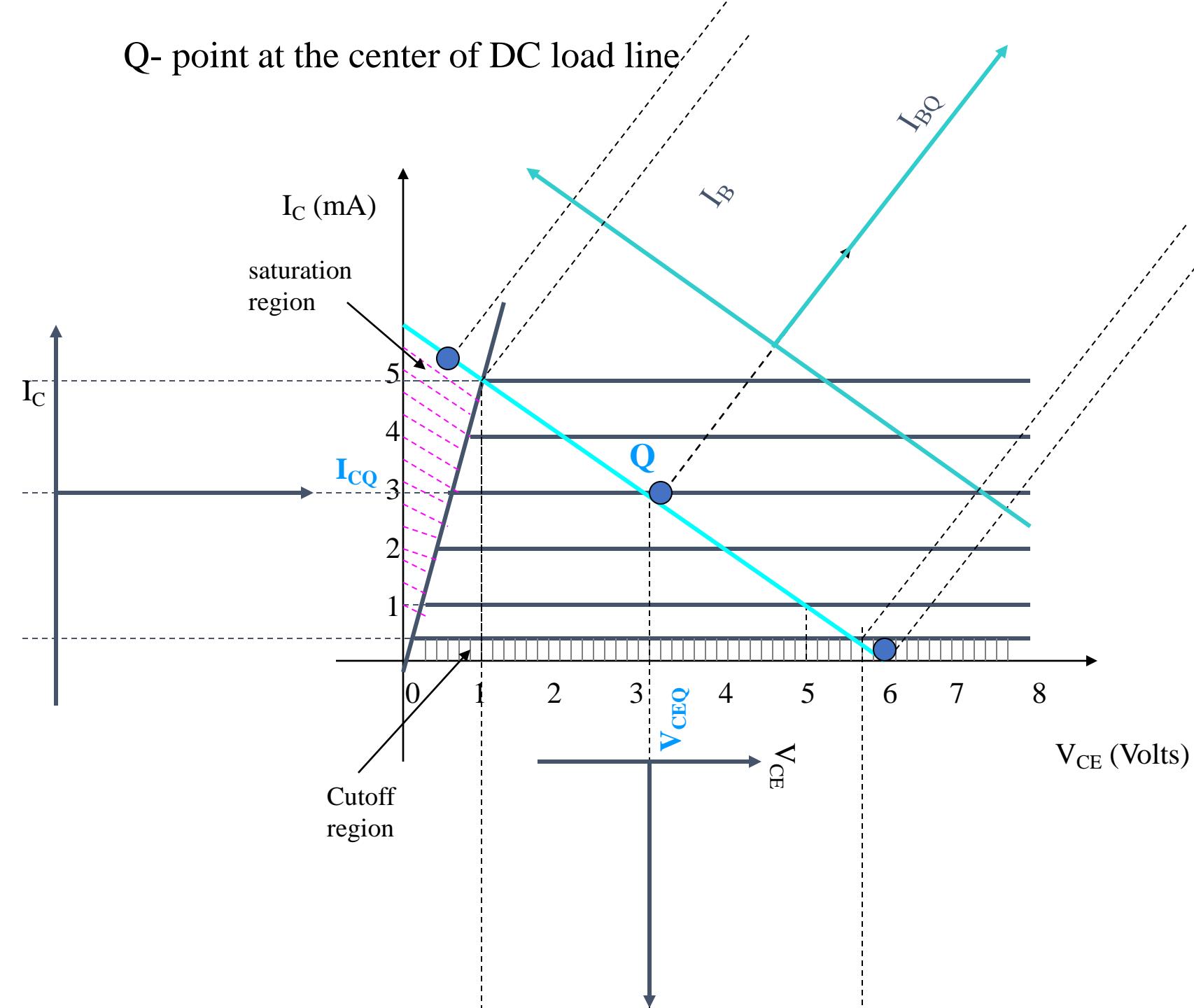

Q- point at the center of DC load line

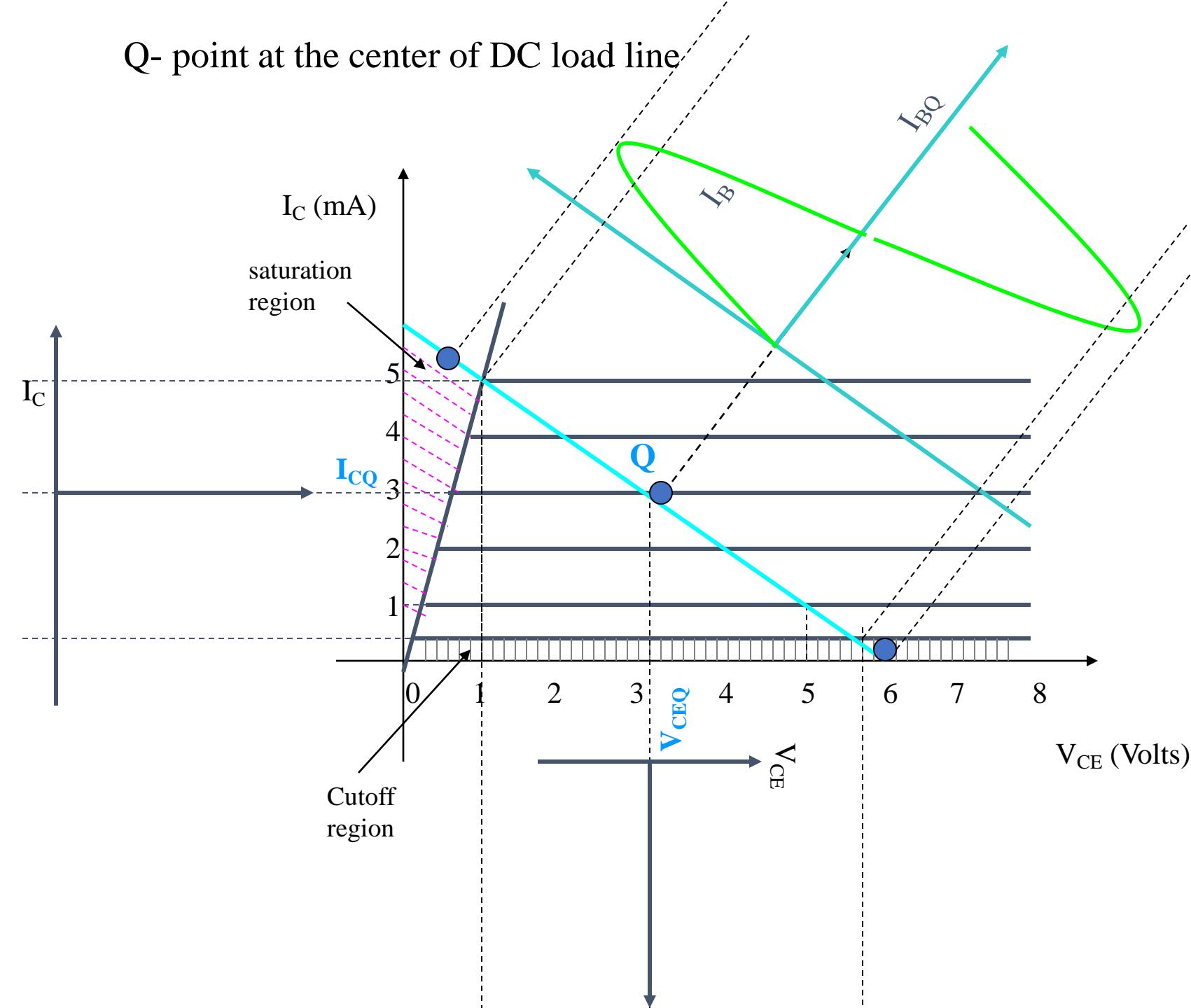


Q- point at the center of DC load line

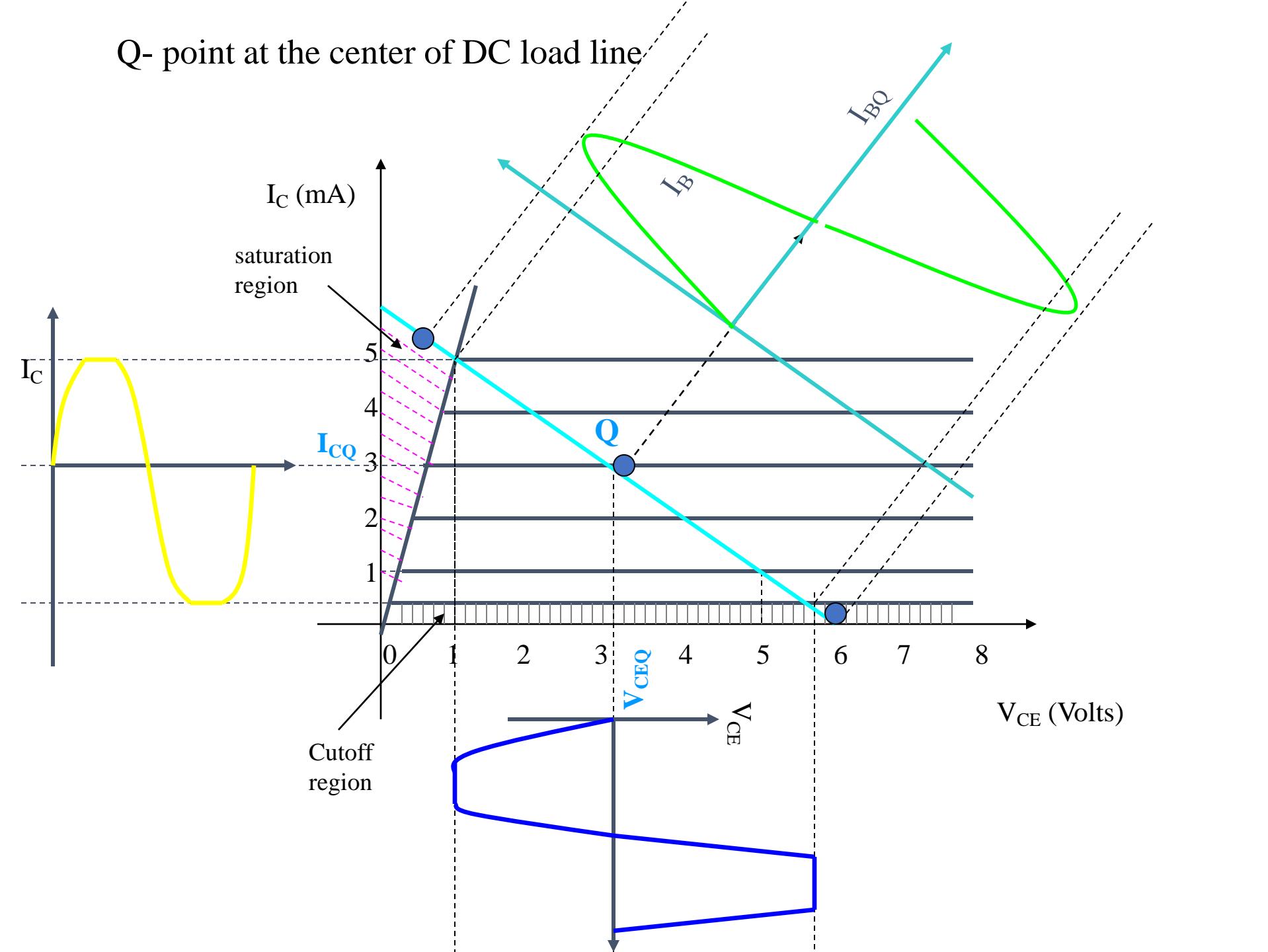


Amplifier Classes

Class	A	B	C	AB
Conduction Angle	360°	180°	Less than 90°	180 to 360°
Position of the Q-point	Centre Point of the Load Line	Exactly on the X-axis	Below the X-axis	In between the X-axis and the Centre Load Line
Overall Efficiency	Poor 25 to 30%	Better 70 to 80%	Higher than 80%	Better than A but less than B 50 to 70%
Signal Distortion	None if Correctly Biased	At the X-axis Crossover Point	Large Amounts	Small Amounts

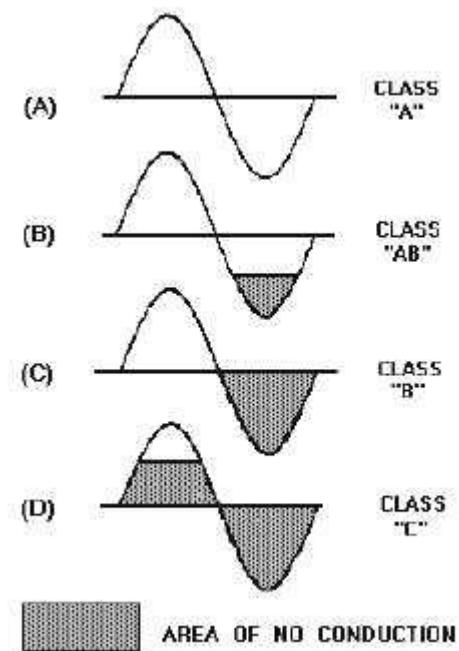


Load Switching


BJT switch using an NPN transistor.

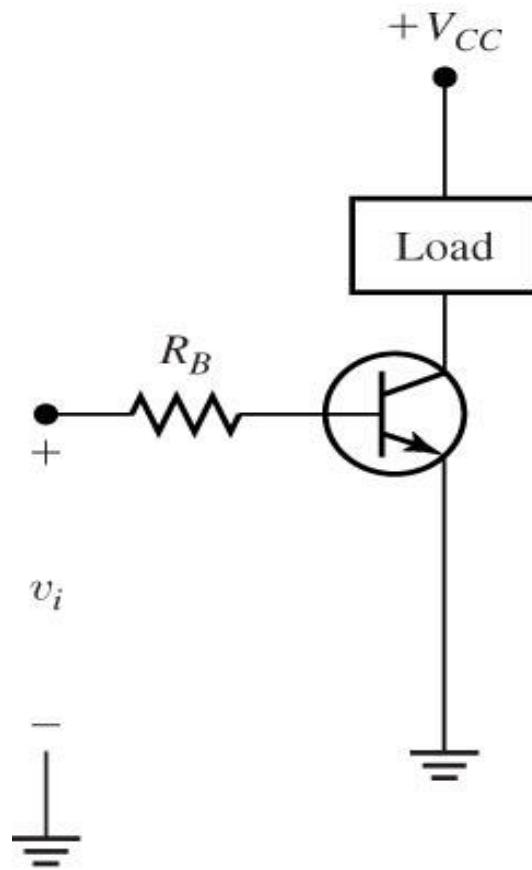

(a)

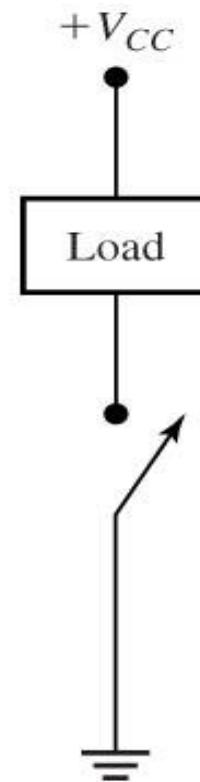


(b) $v_i = 0$

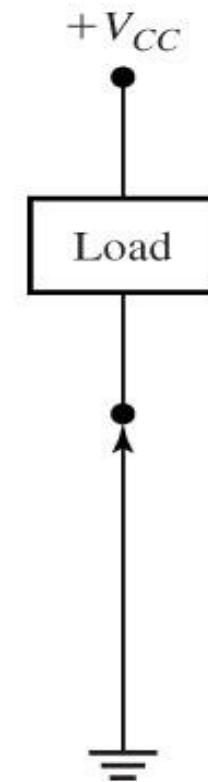


(c) $v_i = V_i$


BJT switch using a PNP transistor.

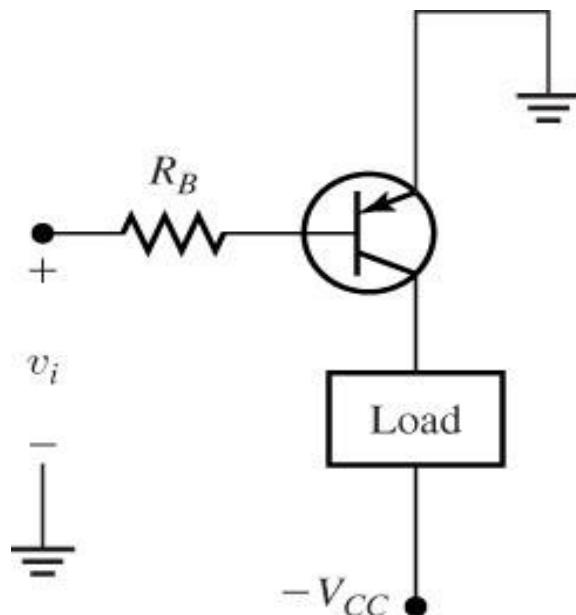

(a)

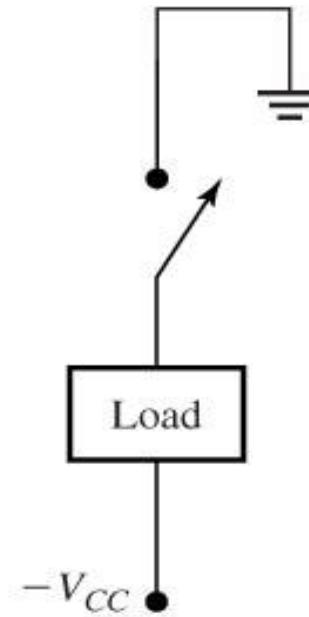

(b) $v_i = 0$

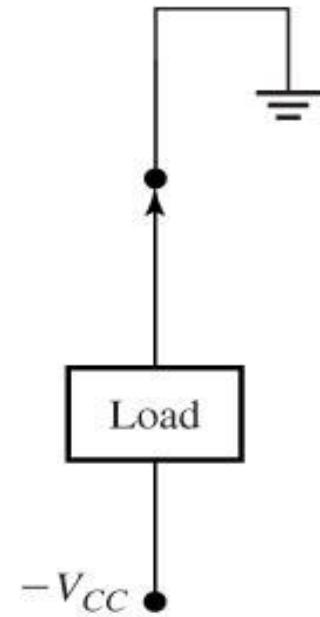

(c) $v_i = -V_i$

BJT as a switch

- In cut off region, both junctions BE & BC are reversed biased.
- Small reverse current flows through transistor.
- Voltage drop across transistor (VCE) is high.
- Hence transistor is like an open switch.
- Input voltage is zero so $IB = IC = 0$

BJT as a switch

Applying KVL to collector ckt.

$$V_{cc} = I_c R_c + V_{CE}$$
$$I_c = 0 \quad \text{so , } V_{cc} = V_{CE}$$


Voltage across transistor CE is very high, equal to V_{cc} & current $I_c = 0$

so

$$V_{cc} = I_c \cdot R$$

$$R = \frac{V_{cc}}{I_c} = \frac{V_{cc}}{0} = \infty$$

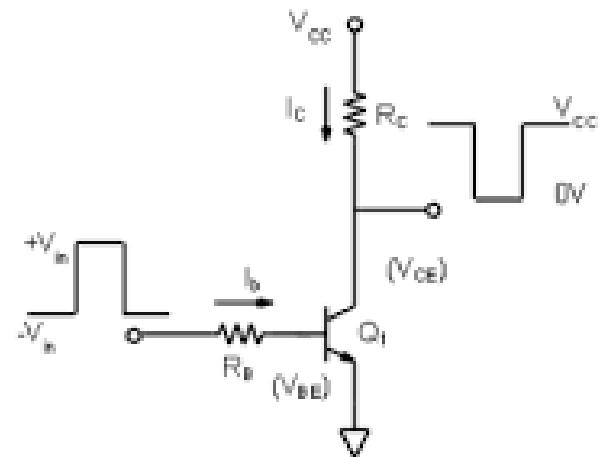Means it offers infinite resistance
 ∞ resistance means open switch.



Transistor in Saturation region

- High input voltage V_{in} is applied at the base.
- R_B value is adjusted such that it satisfies the condition,


$$I_B \geq I_C(\text{sat})/\beta$$

In saturation region, both junctions are FB,
Voltage drop across transistor (V_{CE}) is very small



Low voltage drop, 0.2V (almost zero) & large current through it indicates zero resistance.

$$V = I \cdot R$$

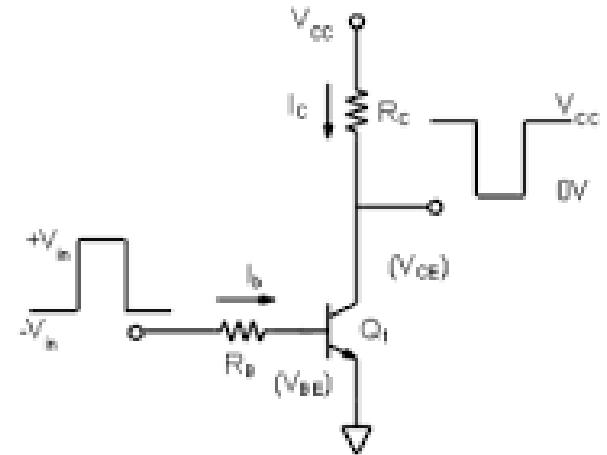$0 = I \cdot R$ Hence $R = 0$ so transistor is equivalent to closed switch.



BJT as a switch

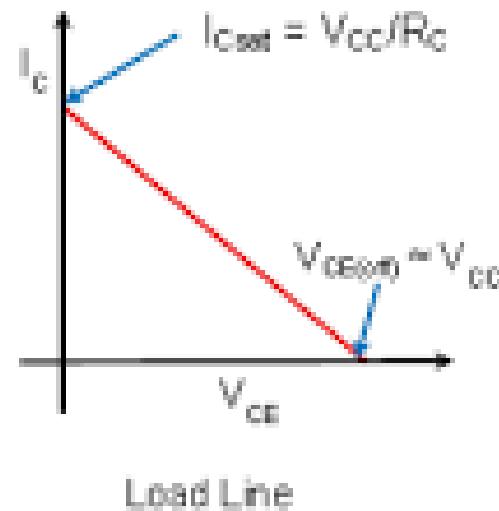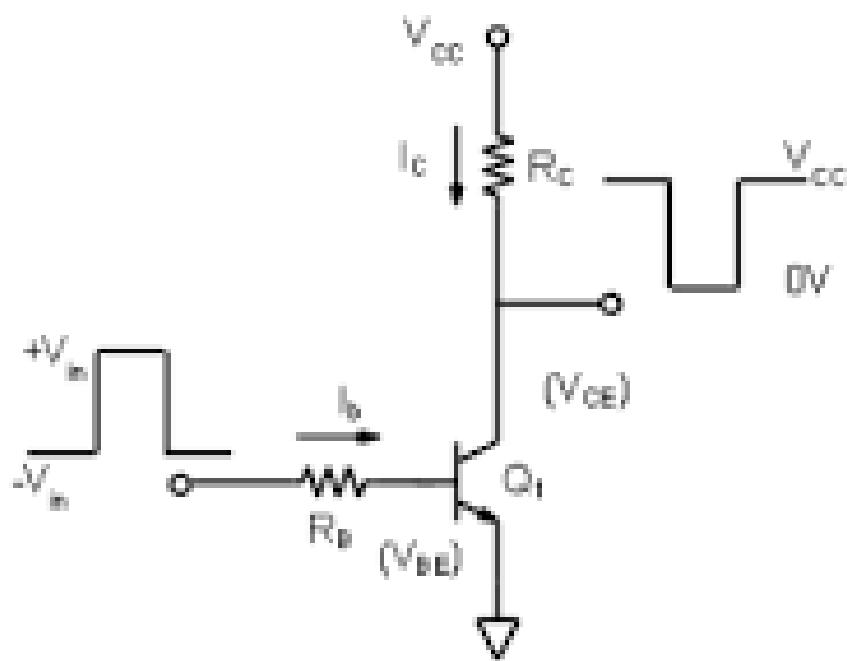

Transistor as an Off switch

A switching circuit

i) Transistor as an OFF switch

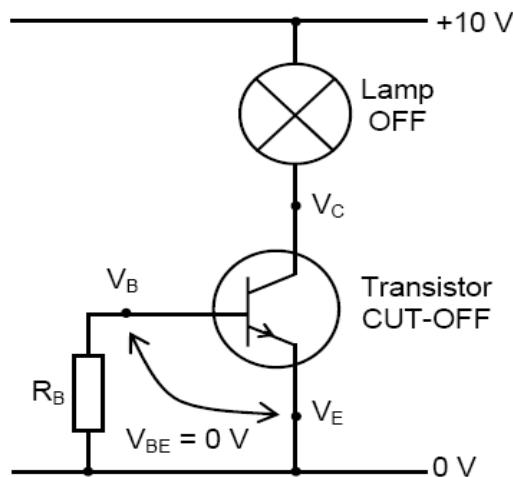


Fig. 5.25(a) – Transistor in CUT-OFF Condition (no current)

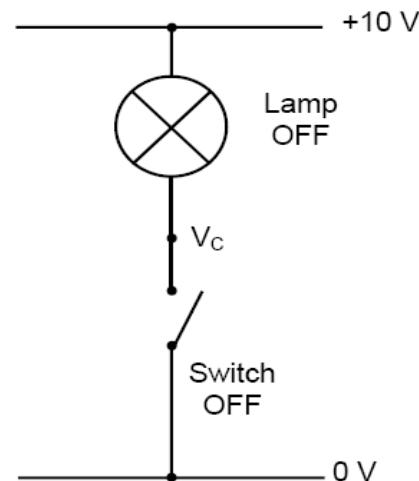


Fig. 5.25(b) – Transistor compared to switch

Transistor in Saturation region

ii) Transistor as an ON switch

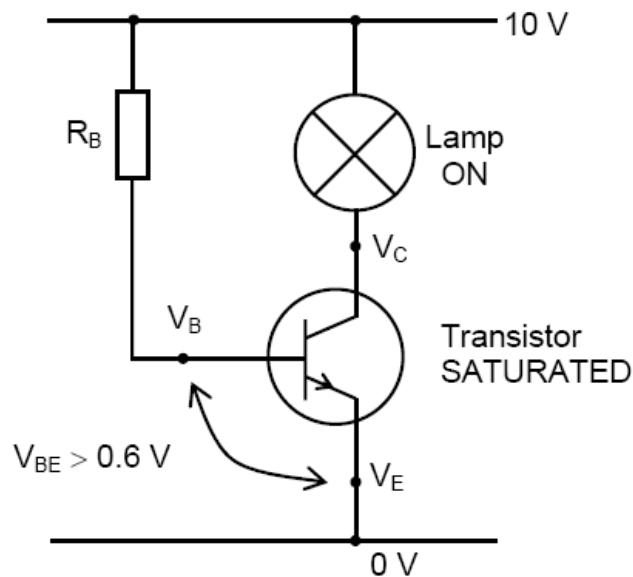


Fig. 5.26(a) – Transistor in SATURATED Condition (maximum current)


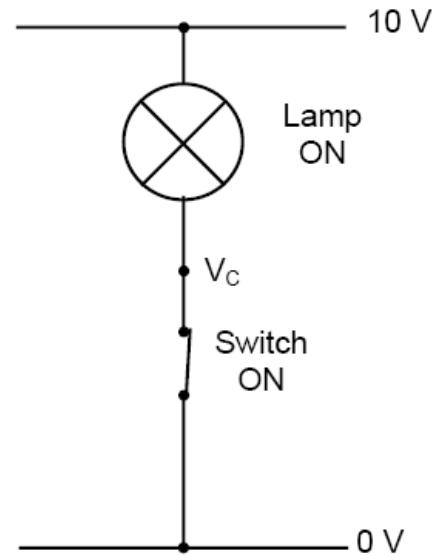



Fig. 5.26(b)

BJT as a switch

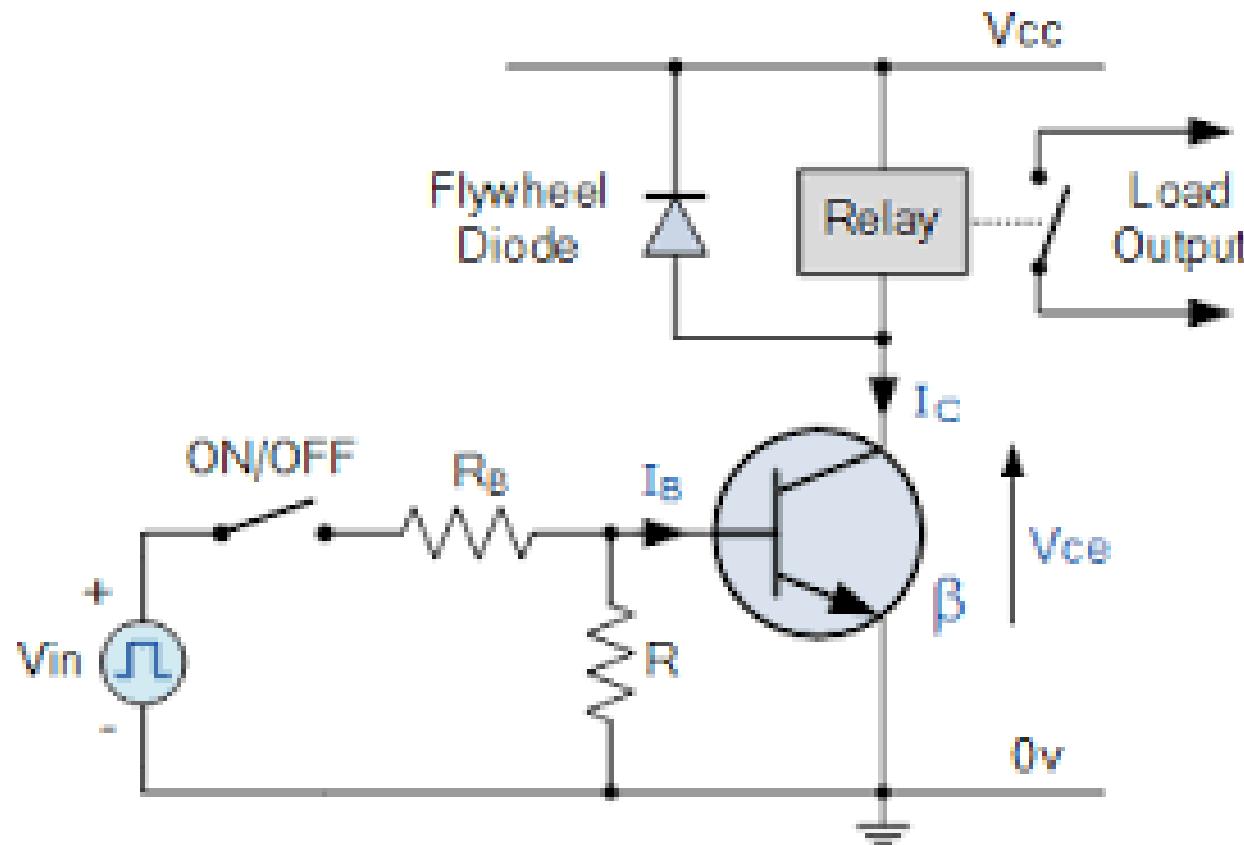


Field Effect Transistors (FET)

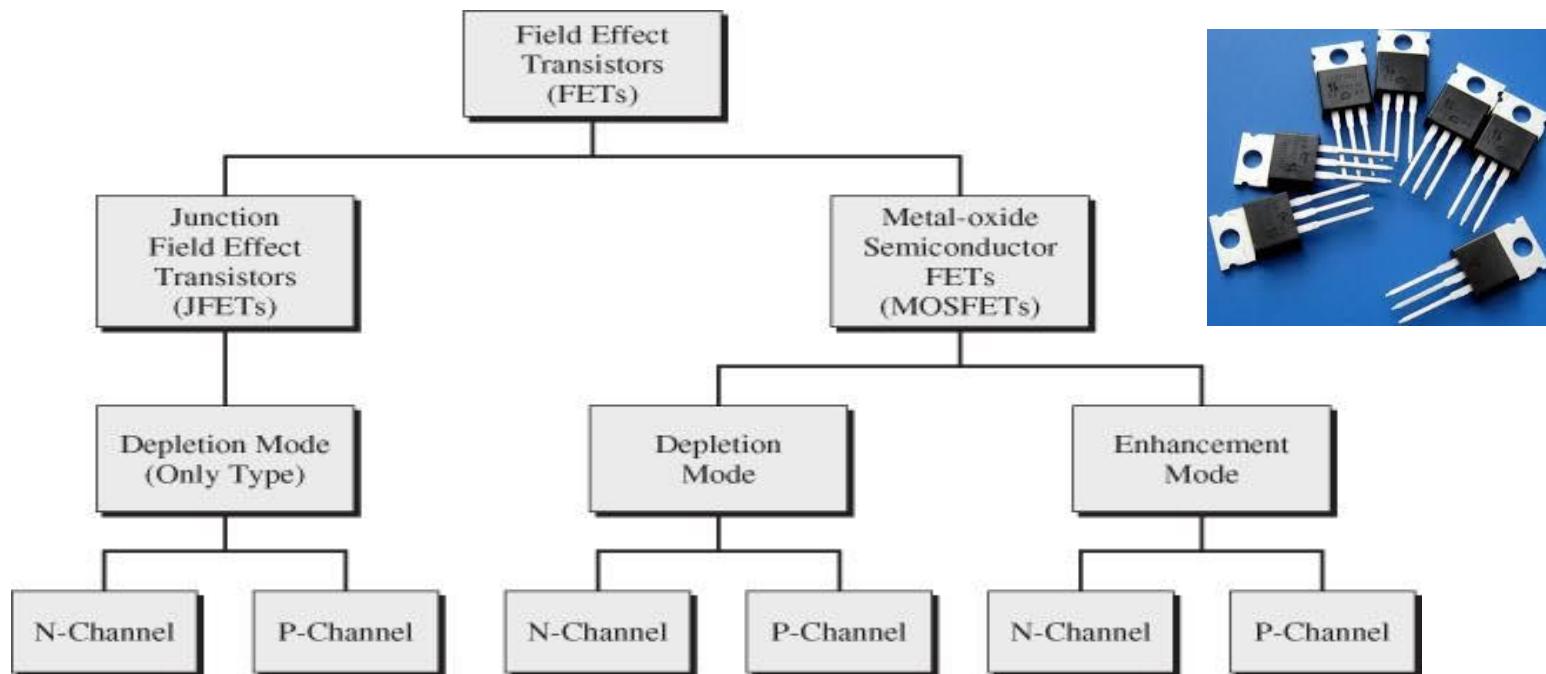- An electronic device which uses an electric field to control the flow of current.
- FETs are devices with three terminals: *source*, *gate*, and *drain*.
- FETs control the flow of current by the application of a voltage to the gate, which in turn alters the conductivity between the drain and source.



MOS Field Effect Transistors (MOSFET)


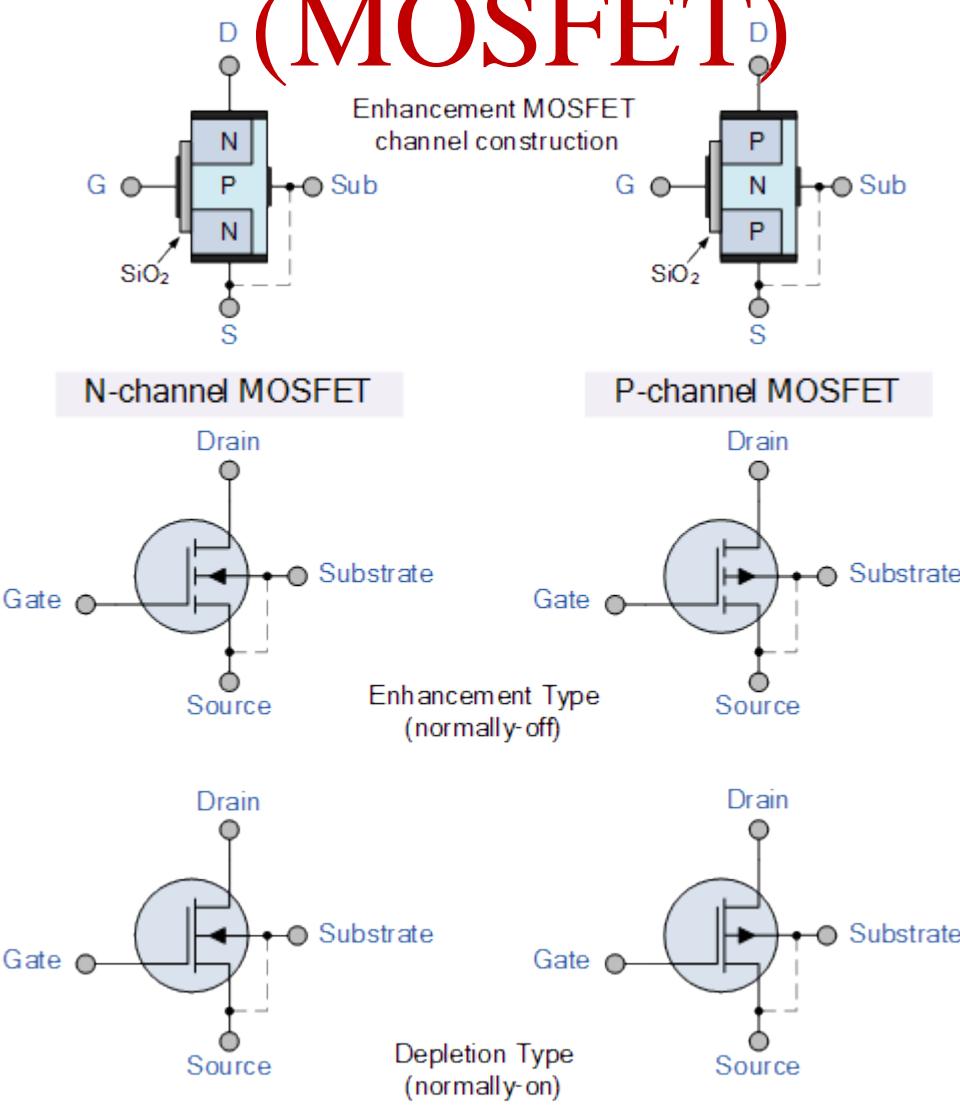


MOSFET



**Sabin Mathew, Founder
Learn Engineering**

MOS Field Effect Transistors (MOSFET)

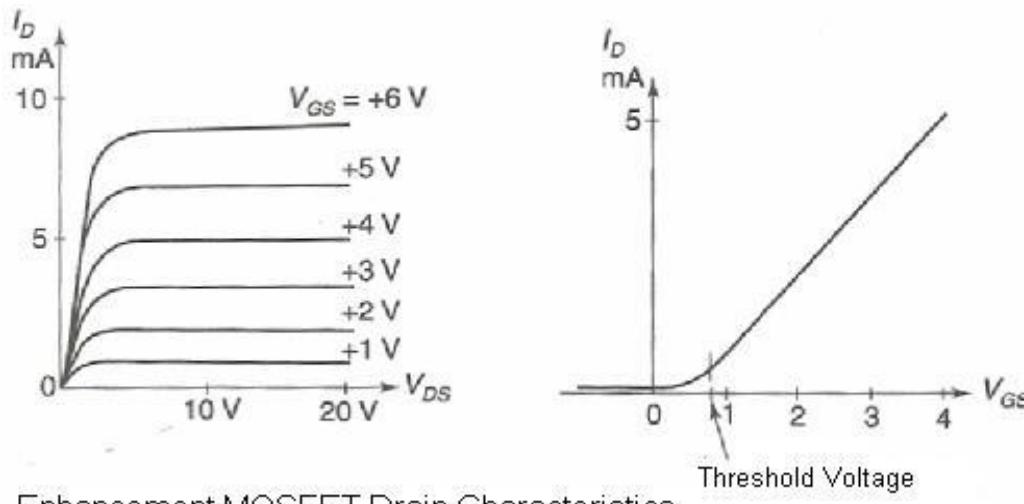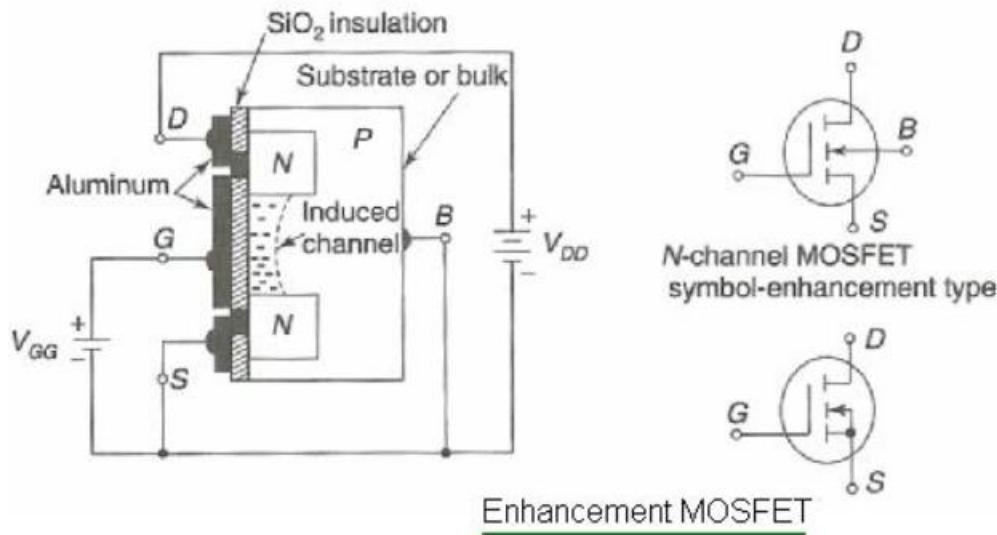

BJT Vs. FET

BJT	FET
High voltage gain	Low voltage gain
Low current gain	High current gain
Low input impedance	Very high input impedance
Low output impedance	High output impedance
Medium Noise Generation	Low Noise generation
Medium switching time	Fast switching time
Robust	Easily damaged
Requires zero input to turn it "OFF"	Some need an input to turn it "OFF"
It is a Current controlled device.	It is a Voltage controlled device.
Cheap	More expensive than BJT.
Easy to bias	Difficult to bias


Checkpoint

Question	A	B	C	D	Answer
In semiconductor transistor to make proper heat dissipation from collector area	Base area is greater than emitter area	collector of transistor is lightly doped	Base area is less than emitter area	emitter of transistor is heavily doped	
The doping concentration is highest in.....region of BJT.	base	emitter	collector	none of these	
The is current gain of CB configuration	α_{DC}	β_{DC}	γ_{DC}	none of these	
What is the collector current for a C-E configuration with a beta of 100 and a base current of 30 μA?	30 μ A	3 μ A	3 mA	30 mA	
Transistor acts as open switch in.....region.	cut-off	active	saturation.	none of these	


Checkpoint

Question	A	B	C	D	Answer
In semiconductor transistor to make proper heat dissipation from collector area	Base area is greater than emitter area	collector of transistor is wider in size	Base area is less than emitter area	emitter of transistor is heavily doped	B
The doping concentration is highest in.....region of BJT.	base	emitter	collector	none of these	B
The is current gain of CB configuration	α_{DC}	β_{DC}	γ_{DC}	none of these	A
Transistor acts as open switch in.....region.	cut-off	active	saturation .	none of these	A

MOSFET as a Switch

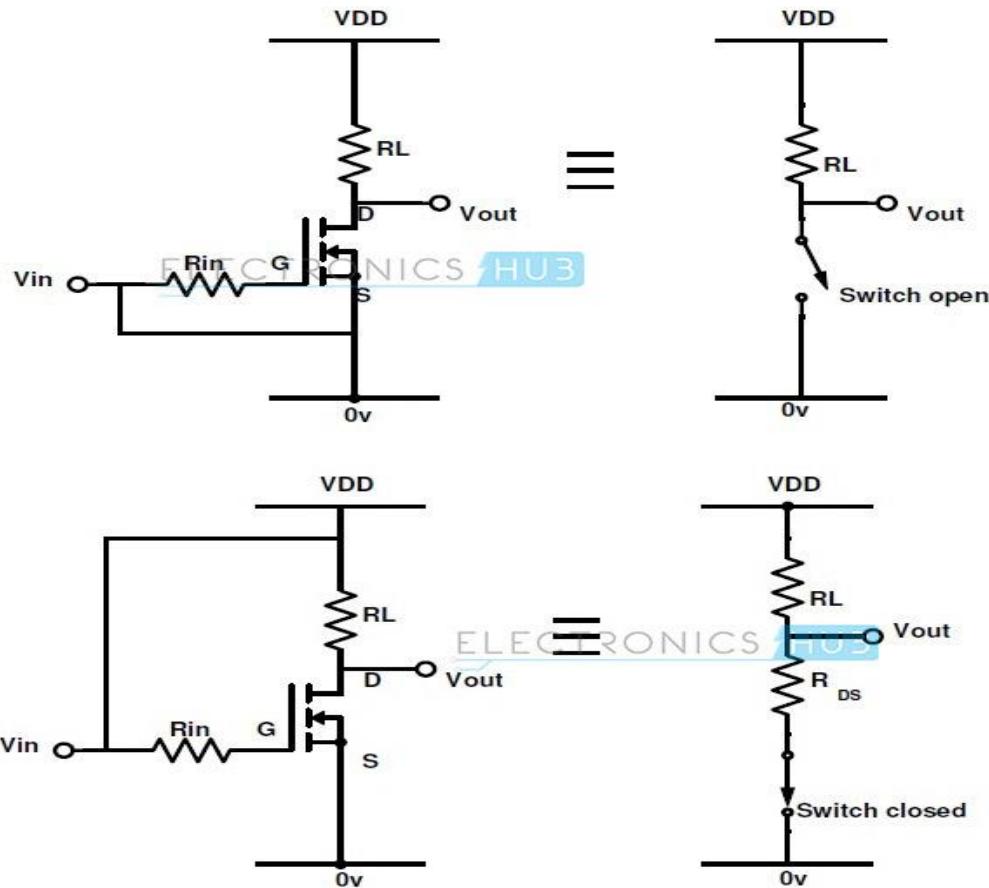


Load Switching

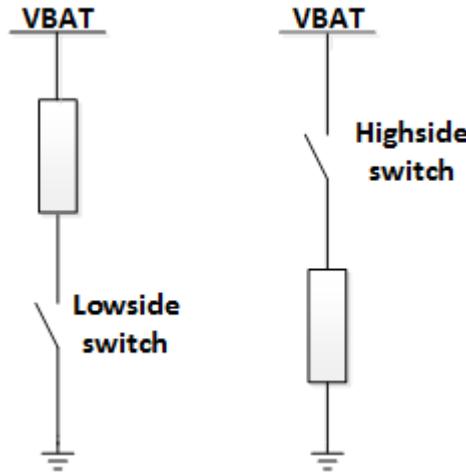


- A high side driver is one in which the switching element is between Vcc and the load.
- A low side driver is one in which the switching element is between the load and common.
- A self-contained load such as a DC motor, solenoid/relay, light or LED string, can usually be driven by either method.

Load Switching

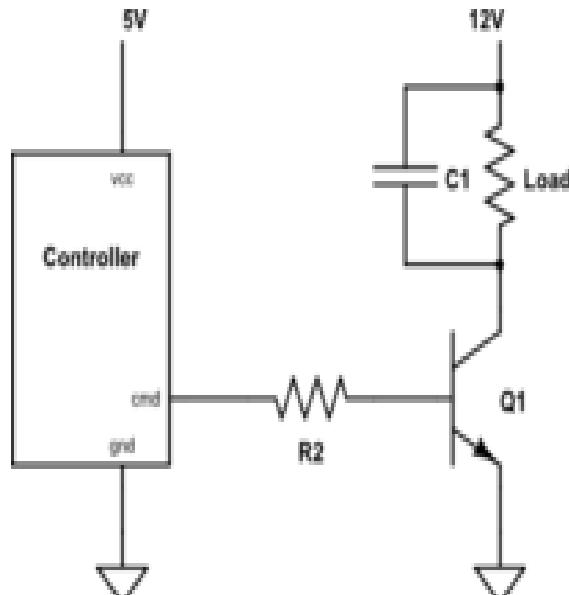


Low side Switch


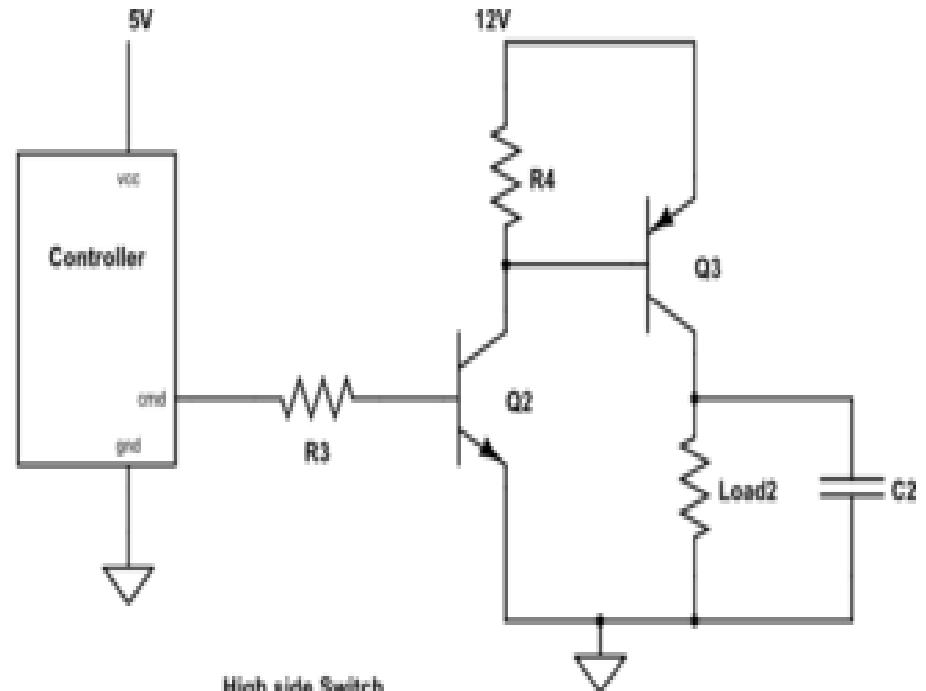


High side Switch


Low-Side Switching

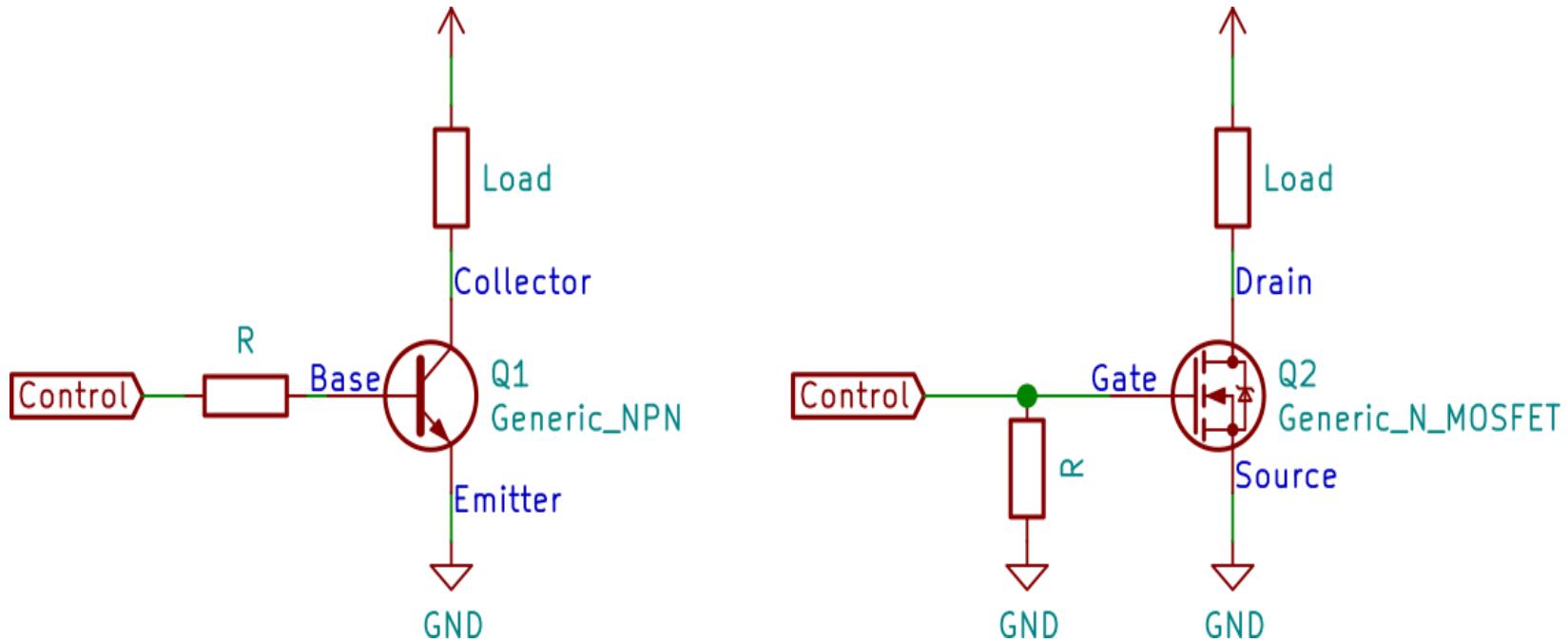


High-Side Switching

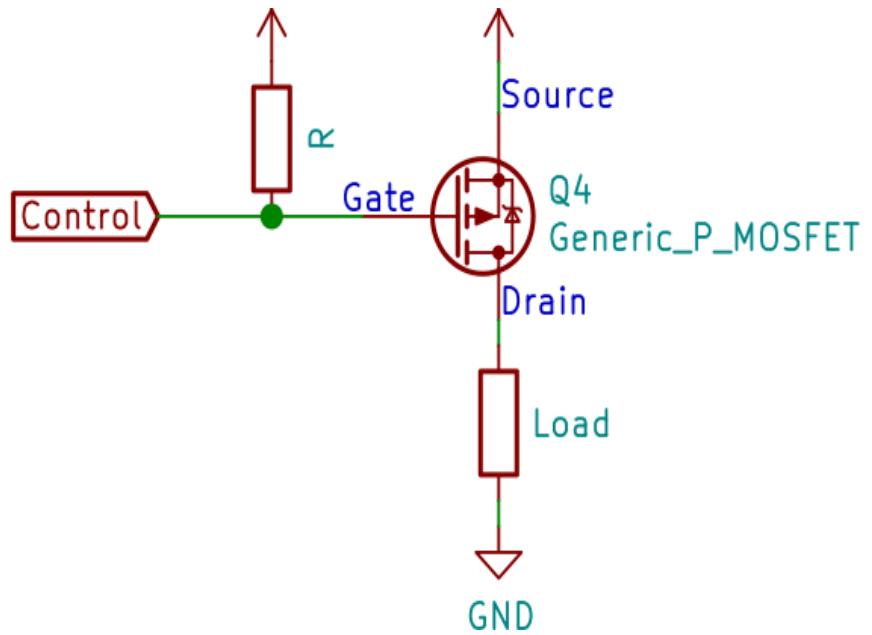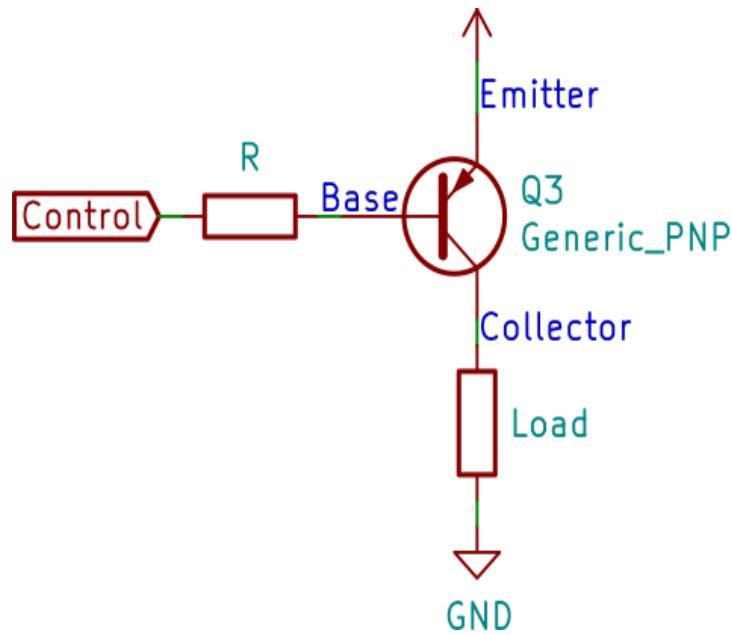

Load Switching

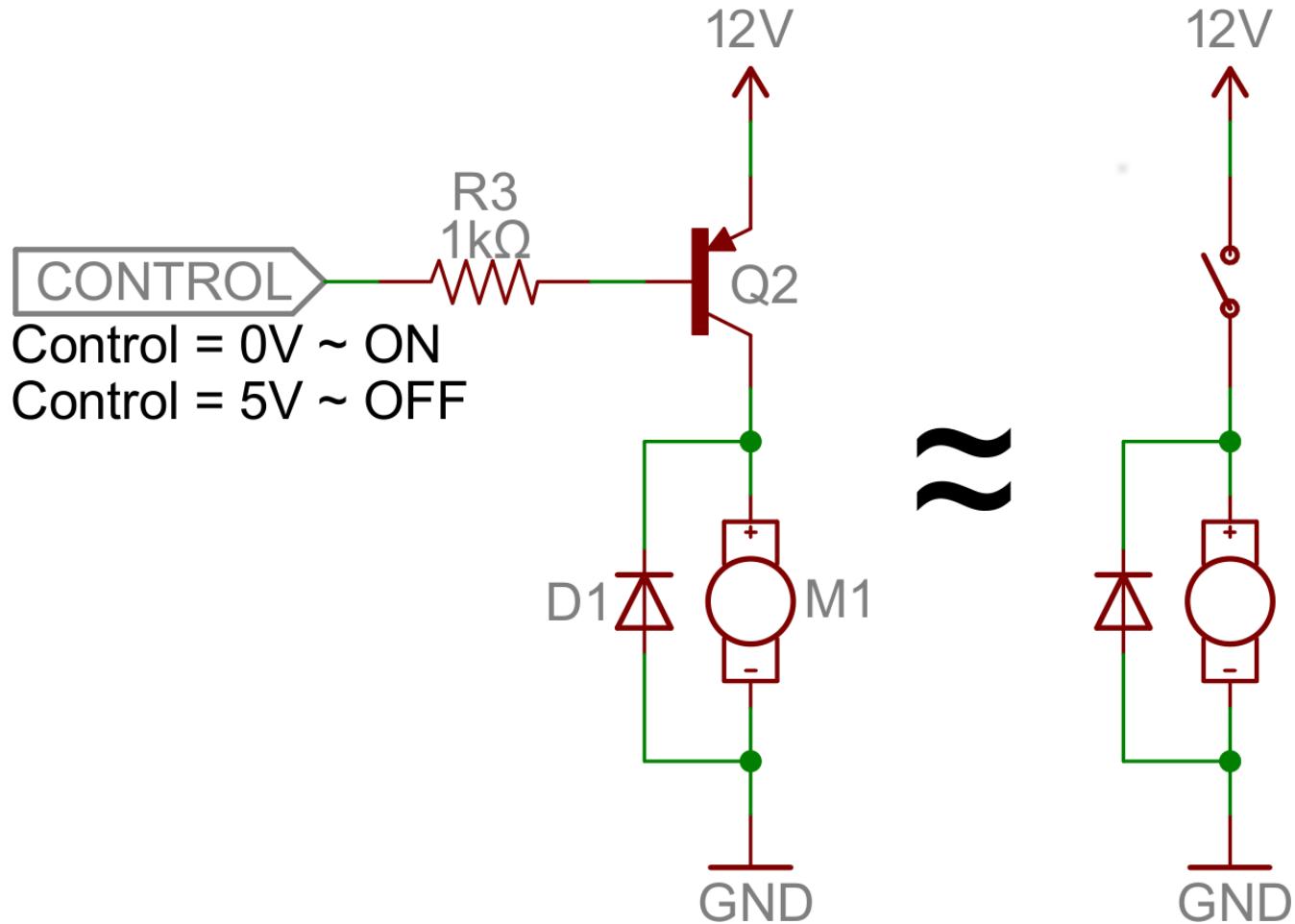


H Bridge

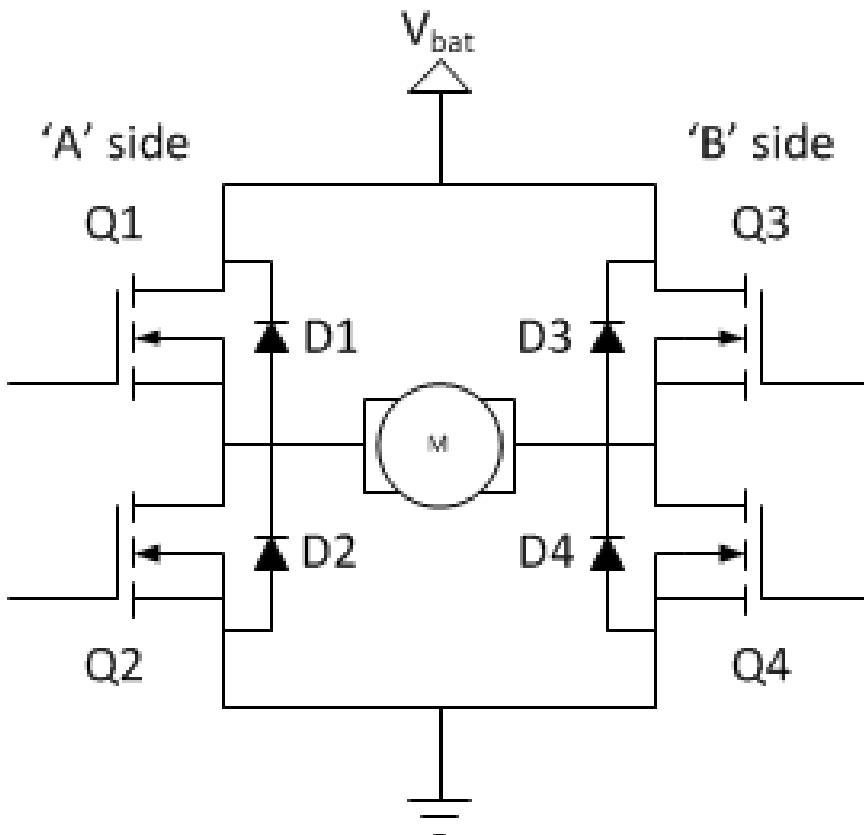


- Contains four switching element, with the load at the center
- The switching elements (Q1..Q4) are usually bi-polar or FET transistors
- Integrated solutions also exist

H Bridge

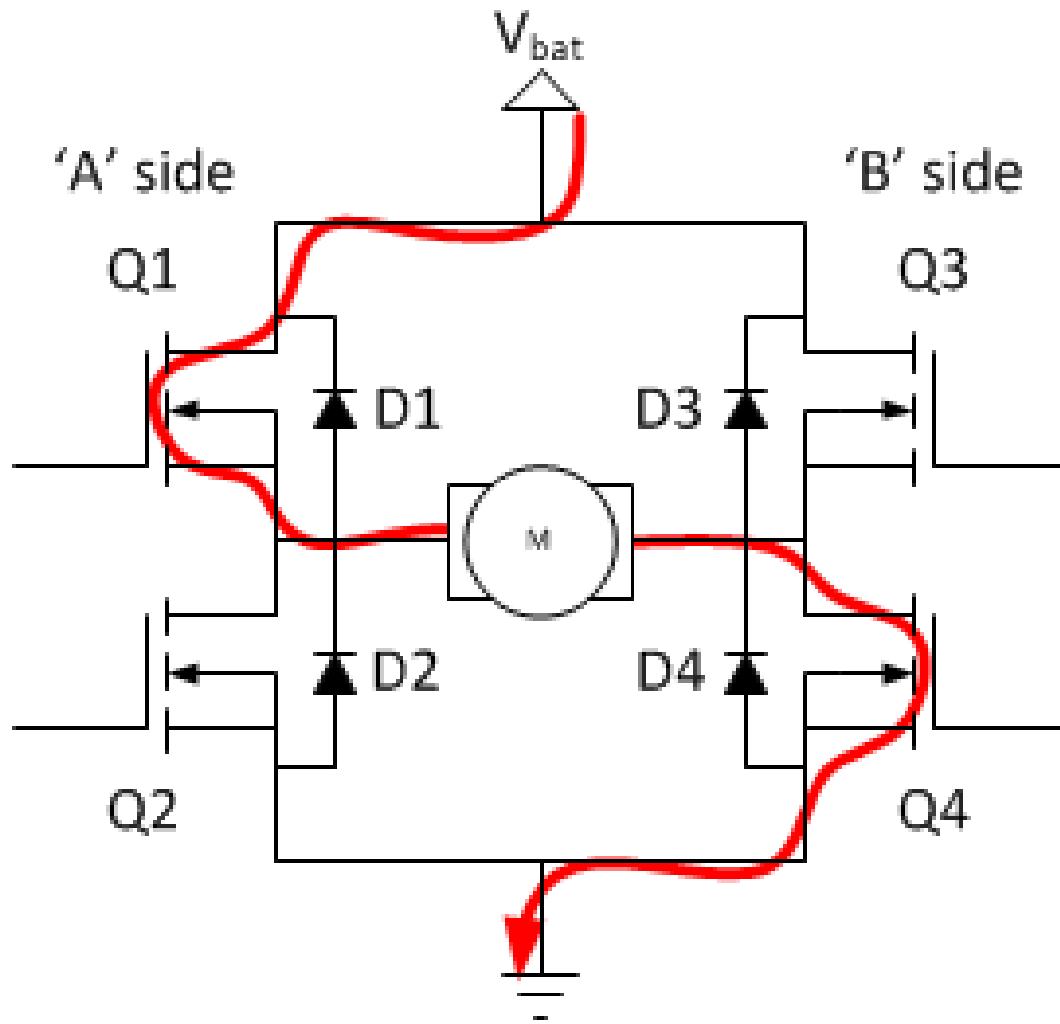

Q1 and Q4 are turned on
the motor starts moving in forward direction


H Bridge

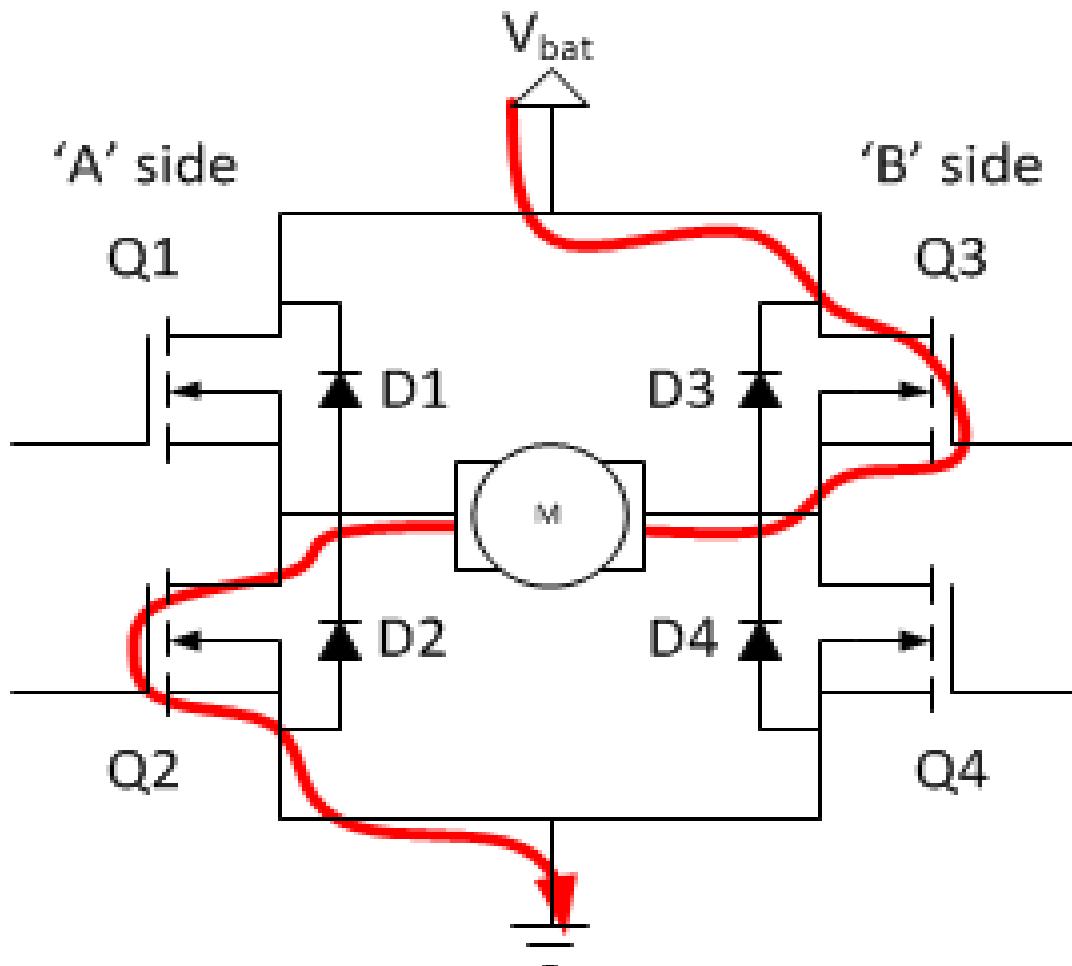

If Q2 and Q3 are turned on,
the motor gets energized in the reverse direction


H Bridge

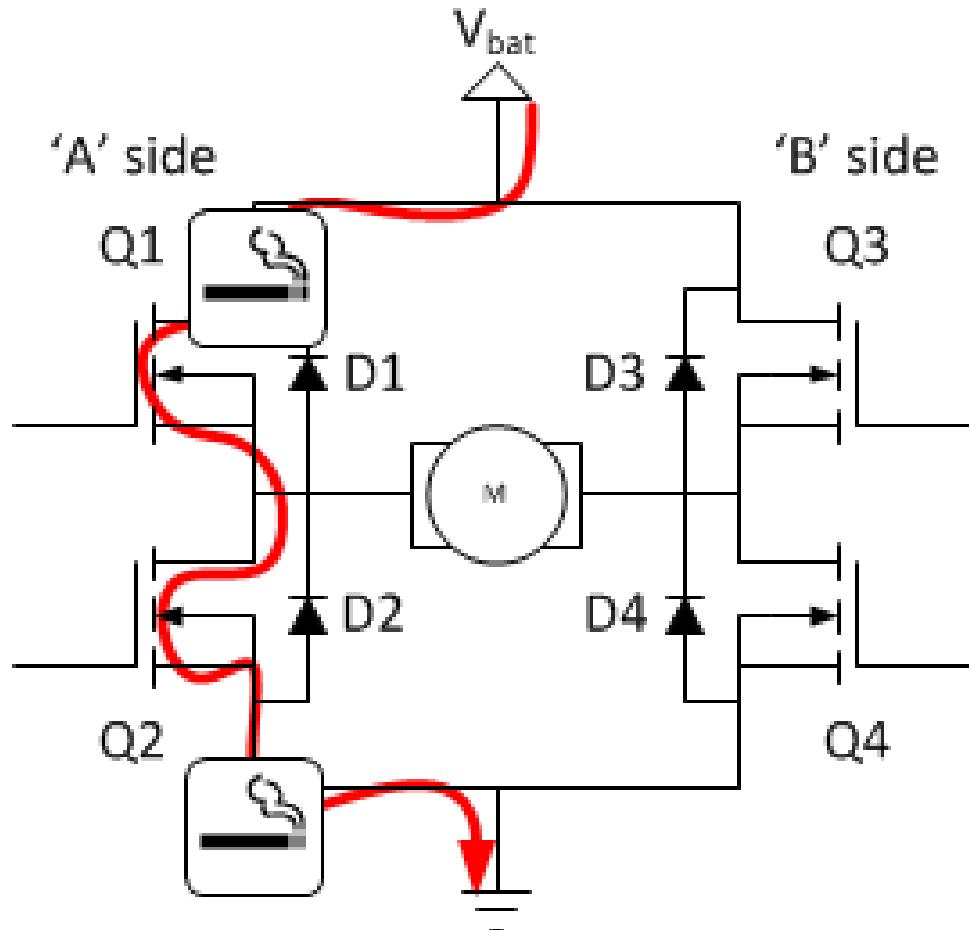In a bridge, you should **never** ever close both Q1 and Q2 (or Q3 and Q4) at the same time.




H - Bridge Demo

H Bridge IC

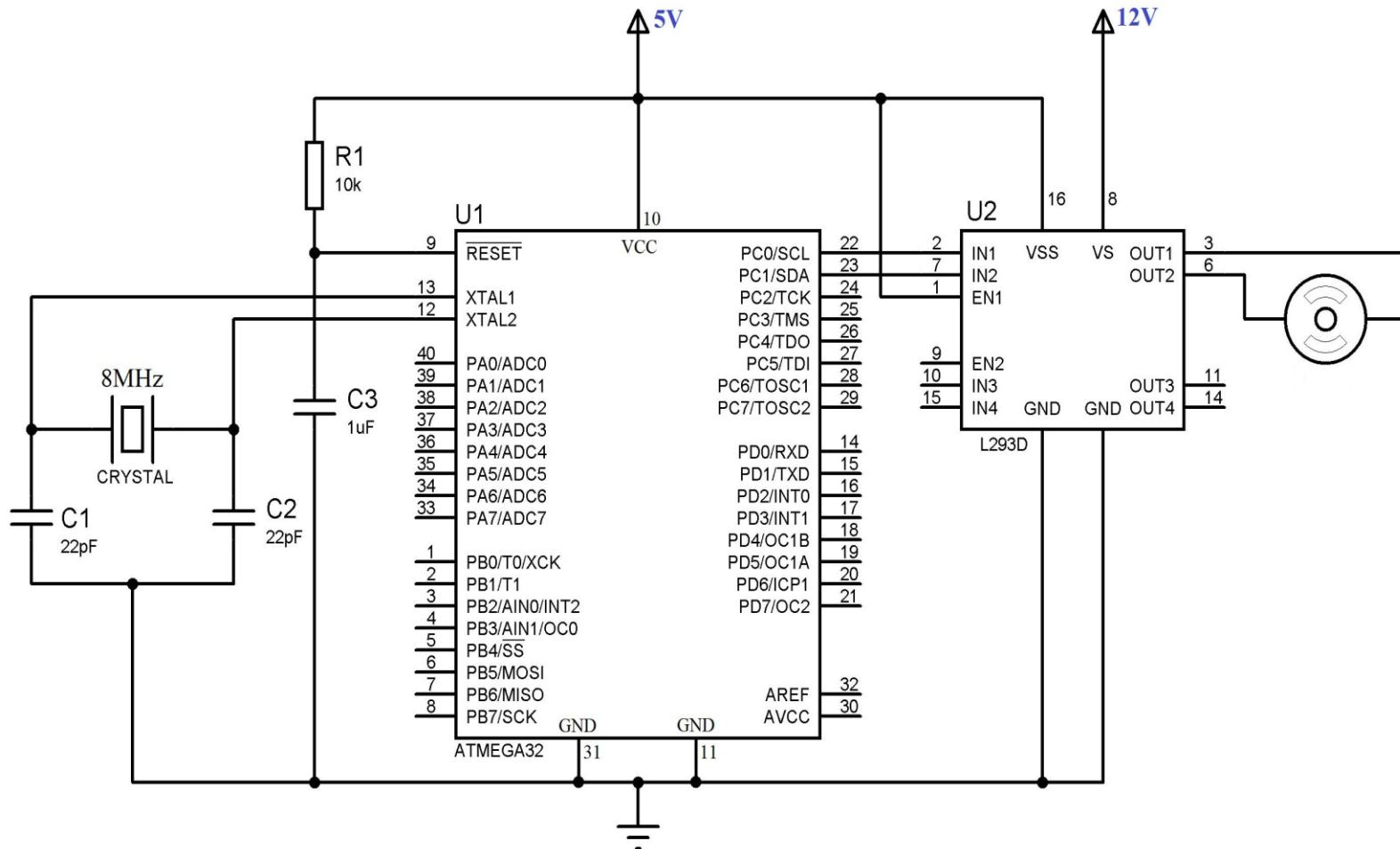

H Bridge IC Module

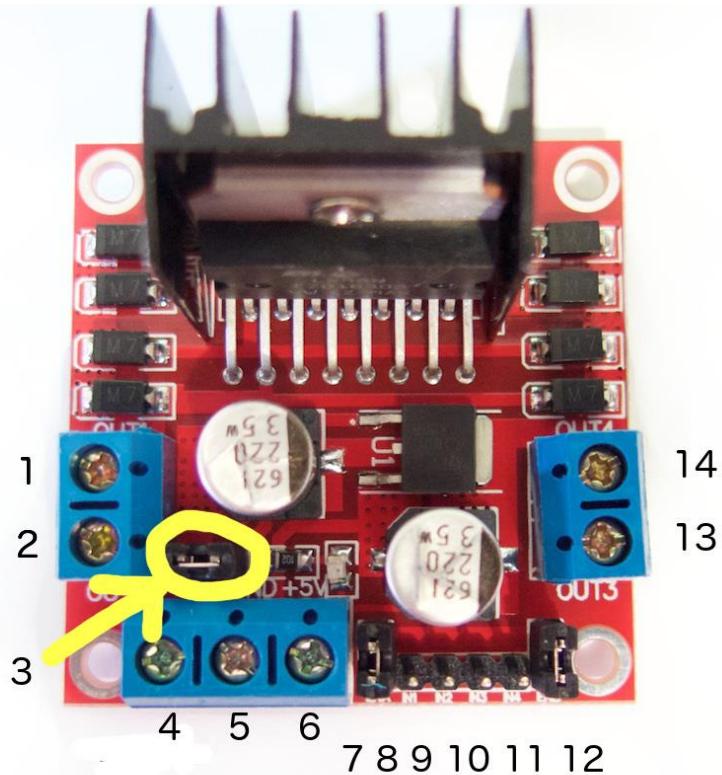


L298N Dual H-Bridge Motor Driver Module

- 1.DC motor 1 "+" or stepper motor A+
- 2.DC motor 1 "-" or stepper motor A-
- 3.12V jumper - remove this if using a supply voltage greater than 12V DC. This enables power to the onboard 5V regulator
- 4.Connect your motor supply voltage here, maximum of 35V DC.
- 5.GND
- 6.5V output if 12V jumper in place, ideal for powering your Arduino (etc)
- 7.DC motor 1 enable jumper. Leave this in place when using a stepper motor. Connect to PWM output for DC motor speed control.
- 8.IN1
- 9.IN2
- 10.IN3
- 11.IN4
- 12.DC motor 2 enable jumper. Leave this in place when using a stepper motor. Connect to PWM output for DC motor speed control.
- 13.DC motor 2 "+" or stepper motor B+
- 14.DC motor 2 "-" or stepper motor B-

Amplifier Opamp Circuits

Amplifier

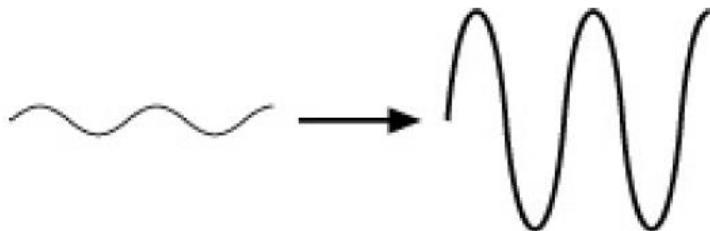


$$\text{Gain} = V_{\text{OUT}} / V_{\text{IN}}$$


- An amplifier is a circuit that increases (or decreases) a given input voltage to produce an output voltage.
- If you had a sensor that produced a maximum output that was 5 mVpp, and this was to be interfaced to a sampling system that required an input signal of 5 Vpp.
- You would use an amplifier between the sensor and the sampling system to increase the sensor's output accordingly

Opamp Circuits


Inverting Op-amp

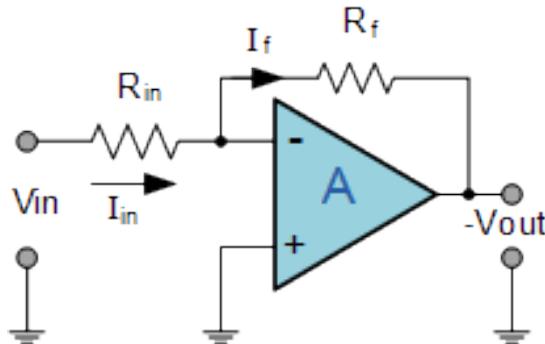

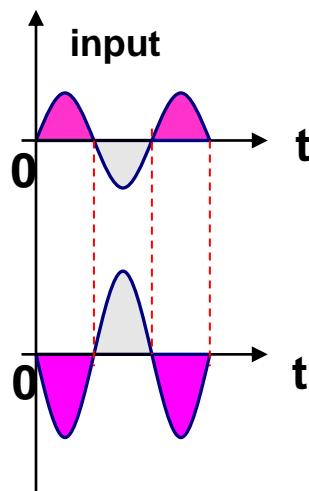
$$A = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$$




Non-inverting Op-amp

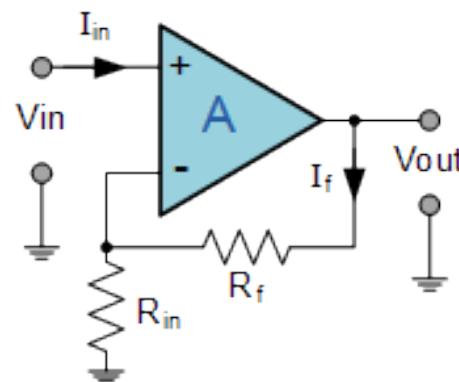
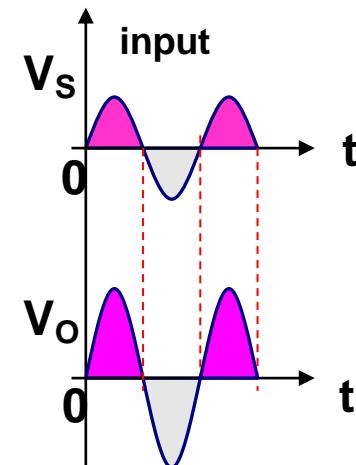
$$A = \frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_{in}}$$




Opamp Circuits

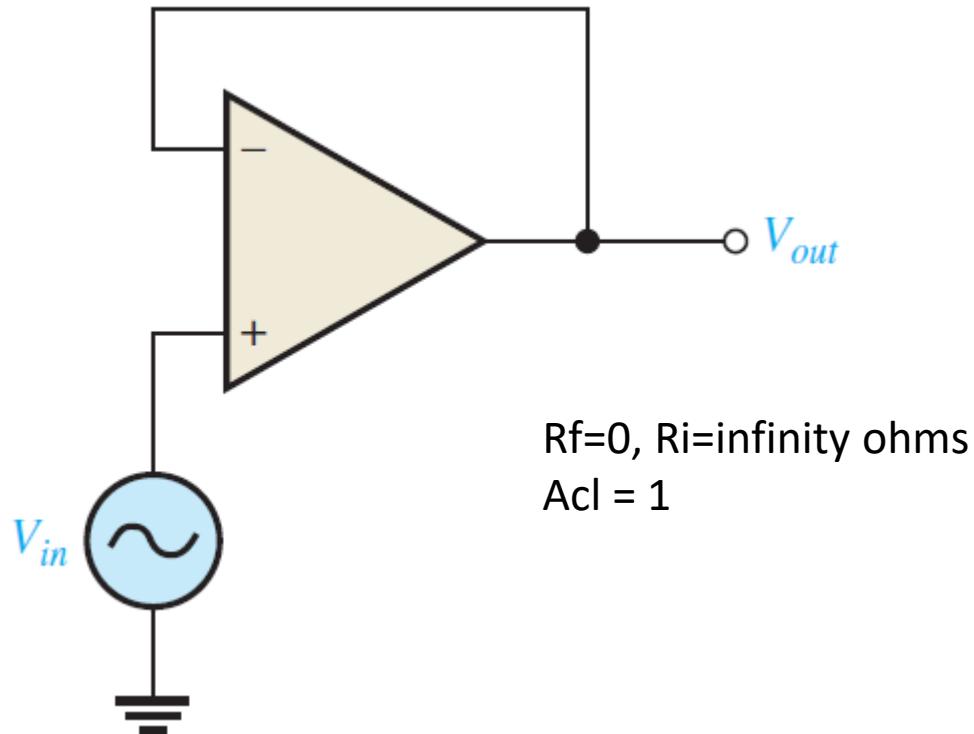


Opamp Circuits

Differential Op-amp

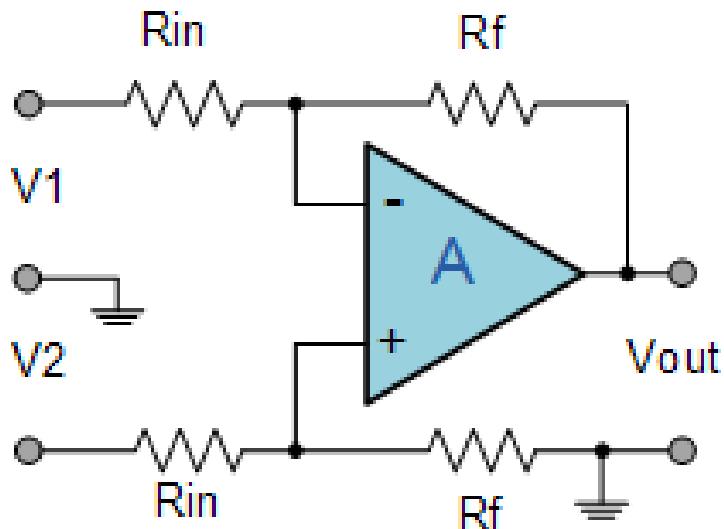


$$V_{out} = \frac{R_f}{R_{in}} (V_2 - V_1)$$

Summing Op-amp

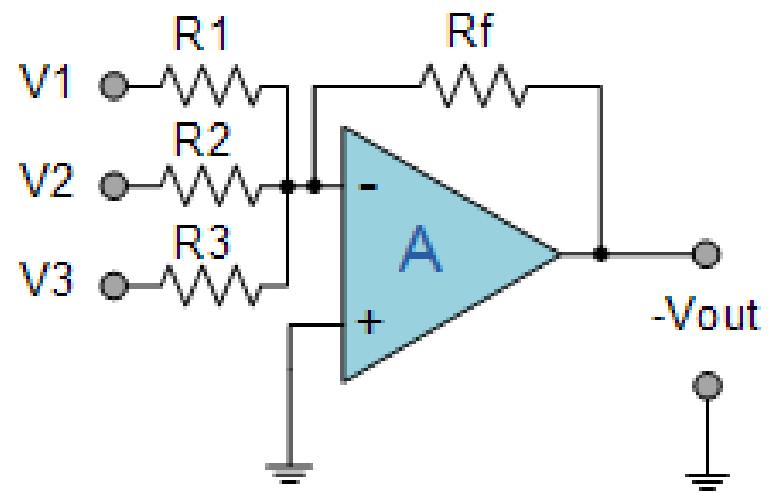


$$V_{out} = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

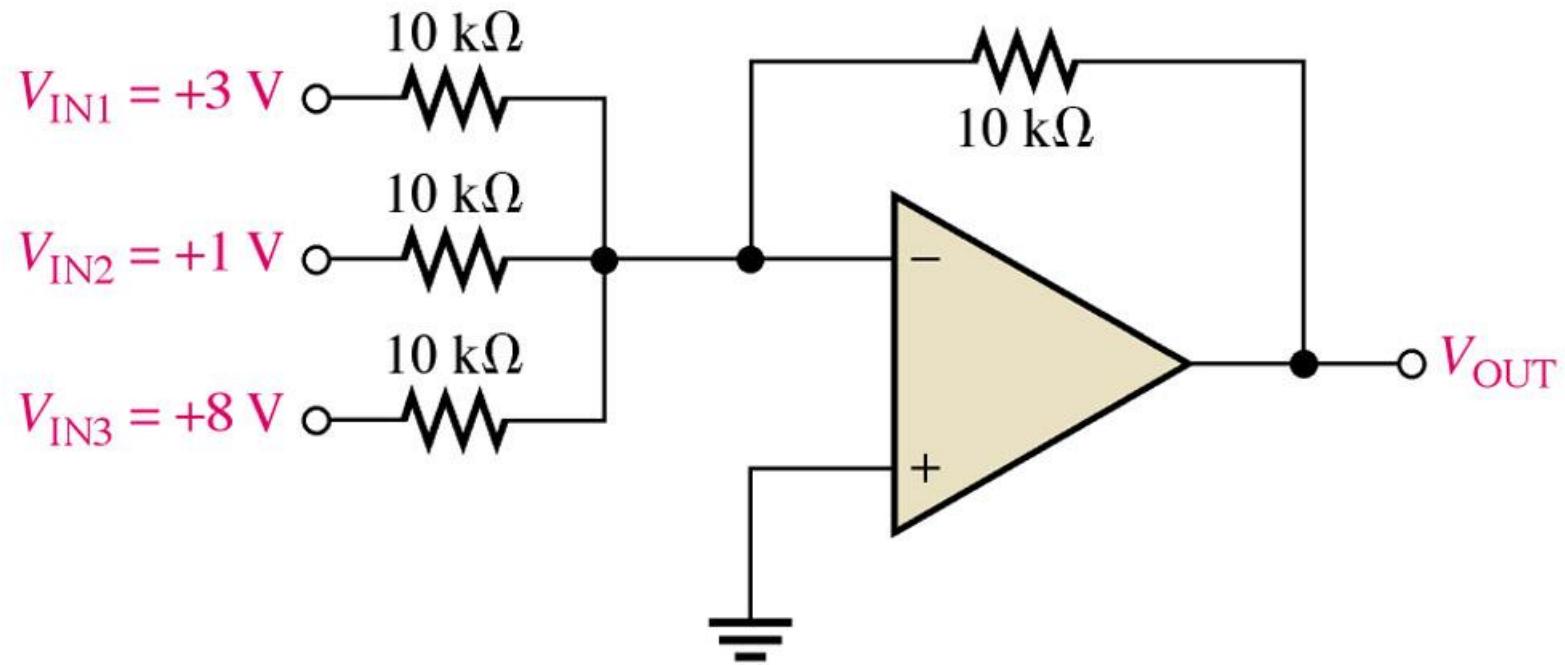Determine the output voltage in given figure




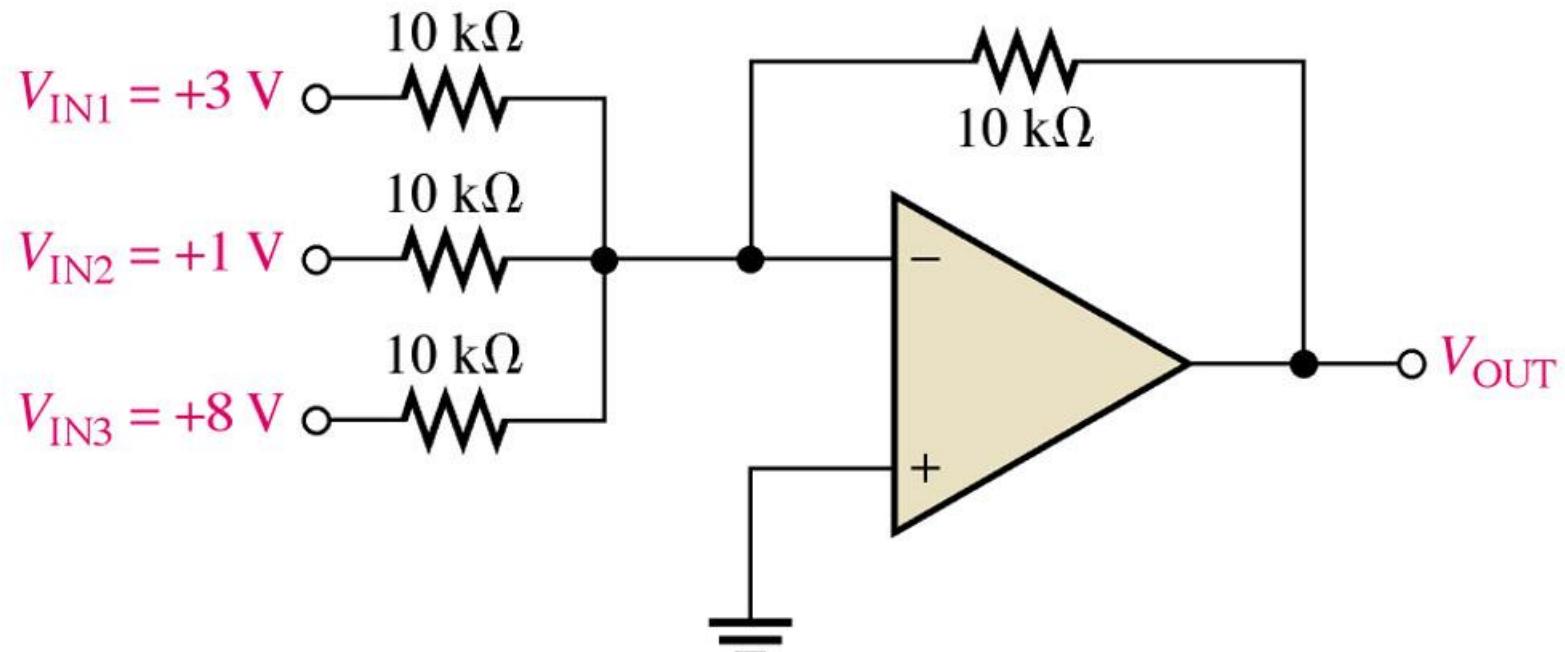Determine the output voltage in given figure




Ans = - 12V

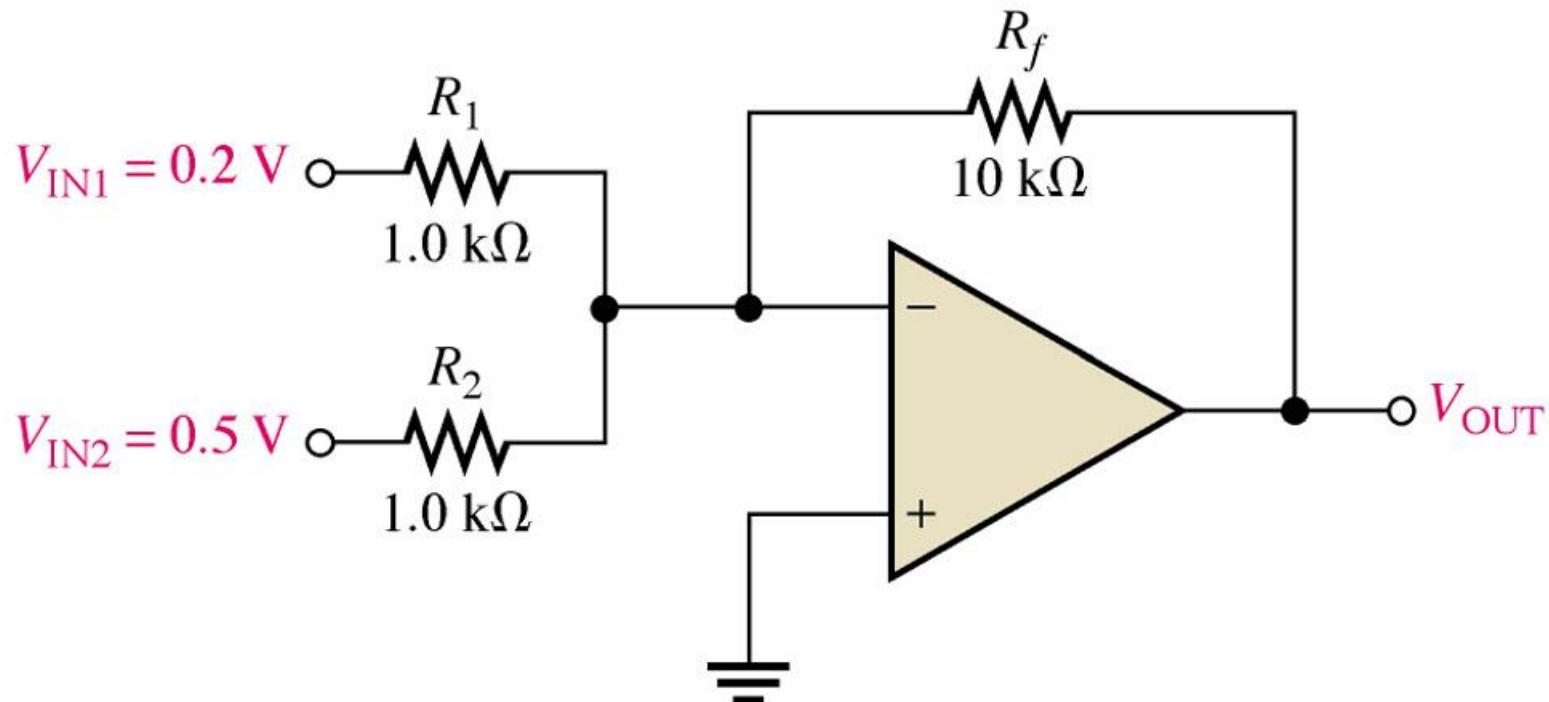
Determine the output voltage in given figure



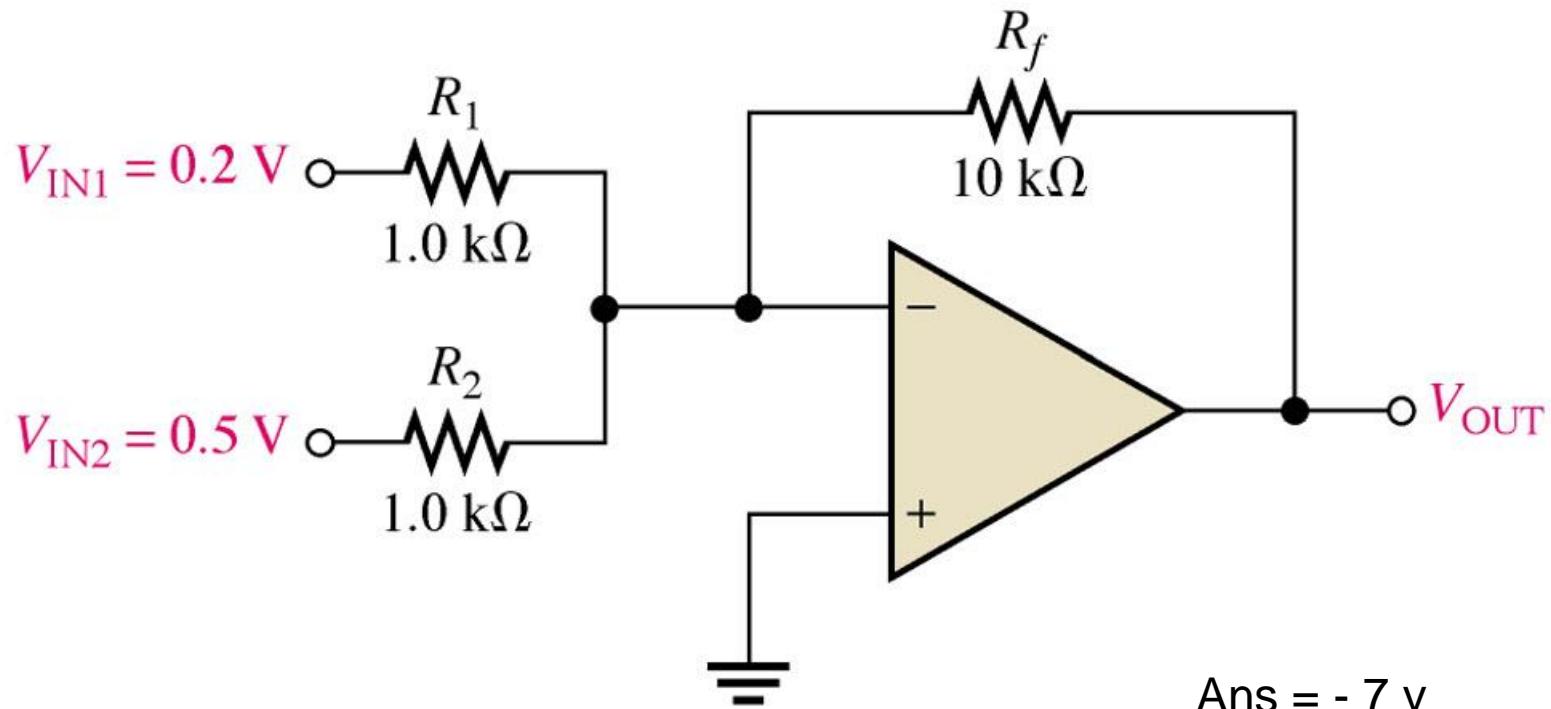
Determine the output voltage in given figure



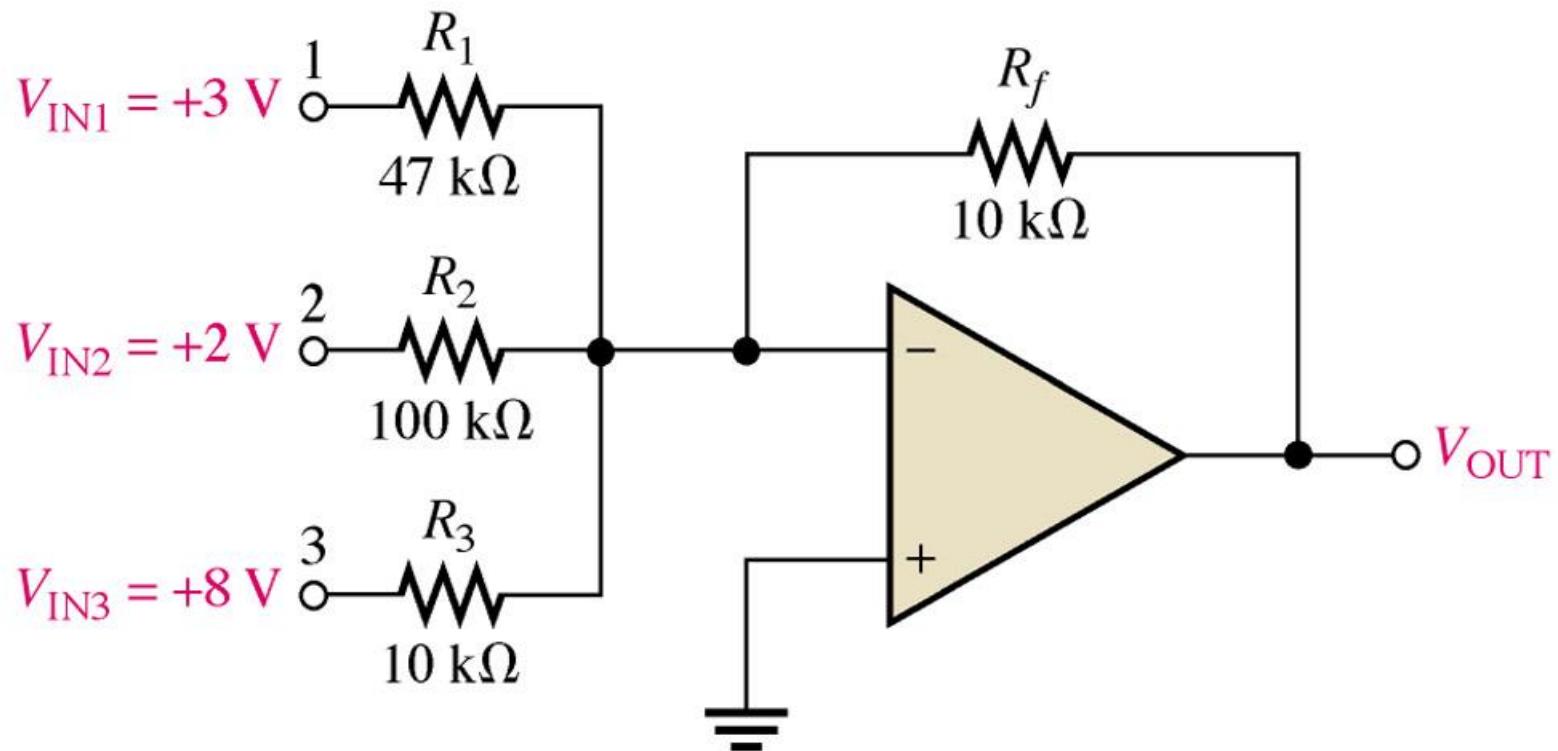Determine the output voltage in given figure




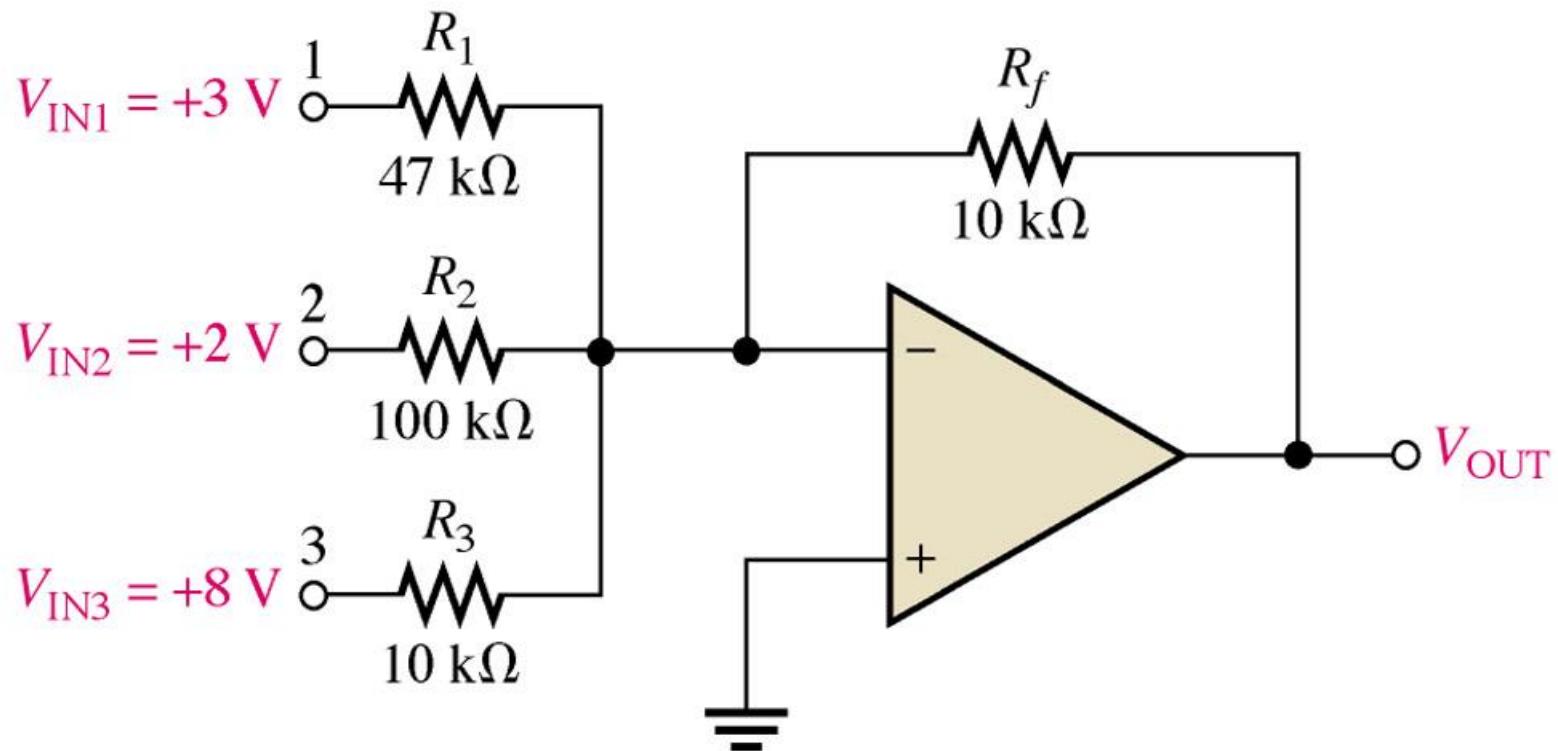Determine the output voltage in given figure




$$\text{Ans} = -8.84\text{ V}$$

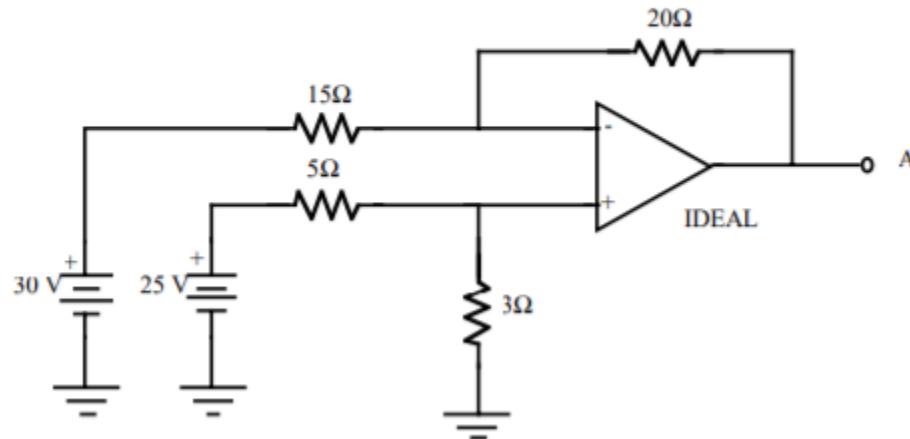For the difference amplifier circuit shown, determine the output voltage at terminal A.



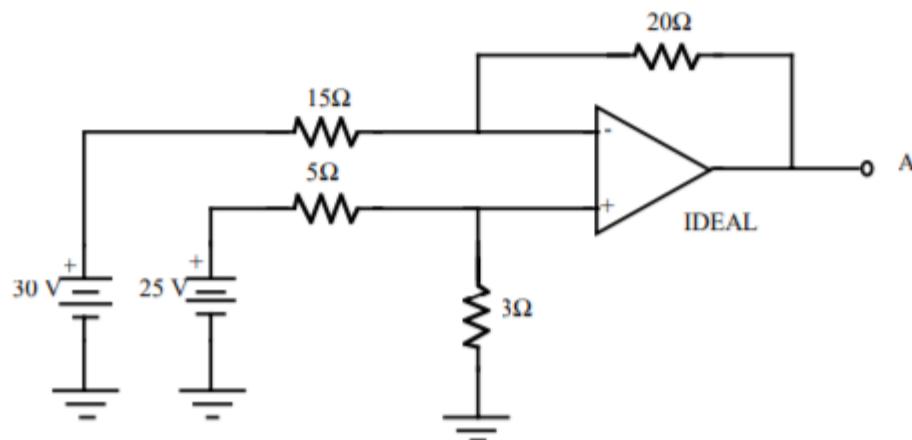For the difference amplifier circuit shown, determine the output voltage at terminal A.



Solution:

By voltage division,

$$v_{in+} = 25V \left(\frac{3\Omega}{5\Omega + 3\Omega} \right) = 9.375V$$

By the virtual short circuit between the input terminals, $v_{in-} = 9.375 V$

Using **Ohm's** law, the current through the 15Ω resistor is


$$I_{15} = \left(\frac{30V - 9.375V}{15\Omega} \right) = 1.375V$$

The input impedance is infinite; therefore, $I_{in-}=0$ and $I_{15}=I_{20}$.

Use Kirchoff's voltage law to find the output voltage at A.

$$v_A = v_{in-} - 20I_{20} = 9.375 V - (20\Omega)(1.375 A) = -18.125 V$$





Instrumentation Amplifier

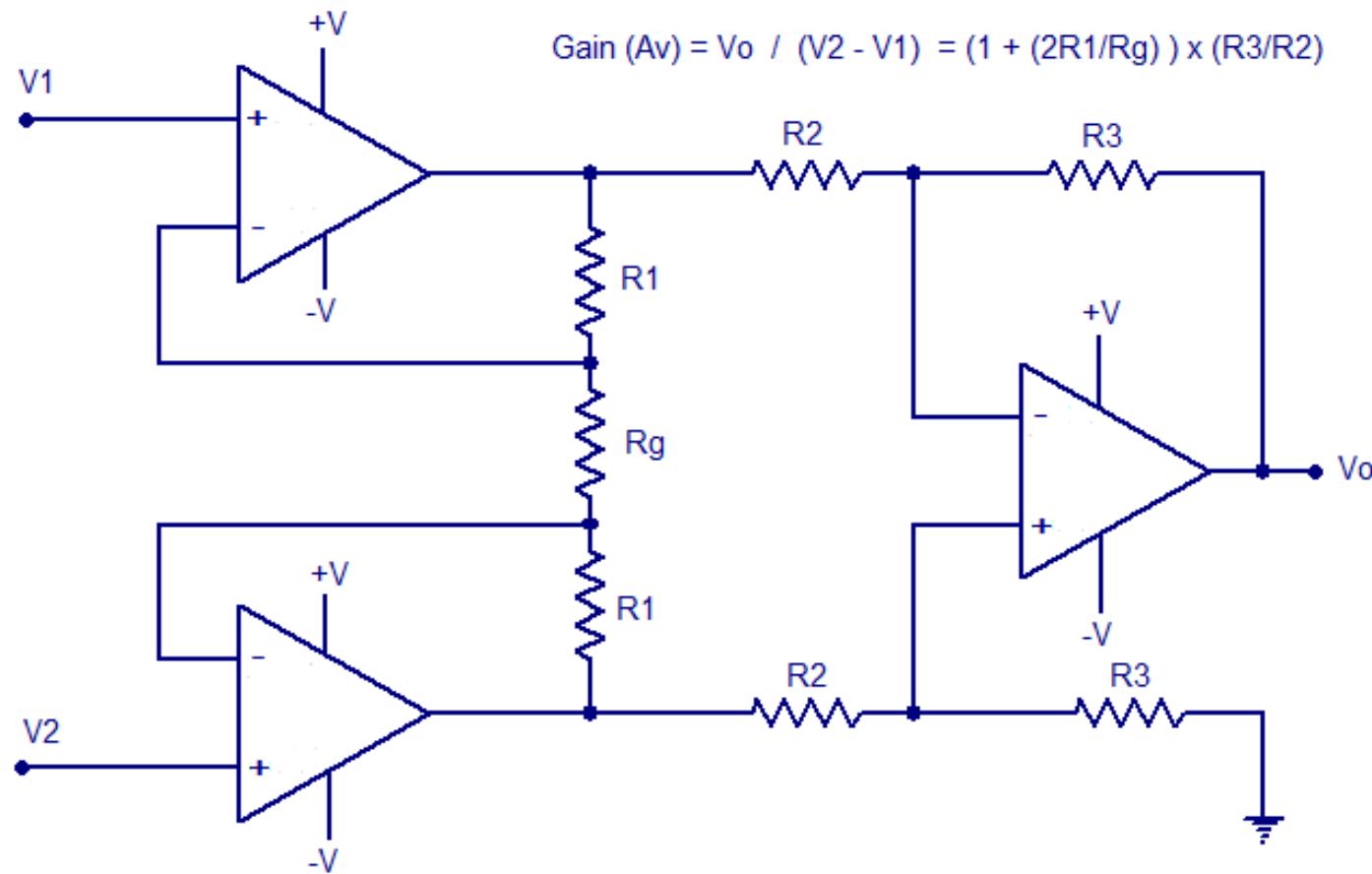

Opamp Demo

Filters

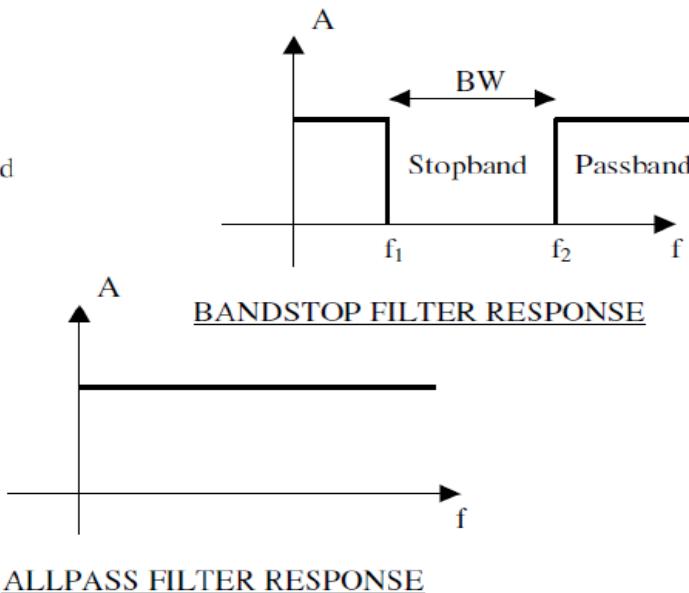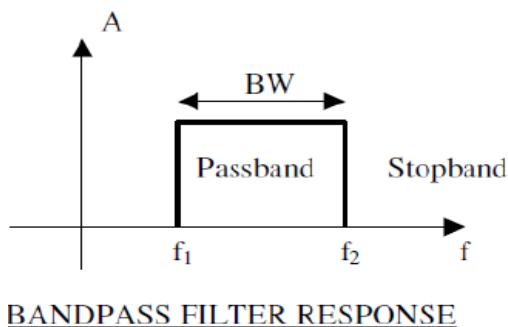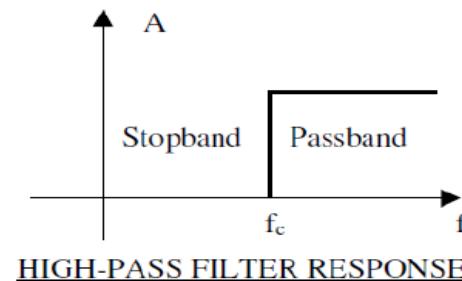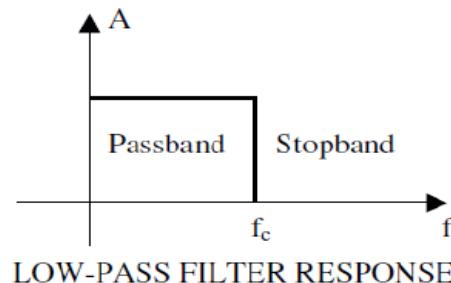
- To filter / cancel out unwanted characteristics of a signal




Filters

- Realistic Filters


lowpass

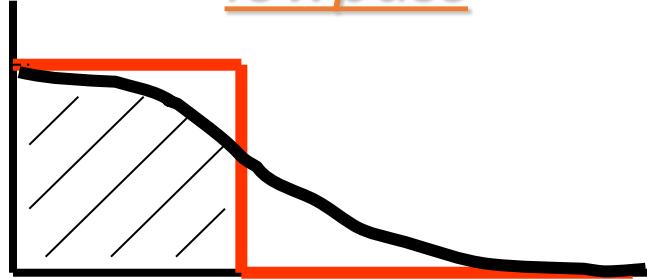


highpass

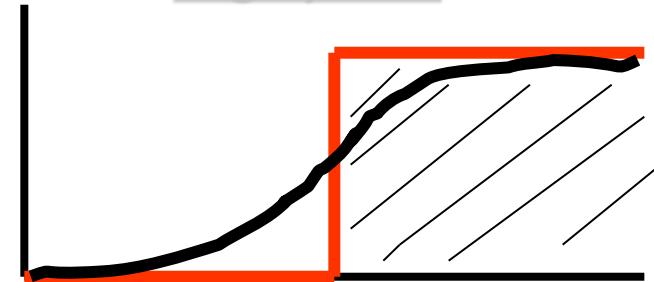

bandpass

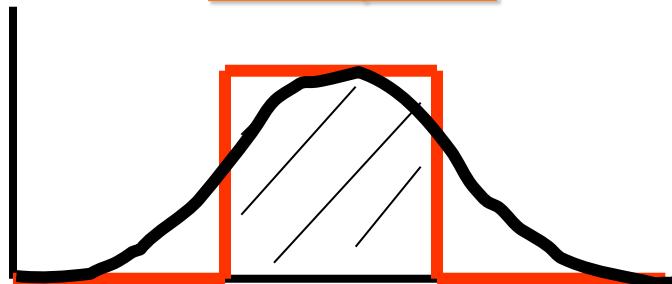

bandstop

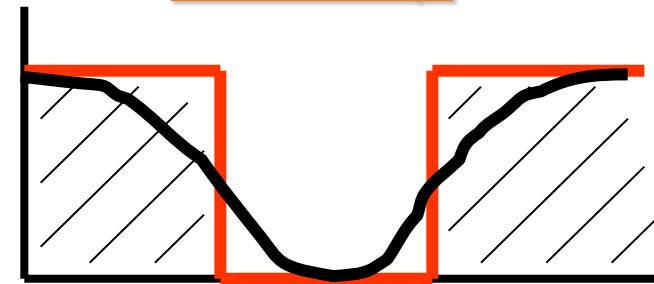


Filters

- Filters may be classified as either digital or analog.
- Digital filters are implemented using a digital computer or special purpose digital hardware.
- Analog filters may be classified as either passive or active and are usually implemented with R, L, and C components and operational amplifiers.

Filters

- An active filter is one that, along with R, L, and C components, also contains an energy source, such as that derived from an operational amplifier.
- A passive filter is one that contains only R, L, and C components.
 - It is not necessary that all three be present.
 - L is often omitted (on purpose) from passive filter design because of the size and cost of inductors – and they also carry along an R that must be included in the design.



Filters

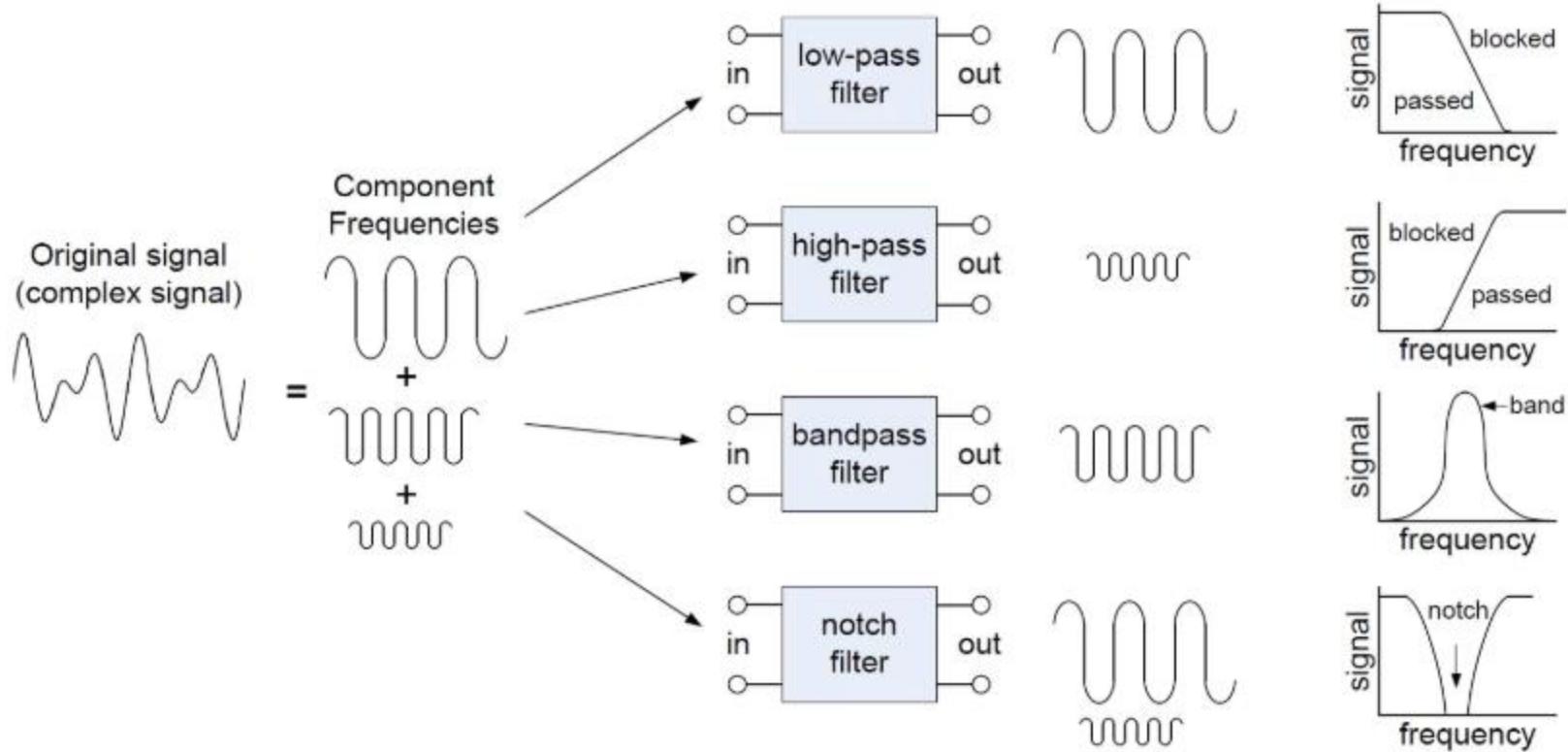

Filters

Low Pass Filter


Consider the circuit below.

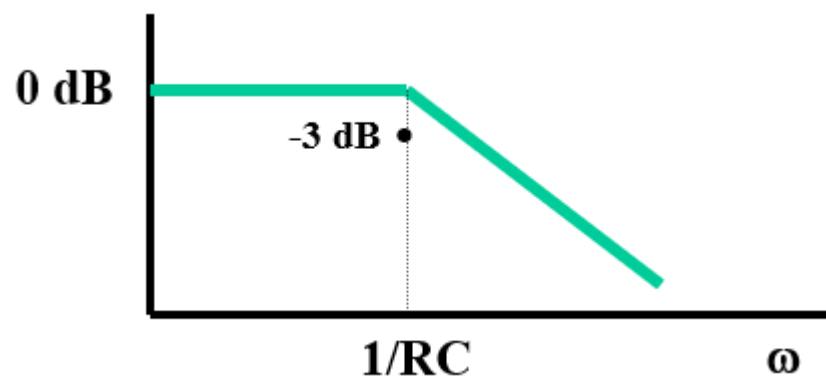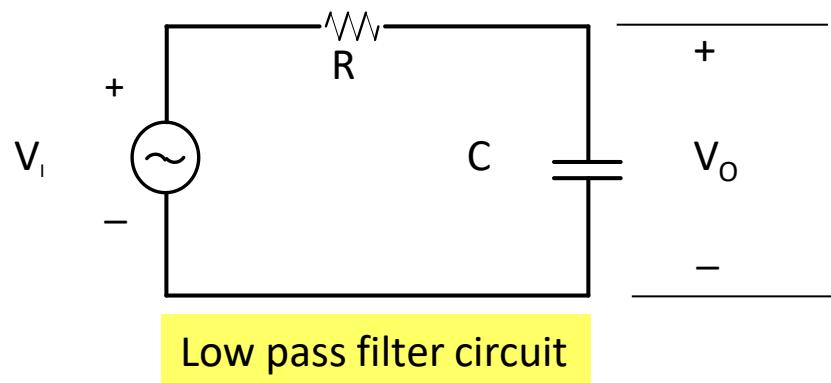


Filters

High Pass Filter

Consider the circuit below.

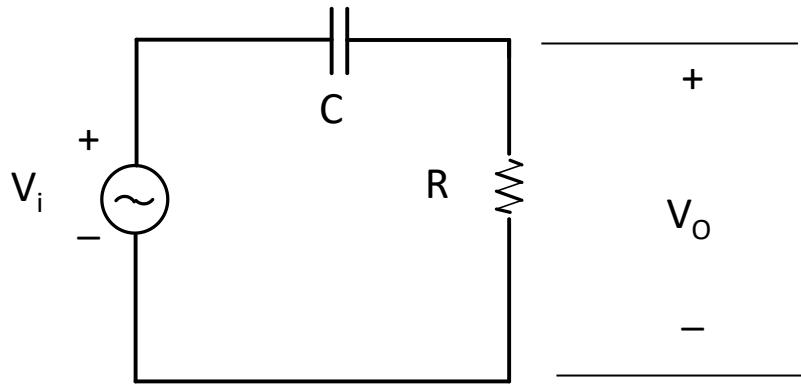



High Pass Filter

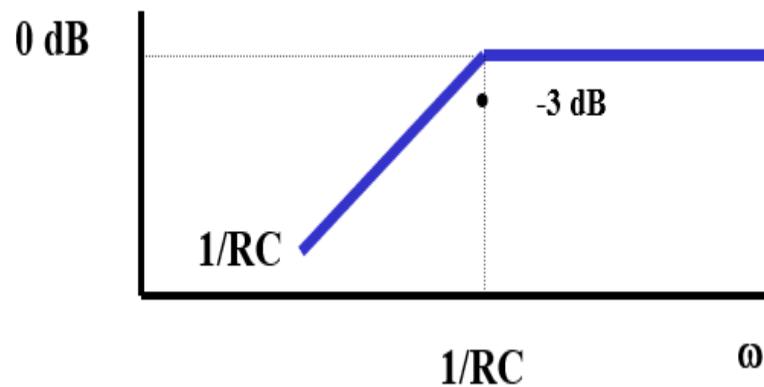

Filters

Bandpass Pass Filter

Consider the circuit shown below:

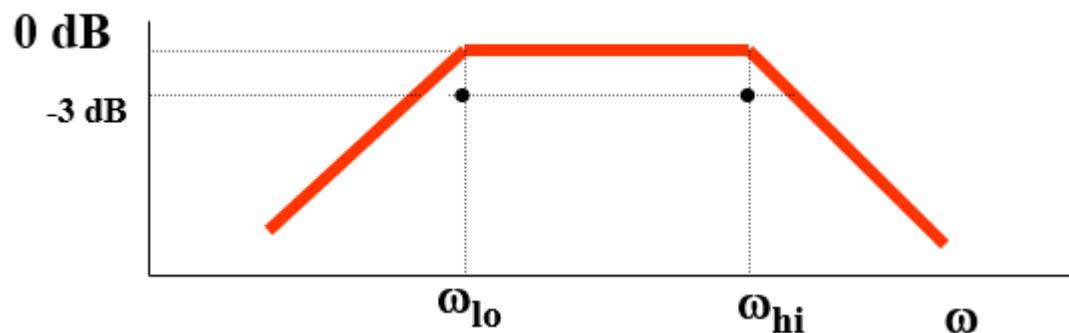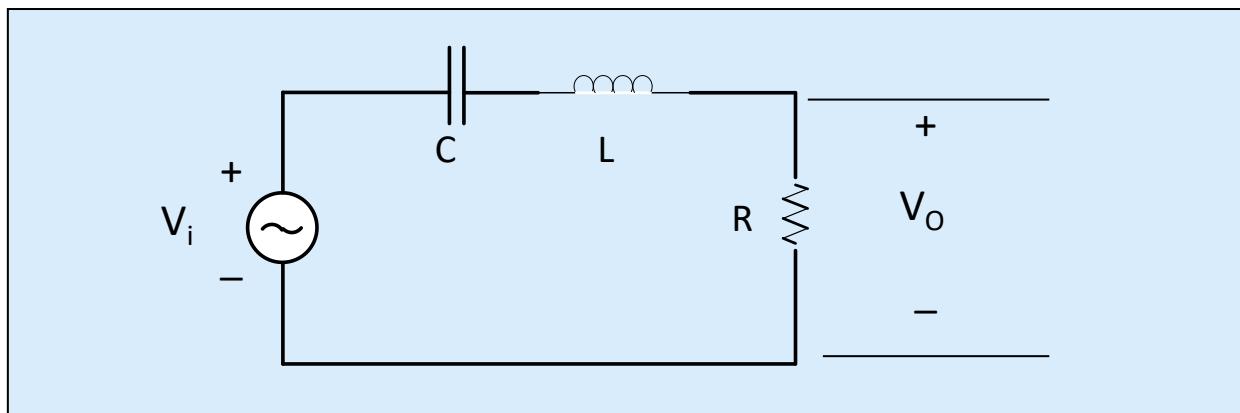



$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Filters

RLC Band stop Filter

Consider the circuit below:

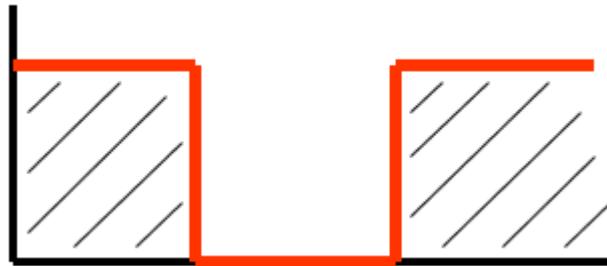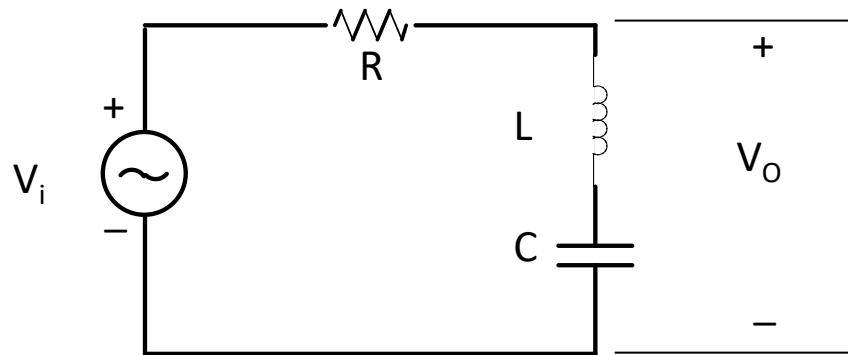

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$


$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

Filters Demo

Electronic
Filter

Input Output Devices

6-Box Model

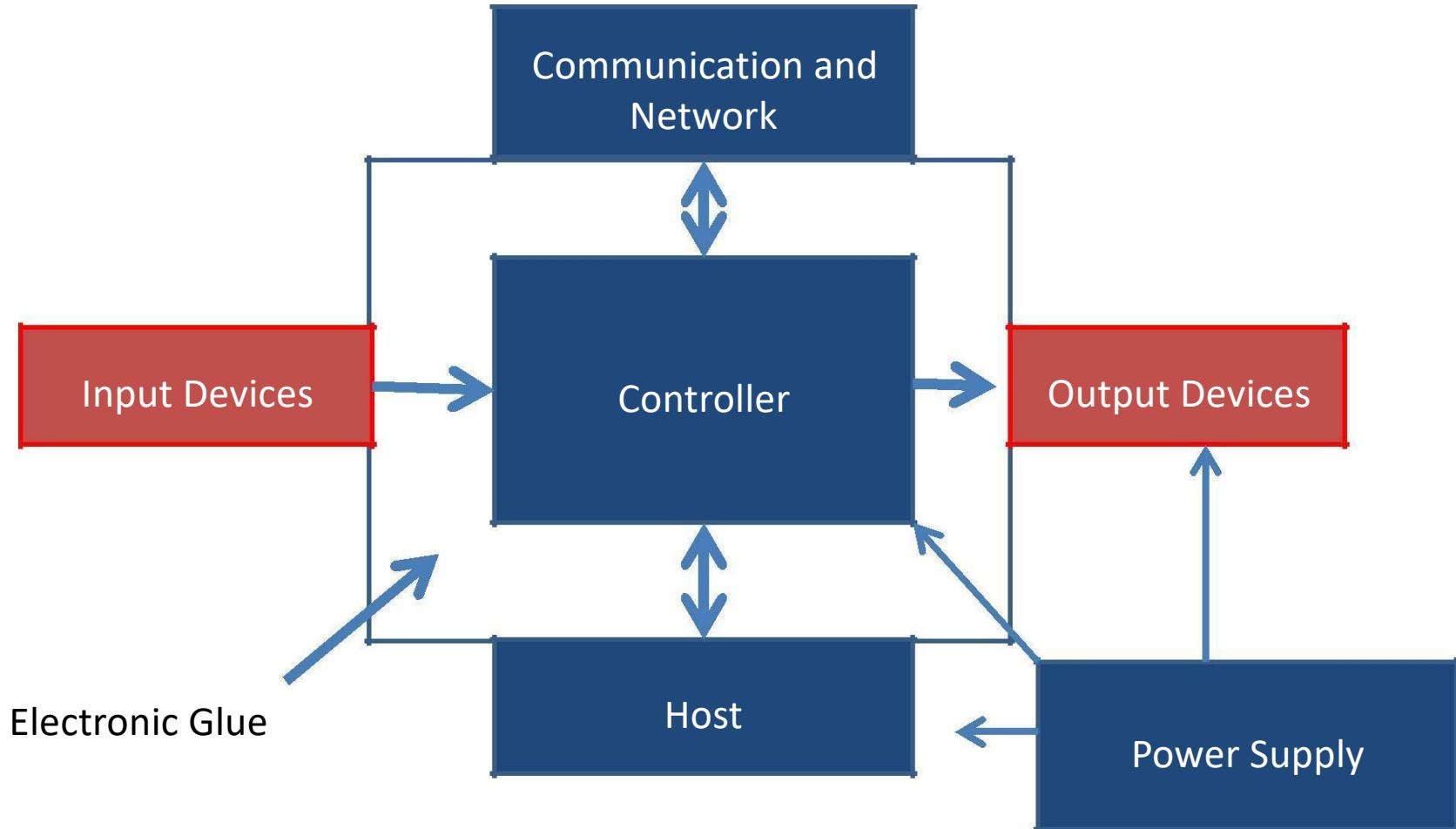

Input Devices



Input Devices

Human Input
Devices

Environment
Sensors

Human Input Devices



- Keyboards
 - Push button
 - Switches (DIP, Slide)
- Pointing device
 - mouse
 - touchpad
 - pointing stick
 - touchscreen
 - trackball

Human Input Devices

- Composite devices
 - Joystick controller
 - Gamepad (or joypad)
 - Paddle (game controller)
 - Jog dial/shuttle (or knob)
 - Wii Remote

Environment Sensors

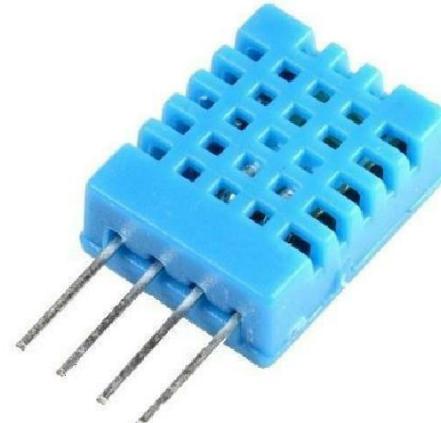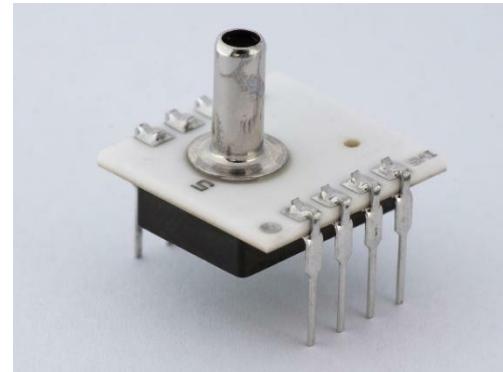- Sensors/Transducers
 - Temperature
 - Light
 - Humidity
 - Sound
 - Magnetic Field
 - Distance
 - Force/Stress/Strain
 - Position/Motion



Multimedia Input Devices

- Graphic input devices
 - Webcam
 - Video Camera
- Audio input devices
 - Microphone

Switches

- An electrical switch is any device used to interrupt the flow of electrons in a circuit.
- A *switch* is an electrical device, usually electromechanical, used to control continuity between two points.
- Binary devices: either completely on (“closed”) or completely off (“open”)

Switches

- Classification:
 - **Mechanical switches**
 - must be activated physically, by moving, pressing, releasing, or touching its contacts.
 - **Electronic switches**
 - do not require any physical contact in order to control a circuit.
 - These are activated by semiconductor action.

Switches

- Classification:
 - *Hand* switches: actuated by human touch.
 - *Limit* switches: actuated by machine motion.
 - *Process* switches: actuated by changes in some physical process (temperature, level, flow, etc.).

Switches

- Types
 - Push button switch
 - DIP Switch
 - Rocker Switch
 - Rotary Switch
 - Toggle Switch
 - Others..!

Push Button Switch





It is a momentary contact switch that makes or breaks connection as long as pressure is applied (or when the button is pushed).

Toggle Switch



These are used for switching high currents (as high as 10 A) and can also be used for switching small currents.

DIP Switches

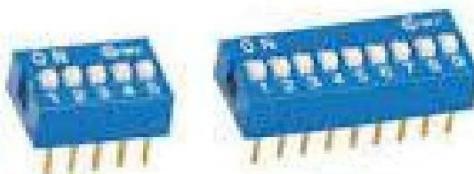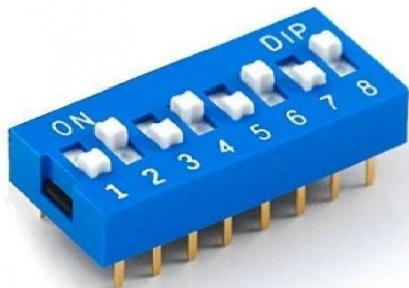

Rocker Switch





- A **rocker switch** is an on/off **switch** that rocks (rather than trips) when pressed
- One side of the **switch** is raised while the other side is depressed much like a rocking horse rocks back and forth.

Rotary Switch



Limit Switch

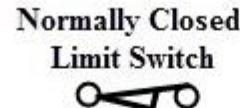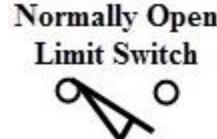


- Switches are operated by the presence of an object or by the absence of objects or by the motion of machine instead of human hand operation.
- These switches are called as limit switches.
- These switches consist of a bumper type of arm actuated by an object.
- When this bumper arm is actuated, it causes the switch contacts to change position.

Limit Switch




Others..!

Selector switch

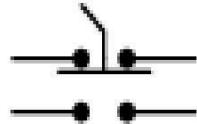

Joystick switch

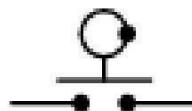

Liquid flow switch



Pressure switch



Temperature switch



Liquid level switch



Others..!


- **Float switches** are mainly used for controlling DC and AC motor pumps according to the liquid or water in a tank or sump.
- **Flow switches** are mainly used to detect the movement of liquid or air flow through a pipe or duct. The air flow switch (or a micro switch) is constructed by a snap-action.
- **Pressure switches** are commonly used in industrial applications in order to sense the pressure of hydraulic systems and pneumatic devices.
- The **temperature switch** contacts are operated when the temperature causes the strip to bend or wrap.
- **Joystick switches** are manually actuated control devices used mainly in portable control equipment's.
 - It consists of a lever which moves freely in more than one axis of motion.
 - Depending on the movement of the lever pushed, one or more switch contacts are actuated.

Keypad




4x4 Matrix Keypad


Keypad Interfacing

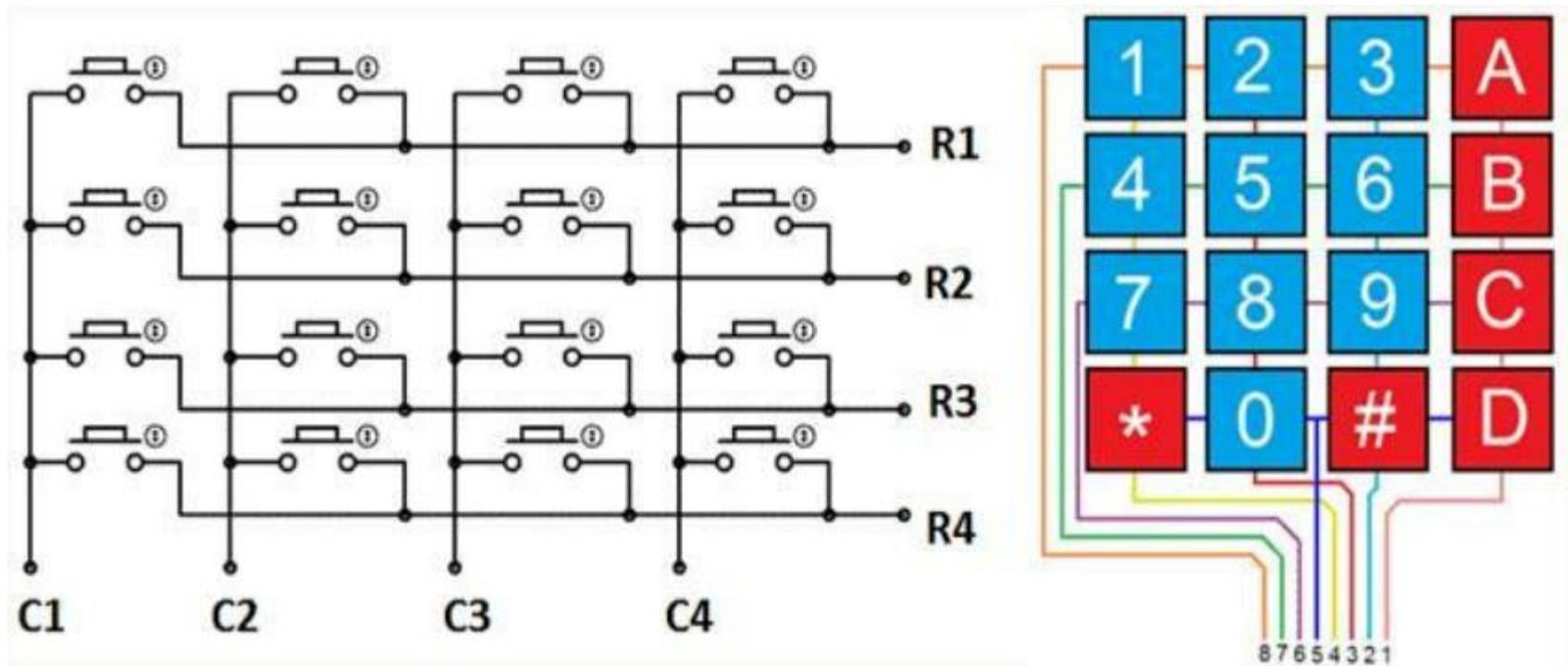



Keypad Interfacing

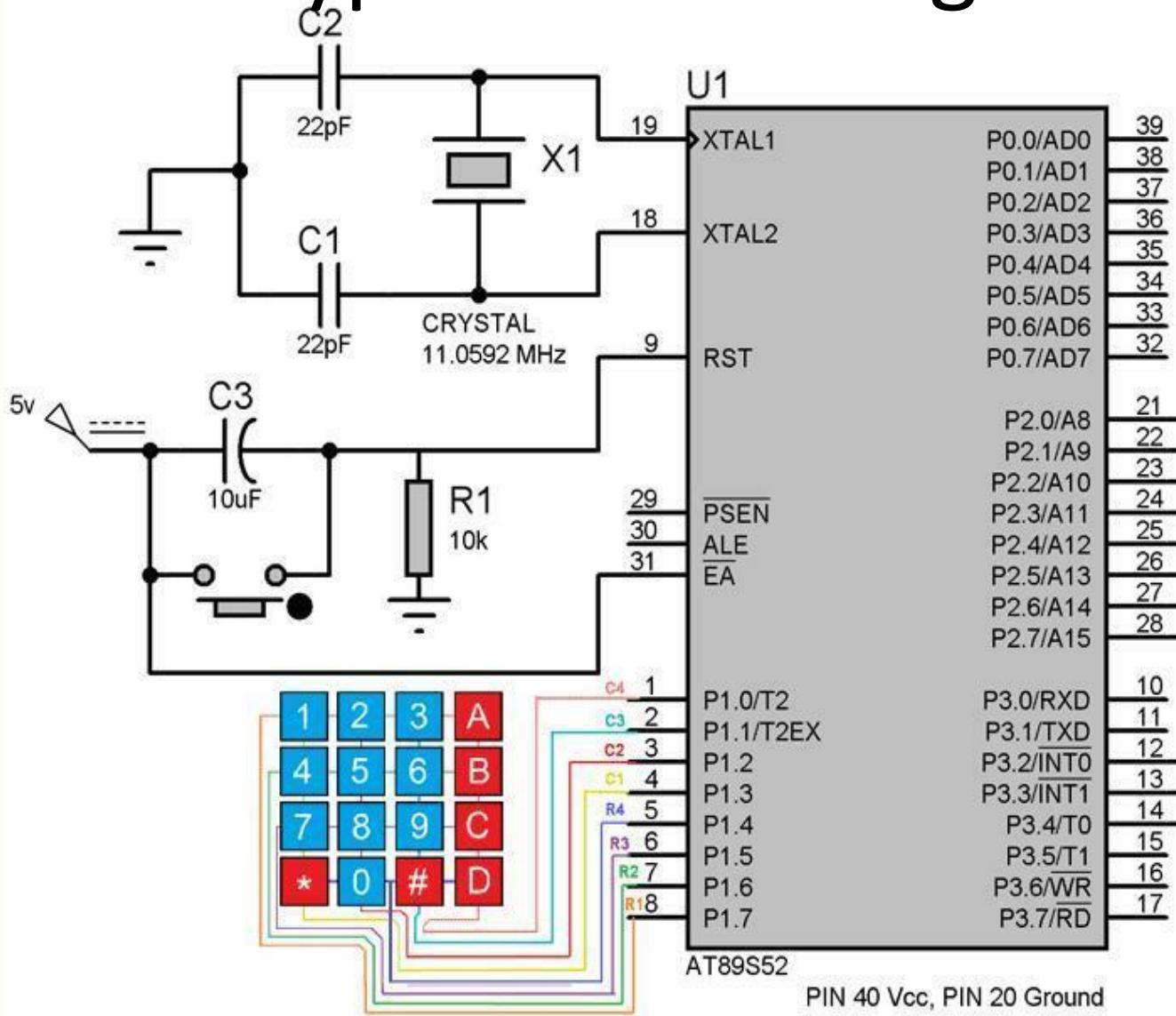

Keypad Interfacing


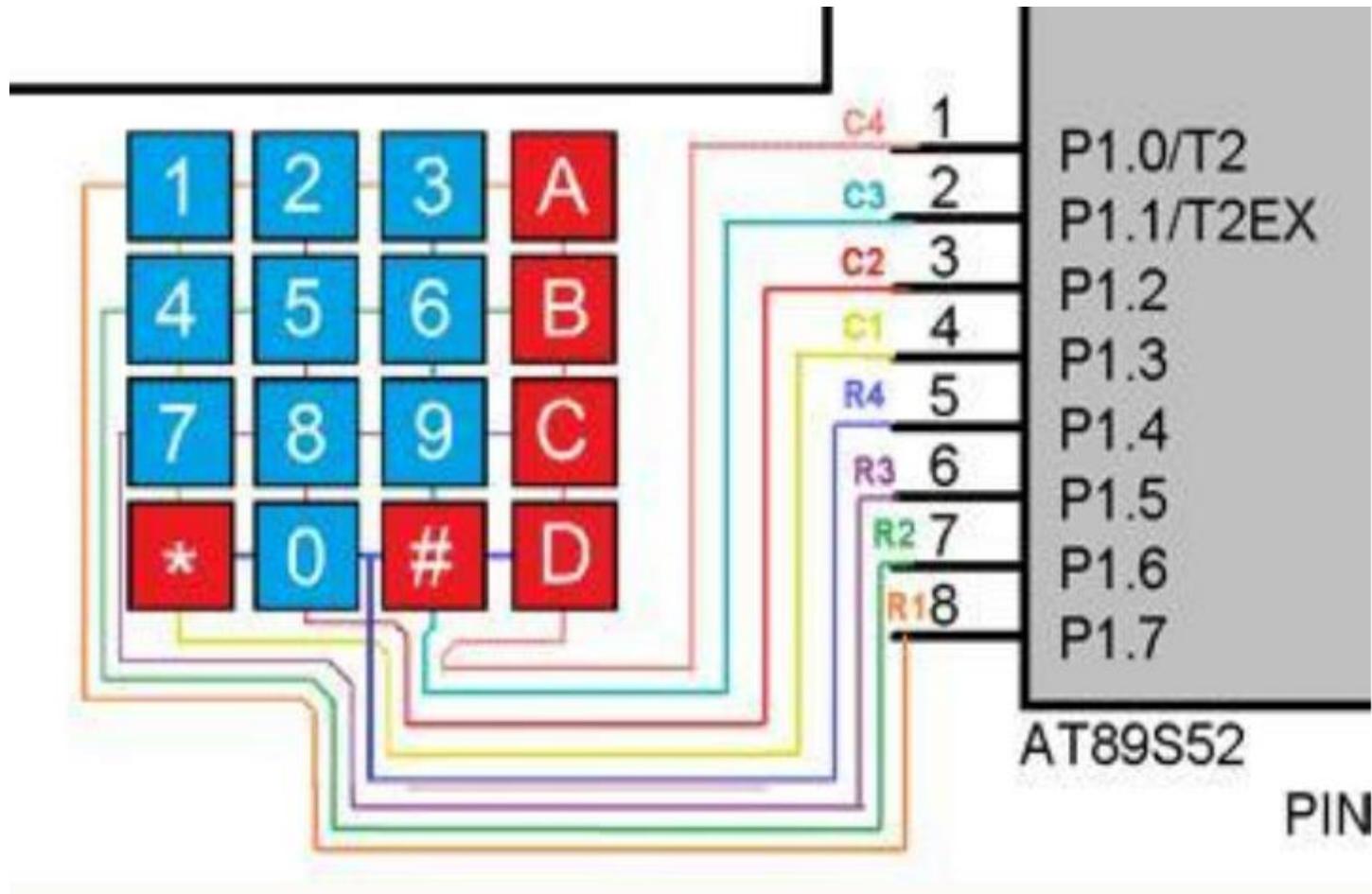


Keypad Interfacing

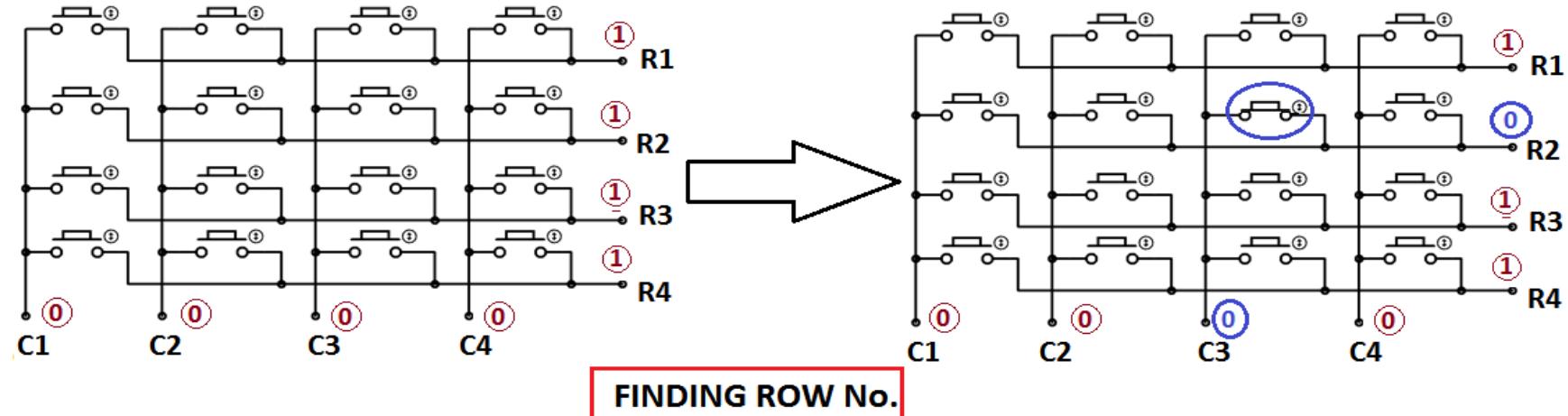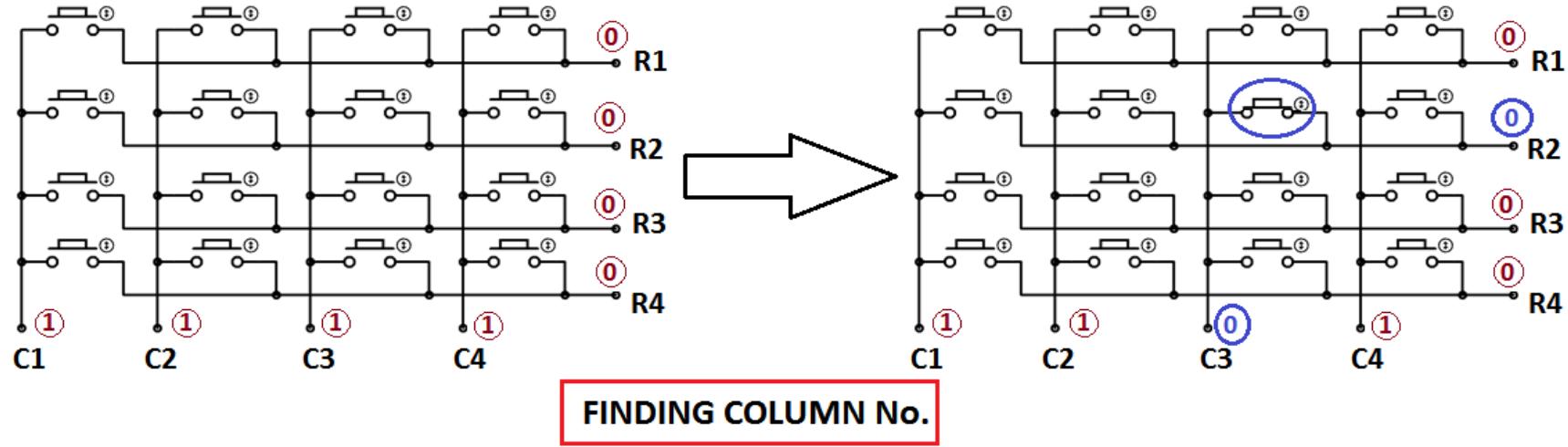

Environment Sensors

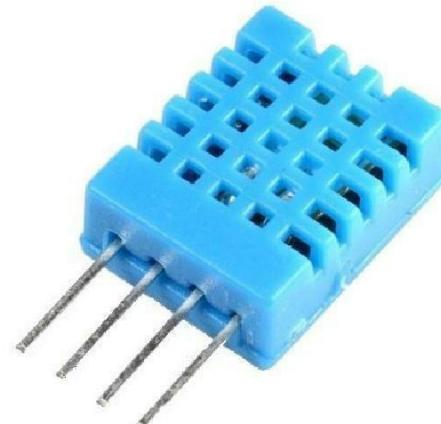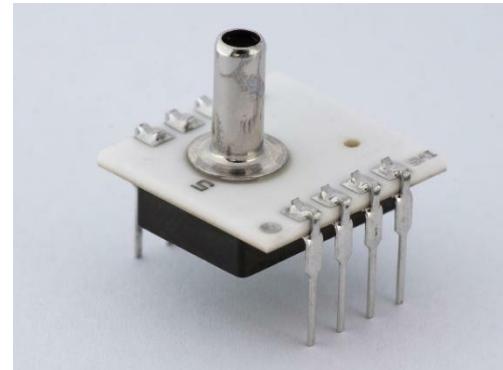- Sensors/Transducers
 - Temperature
 - Light
 - Humidity
 - Sound
 - Magnetic Field
 - Distance
 - Force/Stress/Strain
 - Position/Motion



Temperature Sensors

1. Negative Temperature Coefficient (NTC) thermistor

- The effective operating range is -50 to 250 °C for glass encapsulated thermistors or 150°C for standard.

2. Resistance Temperature Detector (RTD)

- also known as a resistance thermometer
- across -200 to 600 °C.

3. Thermocouple

- Consists of two wires of different metals connected at two points.
- The varying voltage between these two points reflects proportional changes in temperature.
- operate across the widest temperature range, from -200 °C to 1750 °C.


4. Semiconductor-based sensors

- A semiconductor-based temperature sensor is placed on integrated circuits (ICs).
- Two identical diodes with temperature-sensitive voltage vs current characteristics used to monitor changes in temperature.
- narrowest temperature range (-70 °C to 150 °C).


Temperature Sensors

	Thermocouple	RTD	Thermistor	I. C. Sensor
Advantages	<ul style="list-style-type: none"> ■ Self-powered ■ Simple ■ Rugged ■ Inexpensive ■ Wide variety ■ Wide temperature range 	<ul style="list-style-type: none"> ■ Most stable ■ Most accurate ■ More linear than thermocouple 	<ul style="list-style-type: none"> ■ High output ■ Fast ■ Two-wire ohms measurement 	<ul style="list-style-type: none"> ■ Most linear ■ Highest output ■ Inexpensive
Disadvantages	<ul style="list-style-type: none"> ■ Non-linear ■ Low voltage ■ Reference required ■ Least stable ■ Least sensitive 	<ul style="list-style-type: none"> ■ Expensive ■ Current source required ■ Small ΔR ■ Low absolute resistance ■ Self-heating 	<ul style="list-style-type: none"> ■ Non-linear ■ Limited temperature range ■ Fragile ■ Current source required ■ Self-heating 	<ul style="list-style-type: none"> ■ $T < 200^\circ\text{C}$ ■ Power supply required ■ Slow ■ Self-heating ■ Limited configurations



Temperature Sensors

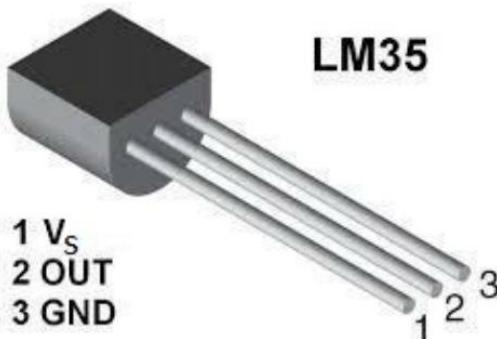

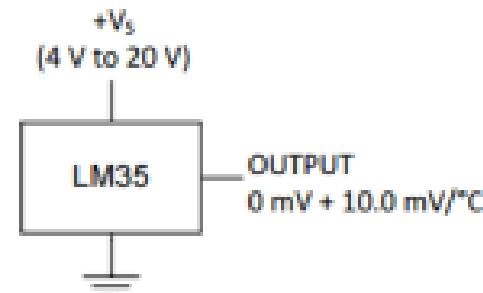**Basic Centigrade Temperature Sensor
(2°C to 150°C)**




Characteristics of LM35

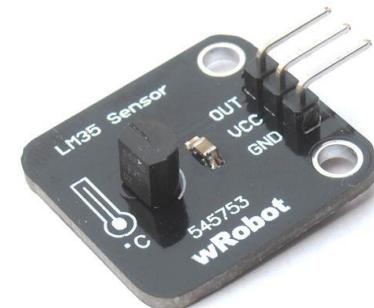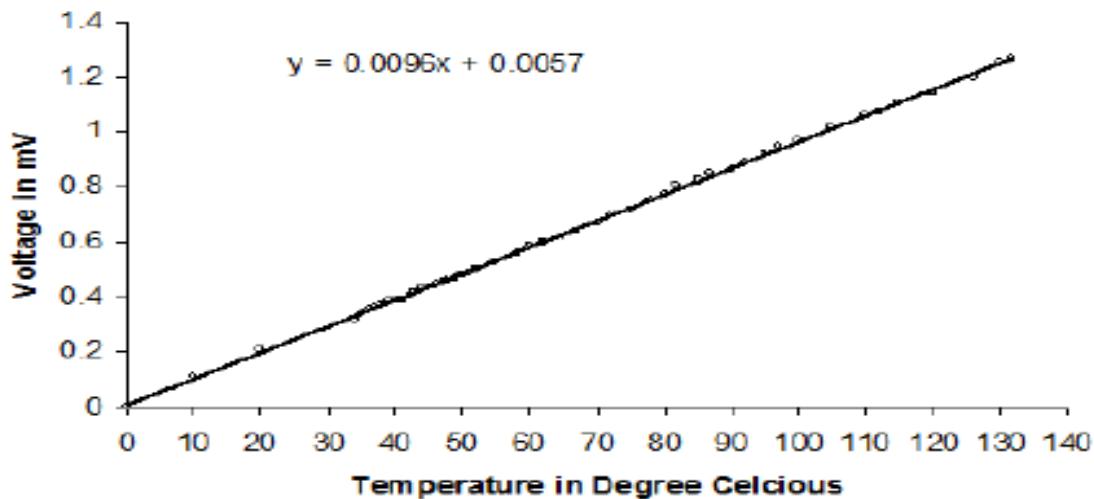

Temperature Sensors

AD22100/AD22103

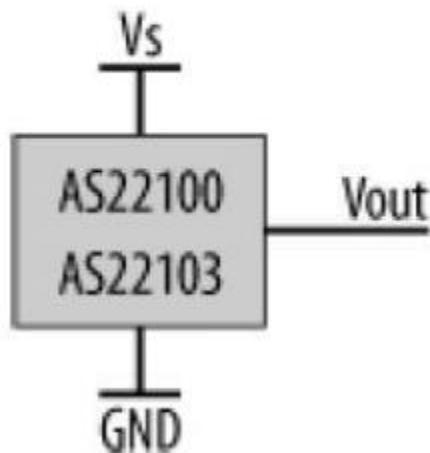


$$TA = ((V_{out} \times 5 / V_s) - 1.375) / 0.0225$$

----- for AD22100 (-50°C to +150 °C)

$$TA = ((V_{out} \times 3.3 / V_s) - 0.25) / 0.028$$

----- for AD22103 (0°C to +100 °C)




Temperature Sensors

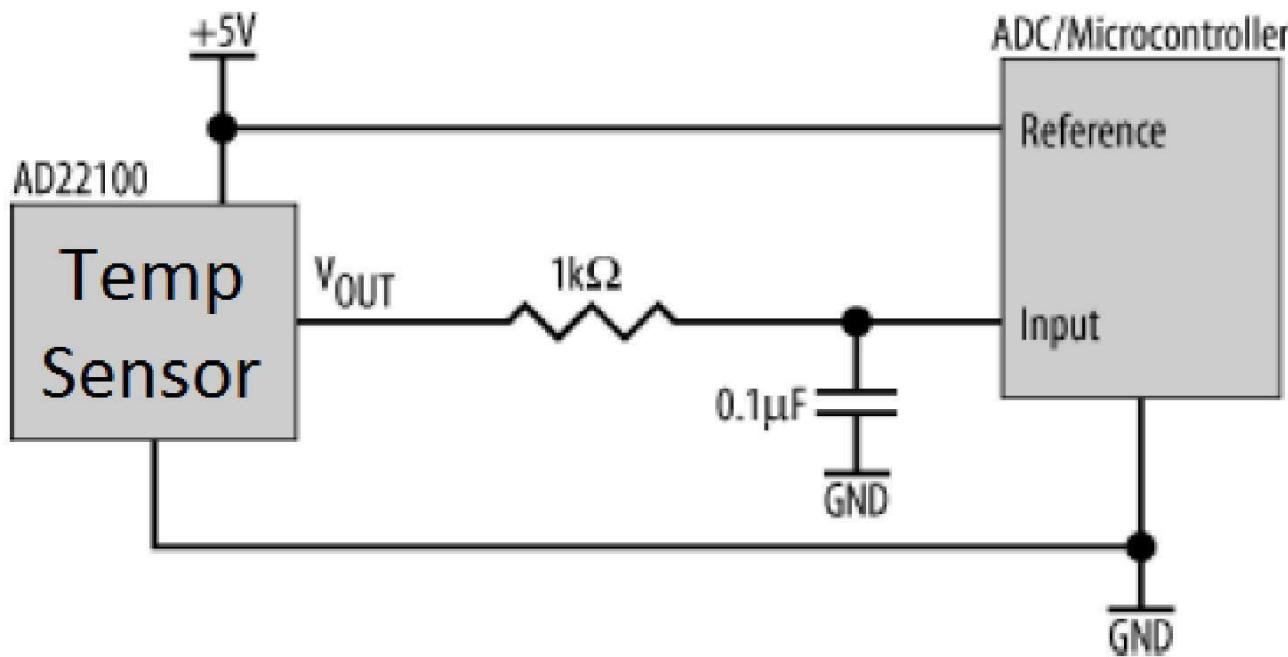

Temperature Sensors

Manufacturer	Part Number	Output Type	Designation	Temp. Range	Accuracy (Typical)	Accuracy (Min)	Linear Temperature Slope	Input Voltage Range	Supply current	Output Voltage Range	Package	Datasheet
Analog Devices	AD590 ^[8]	Analog	IC Temperature Transducer	-55 to 150 °C	+/-0.5 °C		1 μA / °K	4 to 30 V		298.2 μA @25 °C	TO52SO8 FLATPACK LFCSP	AD590
Analog Devices	AD592 ^[9]	Analog	Precision IC Temperature Transducer	-25 to 105 °C	+/-0.5-2 °C	+/-1-3.5 °C	1 μA / °K	4 to 30 V	-	298.2 μA @25 °C	TO92	AD592
Analog Devices	AD22105 ^[10]	Switch	Resistor Programmable Thermostatic Switch	-40 to 150 °C	+/-0.5 °C	+/-3 °C	-	2.7 to 7 V	120 μA max	-	SO8	AD22105
Dallas	DS18B20	Digital	Temperature Sensor with 1wire interface	-55 to +125 °C	+/-0.5 °C (@ -10 - +85 °C)	+/-2 °C		3 to 5.5 V	1 mA (active)		TO928 SO 8 FSOP	
Microchip	EMC1072 ^[11]	Digital	SMBus / I2C Multi Temperature Sensor	-40 to +125 °C	0.25 °C	+/-1 °C		3.0 to 3.6 V	430 μA	-	MSOP8	EMC1072
Microchip	MCP9509 ^[18]	Switch	Resistor-Programmable Temperature Switch	-40 to +125 °C	+/-1 °C	+/-4.5 °C	-	2.7 to 5.5 V	30 μA (50 μA max)	-	4 μASOT23-5	MCP9509
Microchip	MCP9700 ^[19]	Analog	Voltage Temperature Sensor	-40 to +150 °C	1 °C	+/-4 °C	10 mV / °C	2.3 to 5.5 V	6μA (12 μA Max)		SC70-5SOT23-5 TO92	MCP9700
Microchip	MCP9700A ^[20]	Analog	Voltage Temperature Sensor		1 °C	+/-2 °C	10 mV / °C	2.3 to 5.5 V	6μA (12 μA Max)		SC70-5SOT23-5	MCP9700A
Microchip	MCP9701 ^[21]	Analog	Voltage Temperature Sensor		1 °C	+/-4 °C	19.53 mV / °C	3.1 to 5.5 V	6μA (12 μA Max)		SC70-5SOT23-5 TO92	MCP9701
Texas Instruments	LM35 ^[31]	Analog	Analog Output Temperature Sensor	-55 to +150 °C	+/-0.5 °C	+/-1.5 °C	10 mV / °C	4 to 30 V	114 μA		S08TO92 TO220 TO-CAN	LM35
Texas Instruments	LM50 ^[32]	Analog	Analog Output Temperature Sensor	-40 to +125 °C	+/-2 °C	+/-4 °C	10 mV / °C	4.5 to 10 V	130 μA	100 mV to 1.750 V	SOT23	LM50
Texas Instruments	LM73 ^[33]	Digital	Temperature Sensor with IC2/SMBus Interface	-40 to +150 °C	+/-1.0 °C	+/-2.5 °C	-	2.7 to 5.5 V	320 μA (2 μA Shutdown)	-	SOT (6 pin)	LM73
Texas Instruments	LM76 ^[34]	Digital	Temperature Sensor with IC2/SMBus Interface	-55 to +150 °C	+/-1.0 °C		-	4.5 to 5.5 V	250 μA (8 μA max Shutdown)	-	SO8	LM76


Light Sensor

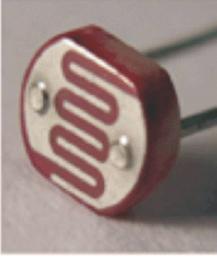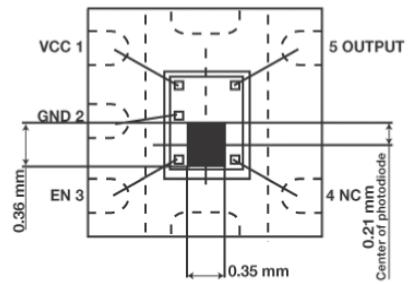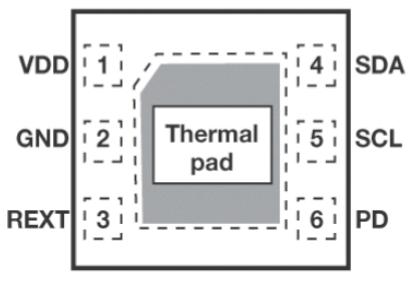Device	Photo resistor	Photo diode	Photo transistor	Photo diode and current amplifier	Photo diode, current amp, ADC and filter
Referenced part #	PDV-P500X	Everlight DTD-15	Everlight DPT-092	EL7900	ISL29001
					
Accuracy	Not guaranteed	Not guaranteed	$\pm 75\%$	$\pm 33\%$	15-bit resolution
Current (1000 lux)	Varies	$3 \mu\text{A}$	2.6 mA (70 klux)	0.9 mA	0.3 mA
Range	1 to 100 lux	7 to 50 klux	1 k to 100 klux	1 to 100 klux	0.3 to 10 klux
Response time	55 ms	6 ns	15 μs	0.5 ms	100 ms
Enable function	No	No	No	Yes	Yes


Light Sensor



Light Sensor

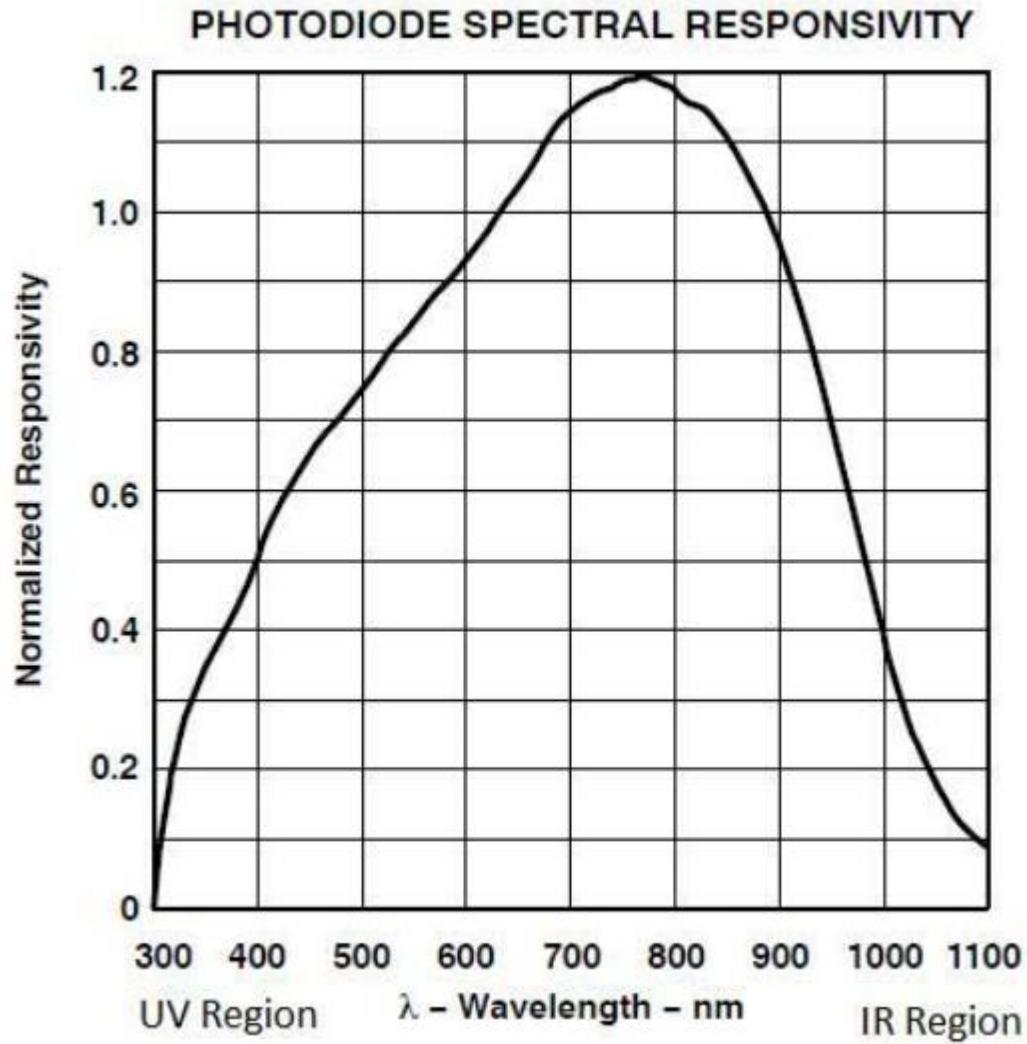

Light Sensor


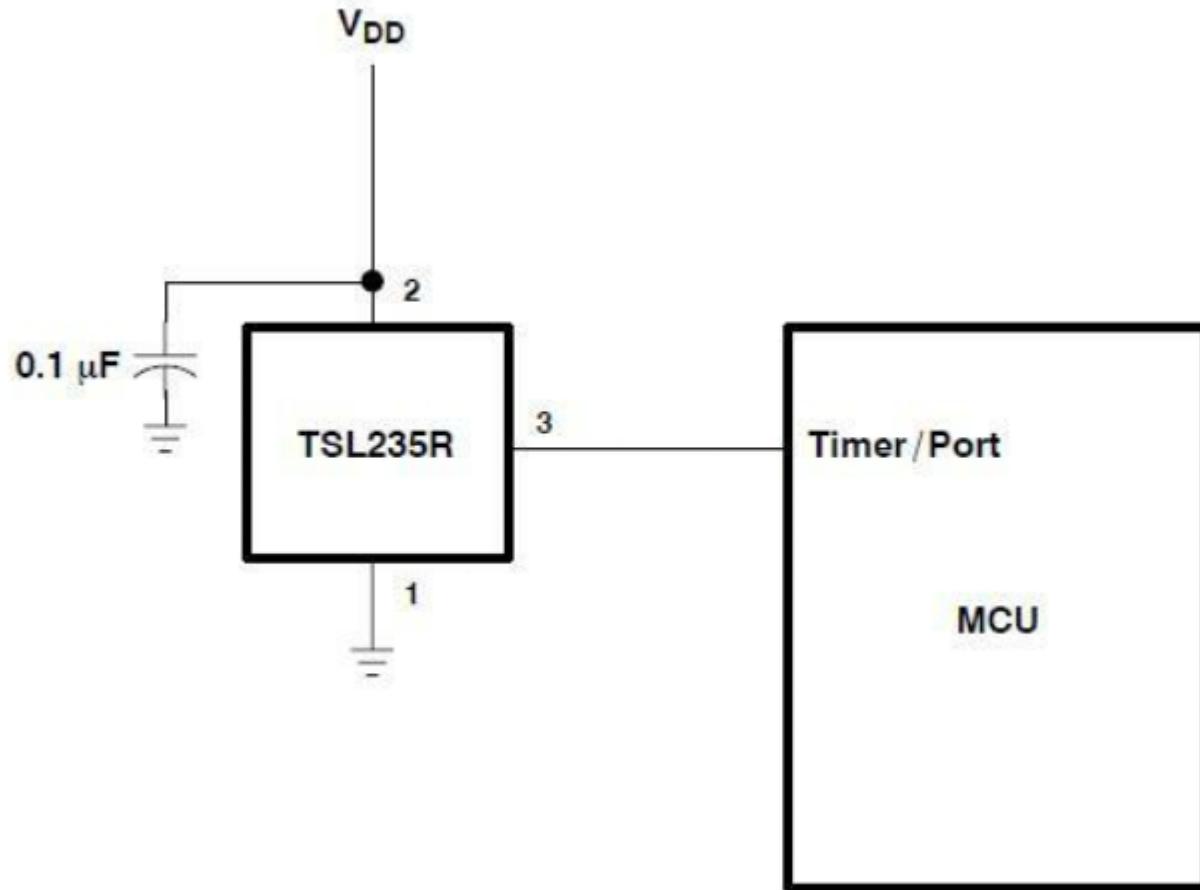


Accelerometer



www.afrotechmods.com

Accelerometer

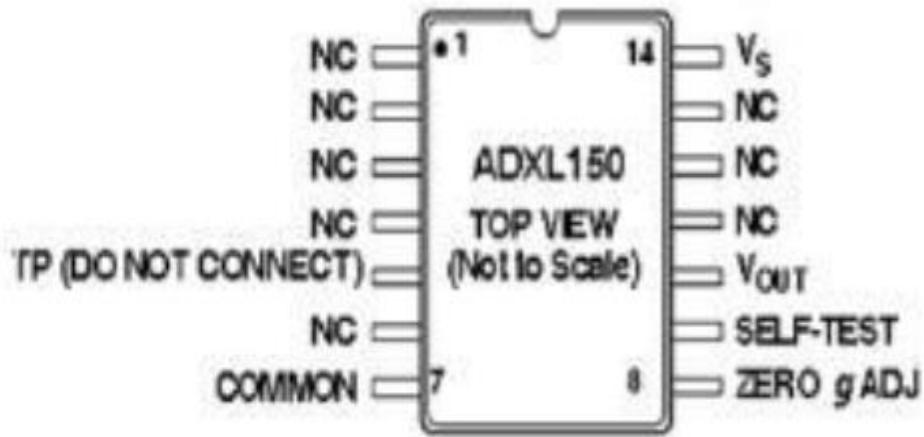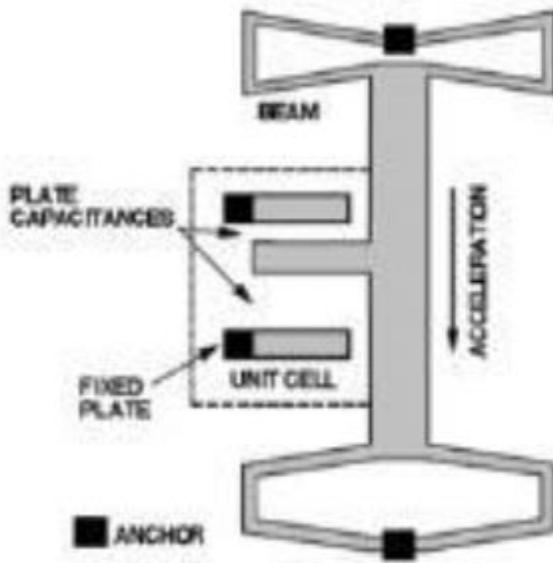

Single / Dual Axis measurement

Obsolete

ADXL335 - 3 axes Accelerometer




**ANALOG
DEVICES**

FEATURES

- 3-axis sensing
- Small, low profile package
 - 4 mm × 4 mm × 1.45 mm LFCSP
- Low power : 350 µA (typical)
- Single-supply operation: 1.8 V to 3.6 V
- 10,000 g shock survival
- Excellent temperature stability
- BW adjustment with a single capacitor per axis
- RoHS/WEEE lead-free compliant

APPLICATIONS

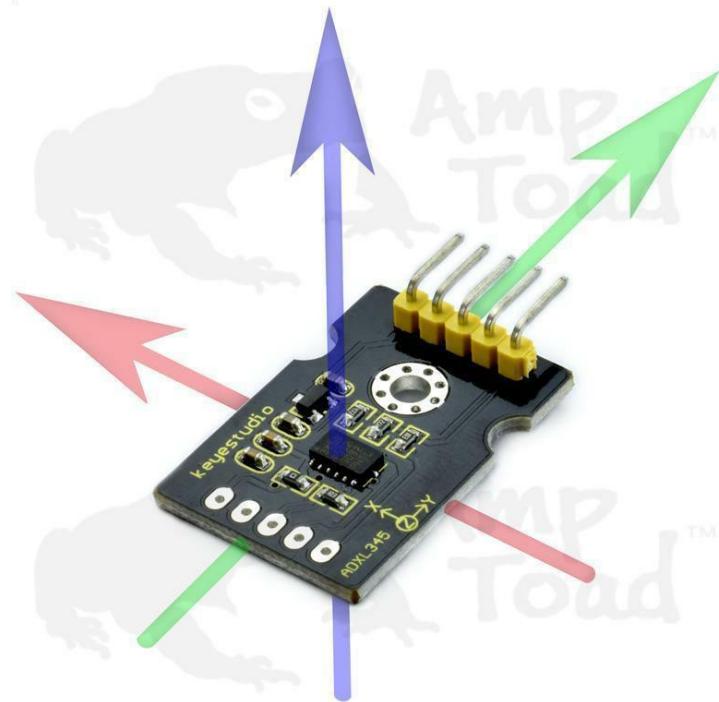- Cost sensitive, low power, motion- and tilt-sensing applications
- Mobile devices
- Gaming systems
- Disk drive protection
- Image stabilization
- Sports and health devices



3 Axes Accelerometer

FUNCTIONAL BLOCK DIAGRAM


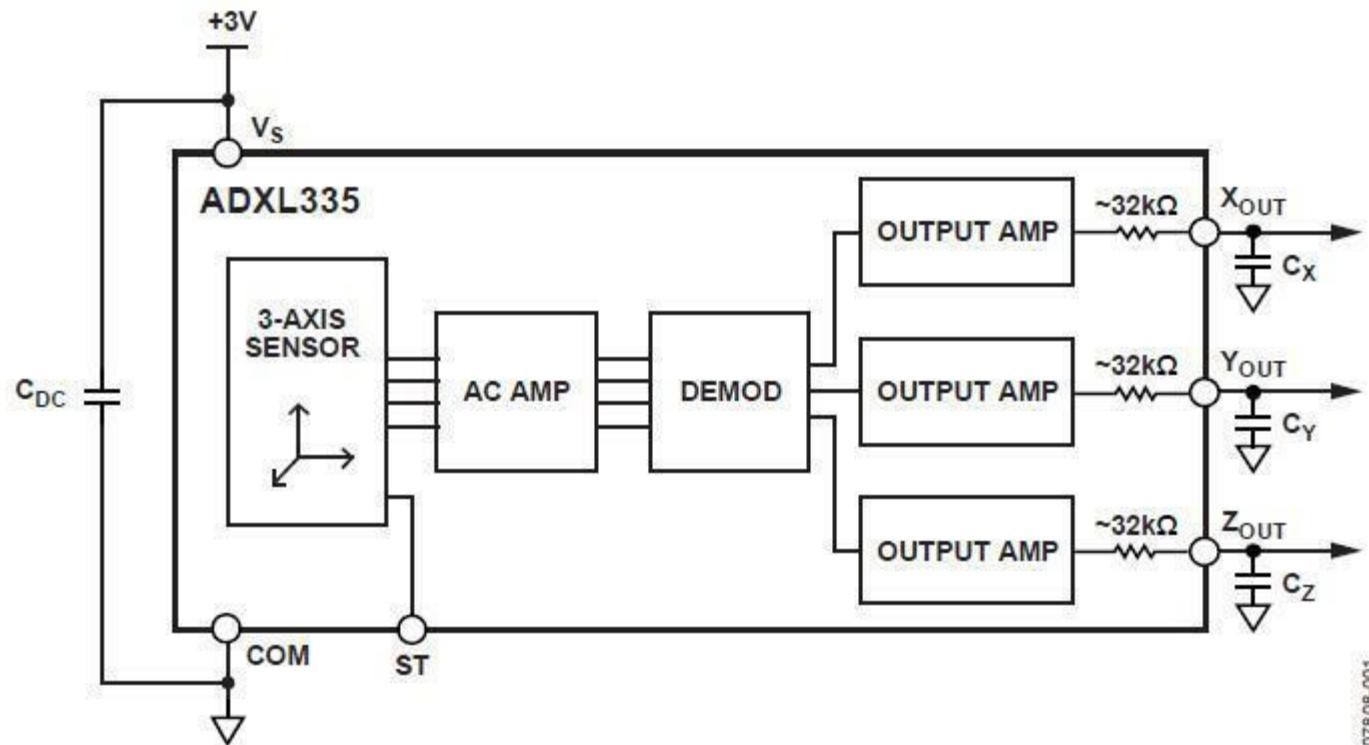



Figure 1.

07808-001

3 Axes Accelerometer

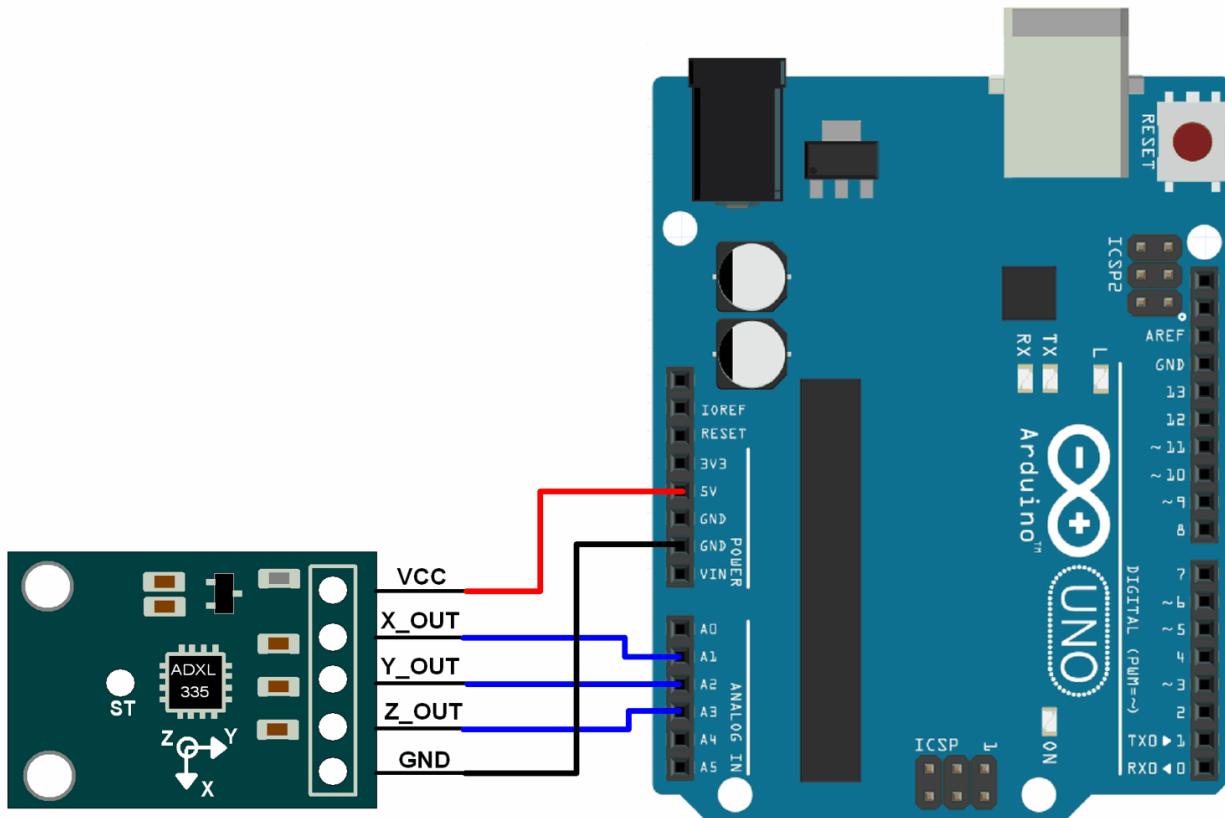

Pressure Sensor

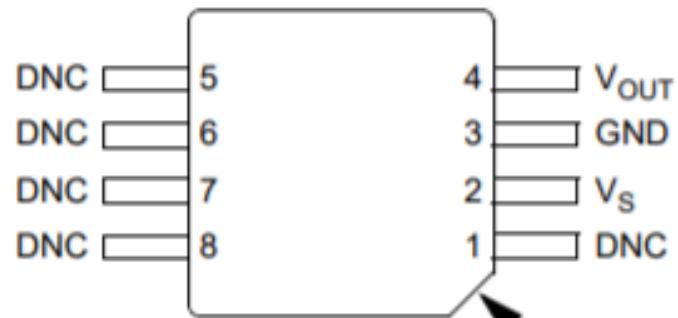

Pin 1 identification
chamfered corner
or notch in pin

Pinout

Piezoresistive material based

A **pressure sensor** is a device for **pressure** measurement of gases or liquids.

Pressure Sensor


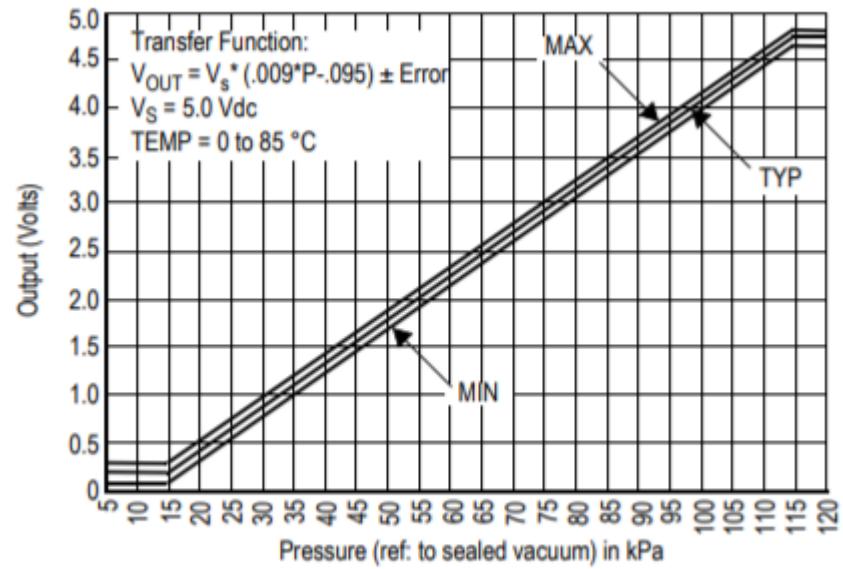
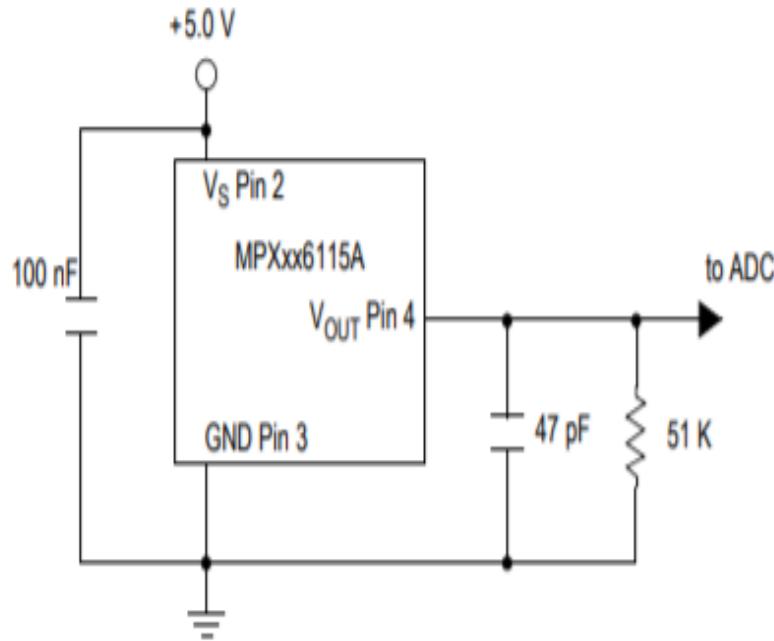


Figure 5. Output vs. absolute pressure

The MPXxx6115A series sensor integrates on-chip, bipolar op amp circuitry and thin film resistor networks to provide a high output signal and temperature compensation

Magnetic Field Sensors

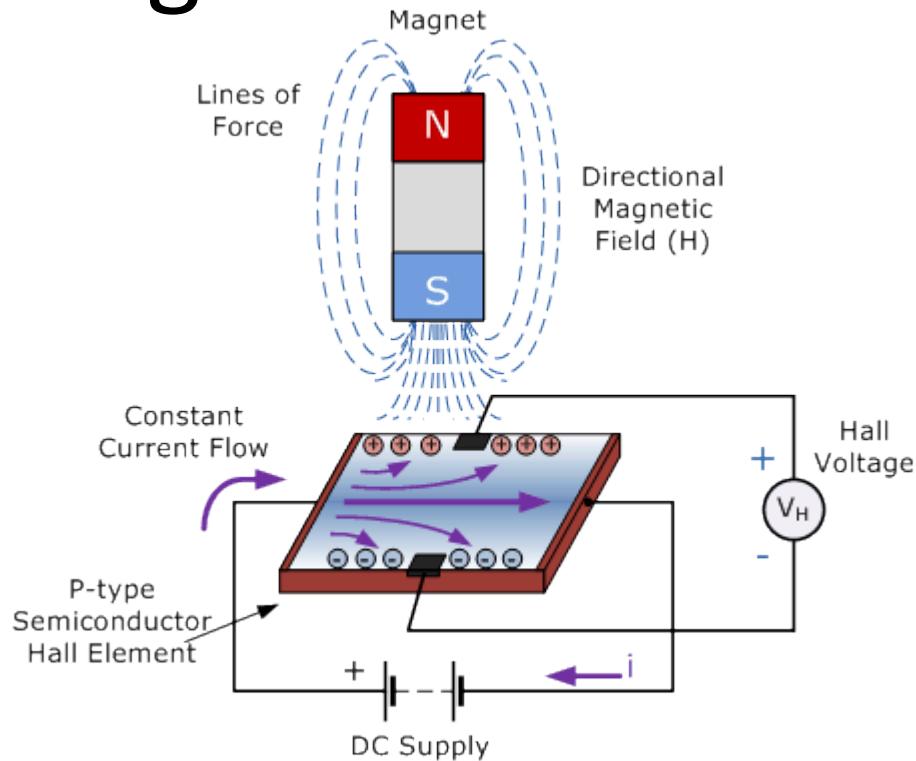


Working principle – Hall Effect

In the presence of a **magnetic field**, the electrons in the metal strip are deflected toward one edge, producing a voltage gradient across the short side of the strip (perpendicular to the feed current).

In its simplest form, the **sensor** operates as an analog transducer, directly returning a voltage.

Magnetic Field Sensors

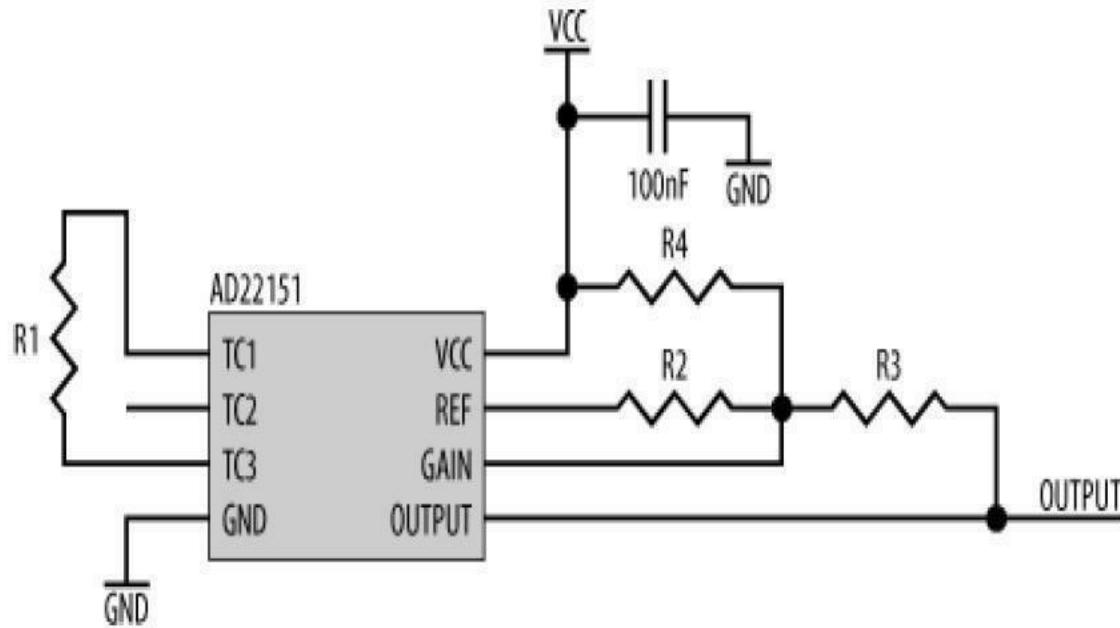


- Works on 5V Supply
- R1: Temperature Compensation Resistor
- R2, R3: Resistor to set the signal gain
- R4: Voltage offset resistor

Magnetic Field Sensors

Humidity Sensor

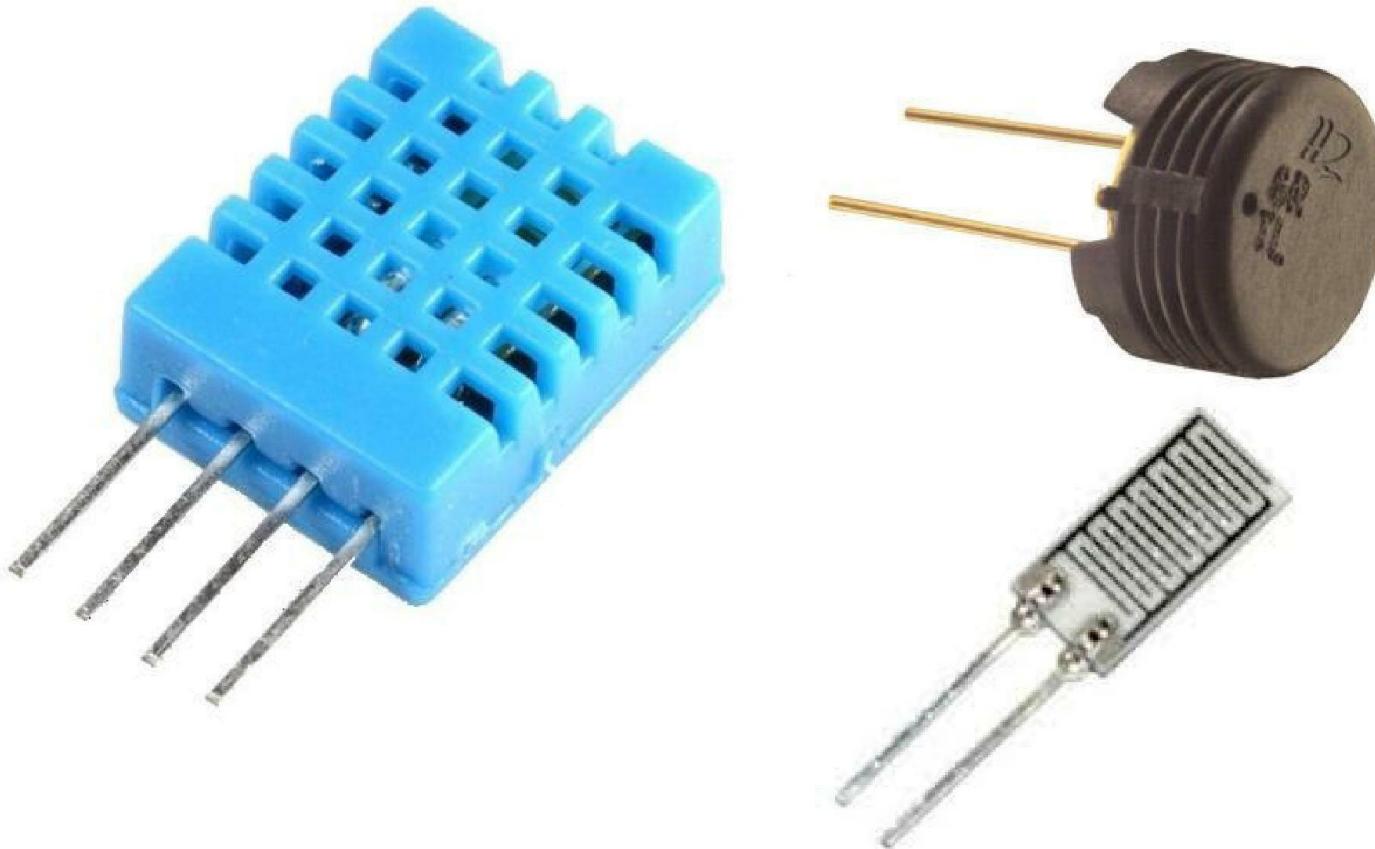Humidity is defined as the amount of water present in the surrounding air.



Humidity Sensor

Absolute humidity

- It is the measure of water vapor (moisture) in the air, regardless of temperature.
- It is expressed as grams of moisture per cubic meter of air (g/m³).
- The maximum absolute humidity of warm air at 30°C is approximately 30g of water vapor - 30g/m³

$$AH = m/V$$

Relative Humidity

- Ratio of the amount of water vapor actually present in the air to the greatest amount possible at the same temperature
- Relative humidity depends on temperature and the pressure of the system of interest.


Humidity Sensor

Humidity sensors work by **detecting changes that alter electrical currents or temperature in the air.**


Types of humidity sensors:

- Capacitive
- Resistive
- Thermal

Humidity Sensor

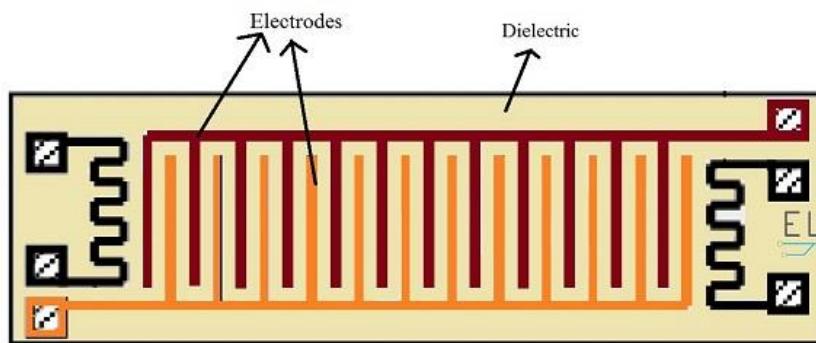

Top View

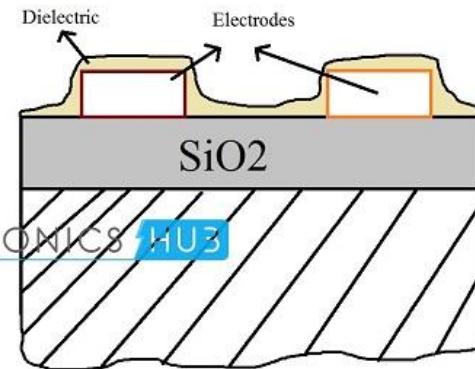

Cross Section


Capacitive

- Measures relative humidity by placing a thin strip of metal oxide between two electrodes.
- The metal oxide's electrical capacity changes with the atmosphere's relative humidity.
- The capacitive type sensors are linear and can measure relative humidity from 0% to 100%.
- These are the only types of full-range relative humidity measuring devices down to 0% relative humidity.

Humidity Sensor

Resistive

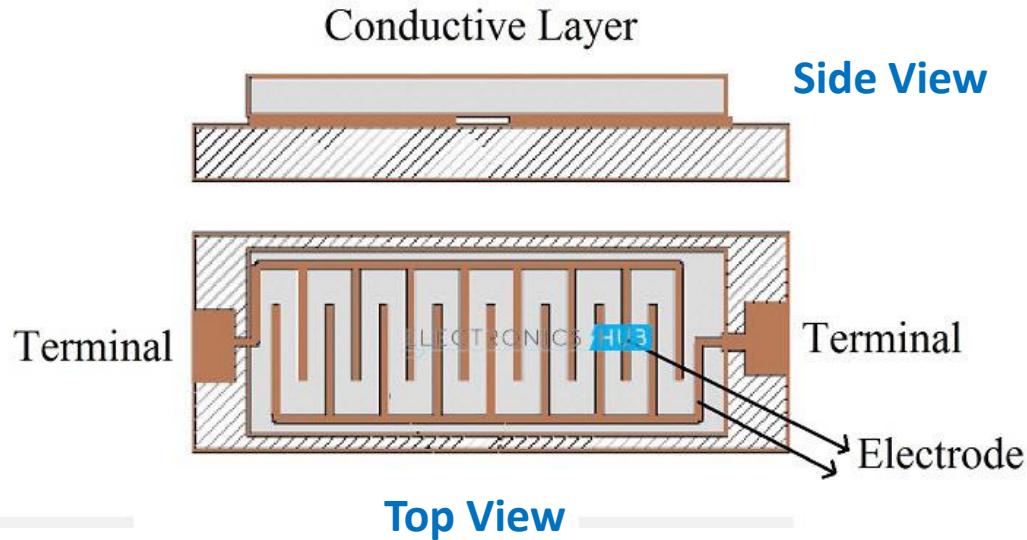- The Resistive Humidity Sensor is usually made up of materials with relatively low resistivity
- The resistivity changes significantly with changes in humidity.
- The resistivity between the electrodes changes when the top layer absorbs water




Humidity Sensor

Thermal

- Two thermal sensors conduct electricity based upon the humidity of the surrounding air.
- One sensor is encased in dry nitrogen while the other measures ambient air.
- The difference between the two measures the humidity.

Humidity Sensor

DHT 11
Humidity &
Temperature
Sensor

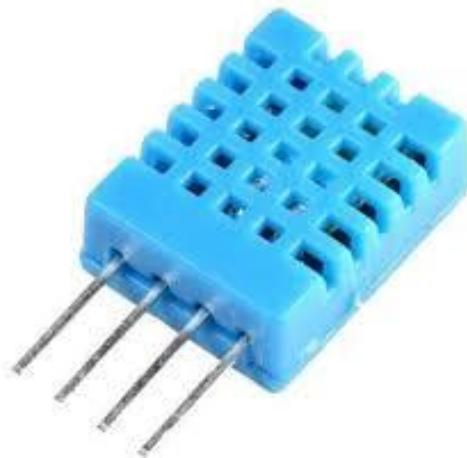

- Digital temperature and humidity **sensor**.
- Uses a capacitive humidity **sensor** and a thermistor
- Gives out a digital signal on the data pin

Item	Measurement Range	Humidity Accuracy	Temperature Accuracy	Resolution	Package
DHT11	20-90%RH 0-50 °C	±5%RH	±2°C	1	4 Pin Single Row

Typical Application

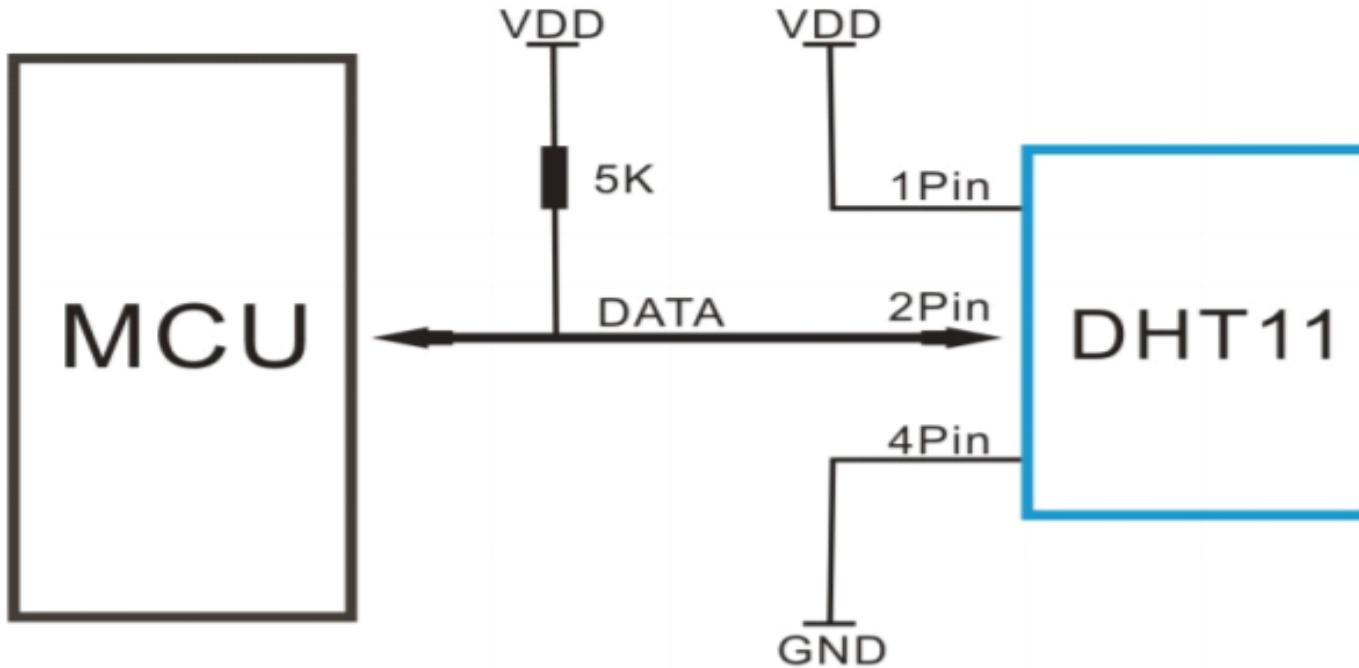



Figure 1 Typical Application

Note: 3Pin – Null; MCU = Micro-computer Unite or single chip Computer

Communication Process: Serial Interface (Single-Wire Two-Way)

Humidity Sensor

HIH-4000-001 by Honeywell

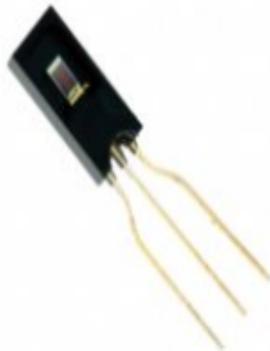

This thermoset polymer-based capacitive sensor offers accuracy: $\pm 3.5\%$ RH, humidity range 0 ~ 100% RH, operating supply current: 200 uA, operating Temperature: -40°C ~ 85°C, supply voltage: 4 V ~ 5.8 V, analog voltage output.

SHT15 by Sensirion



This digital output capacitive sensor offers accuracy: $\pm 2\%$ RH, humidity range 0 ~ 100% RH, operating supply current: 28 uA, operating temperature -40°C ~ 123.8°C, supply voltage: 2.4 V ~ 5.5 V, resolution 12 bit.

Humidity and Temperature Sensor Interfacing

Sound Sensor



Microphone/ Mic

Condenser Microphone,

A parallel plate capacitor and works on the principle of a variable capacitance.


It consists of two plates, one fixed (called the back plate) and the other moveable (called Diaphragm) with a small gap between them.

An electric potential charges the plate. When sound strikes the diaphragm it starts moving, thereby changing the capacitance between the plates which in turn results in a variable electric current to flow.




Sound Sensor Module

Sound Sensor

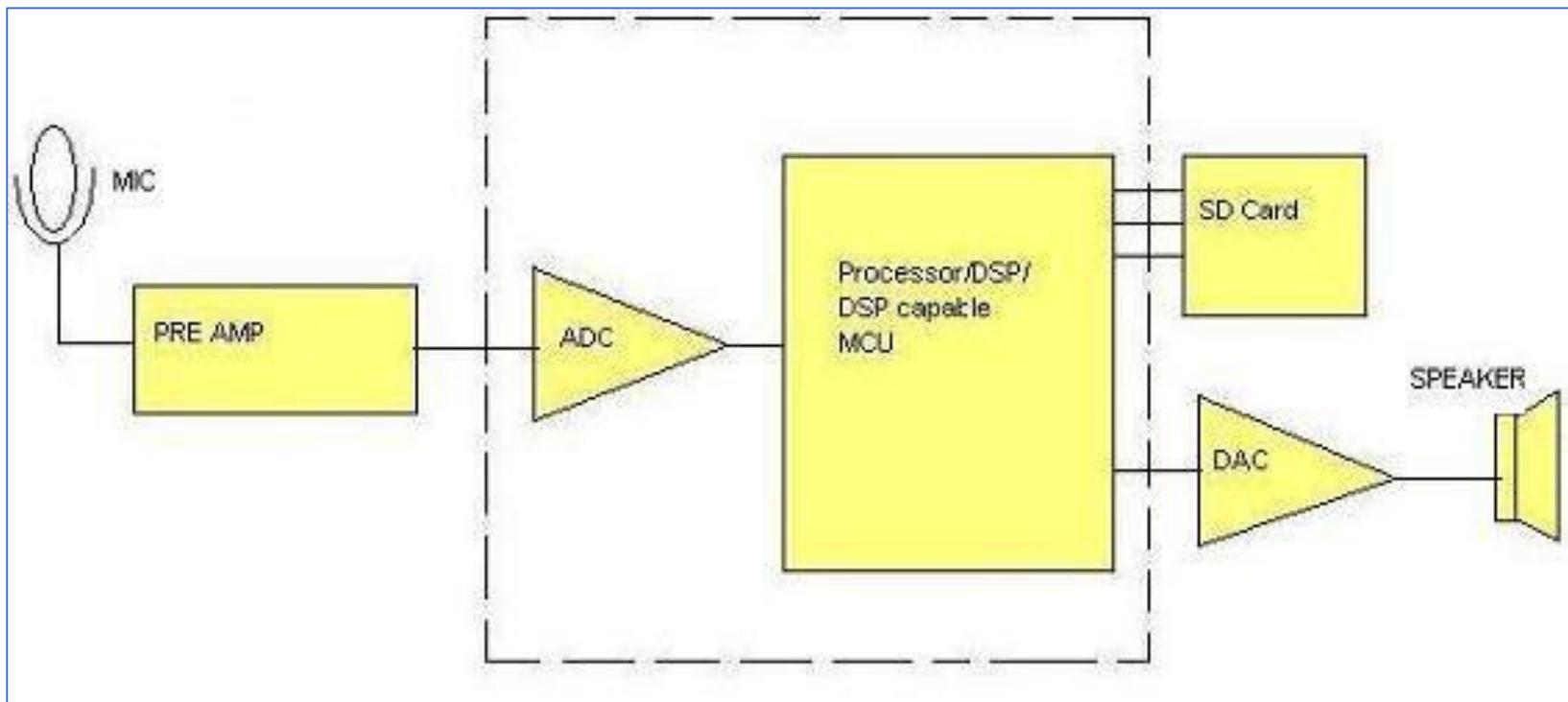


Sound Sensor

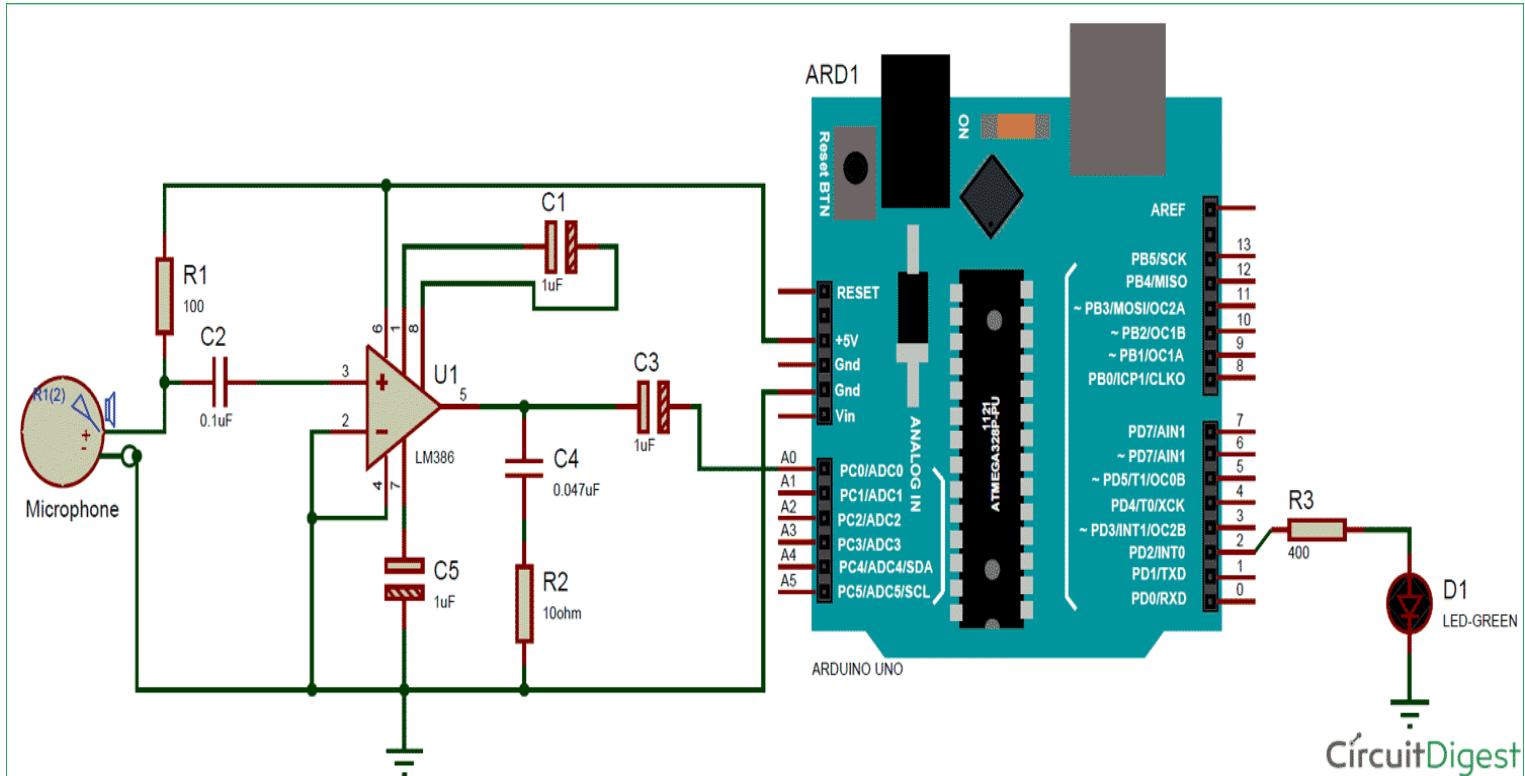

Distance Sensor

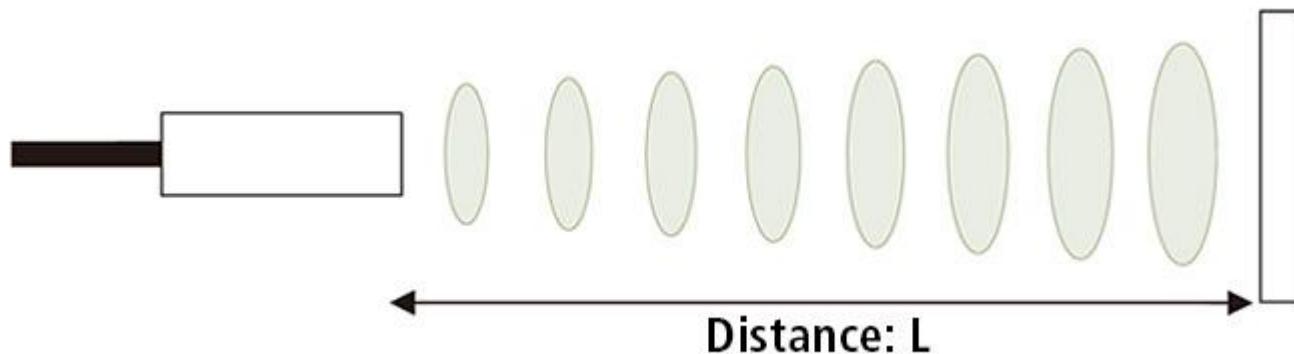- Ultrasonic sensors measure distance by using ultrasonic waves. The sensor head emits an ultrasonic wave and receives the wave reflected back from the target.
- Ultrasonic Sensors measure the distance to the target by measuring the time between the emission and reception.



The distance can be calculated with the following formula:

$$\text{Distance } L = \frac{1}{2} \times T \times C$$

- L is the distance,
- T is the time between the emission and reception,
- C is the sonic speed.
- (The value is multiplied by 1/2 because T is the time for go-and-return distance.)

Distance Sensor

Sensor Module - HC-SR04




The Module automatically sends eight **40 kHz** and detect whether there is a pulse signal back.

Features

- Output: Digital
- Voltage: 5VDC
- Detection distance: 2cm-400cm (0.02M - 4.0M)
- Static current: < 2mA
- Level output: high-5V
- High precision: up to 0.3cm

Distance Sensor

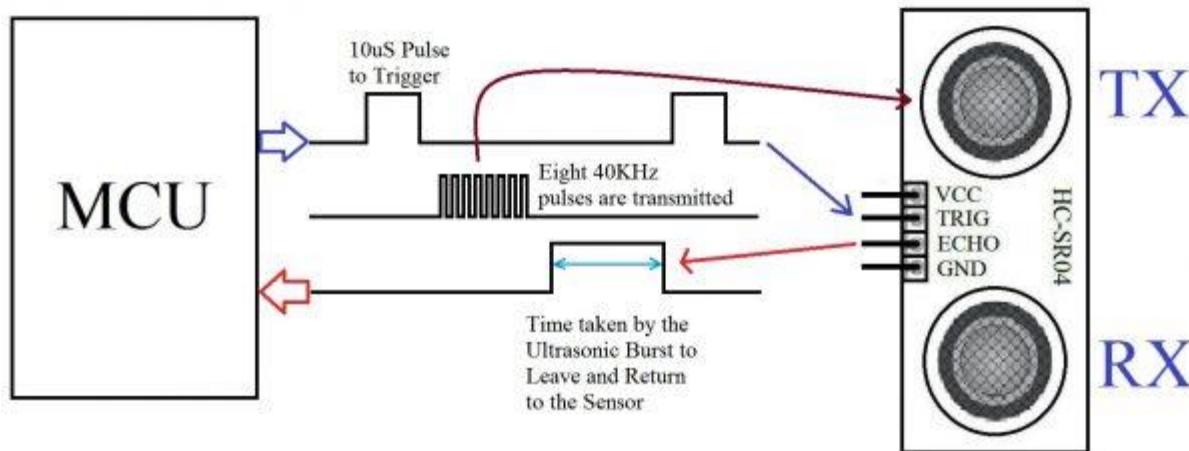

1. Provide TRIGGER signal
2. The module will automatically transmit eight 40KHz ultrasonic burst.
3. If there is an obstacle in-front of the module, it will reflect the ultrasonic burst.
4. If the signal is back, ECHO output of the sensor will be in HIGH state (5V) for a duration of time taken for sending and receiving ultrasonic burst.


Pulse width ranges from about $150\mu\text{s}$ to $25\text{m}\text{s}$ and if no obstacle is detected, the echo pulse width will be about 38ms .

Ultrasonic Sensor

Output Devices



Output Devices

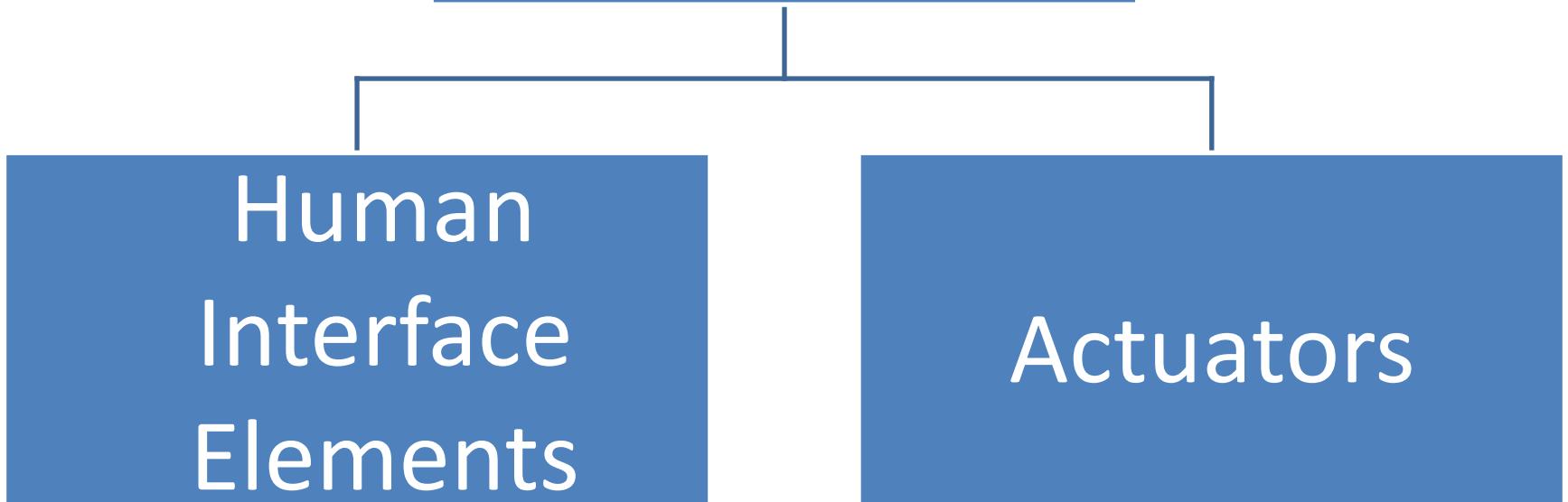



Output Devices

- Position
 - Motors
- Flow (valves)
- Audio
 - Speakers
 - Headphones
- Printer
 - Punched tape
 - Braille embosser
 - Plotter
- Temperature
 - Heating
 - Cooling



Output Devices

- Graphics
 - Screen (Monitor)
 - Automotive navigation system
 - LCD, LED
- Data through wired/wireless communication


LED

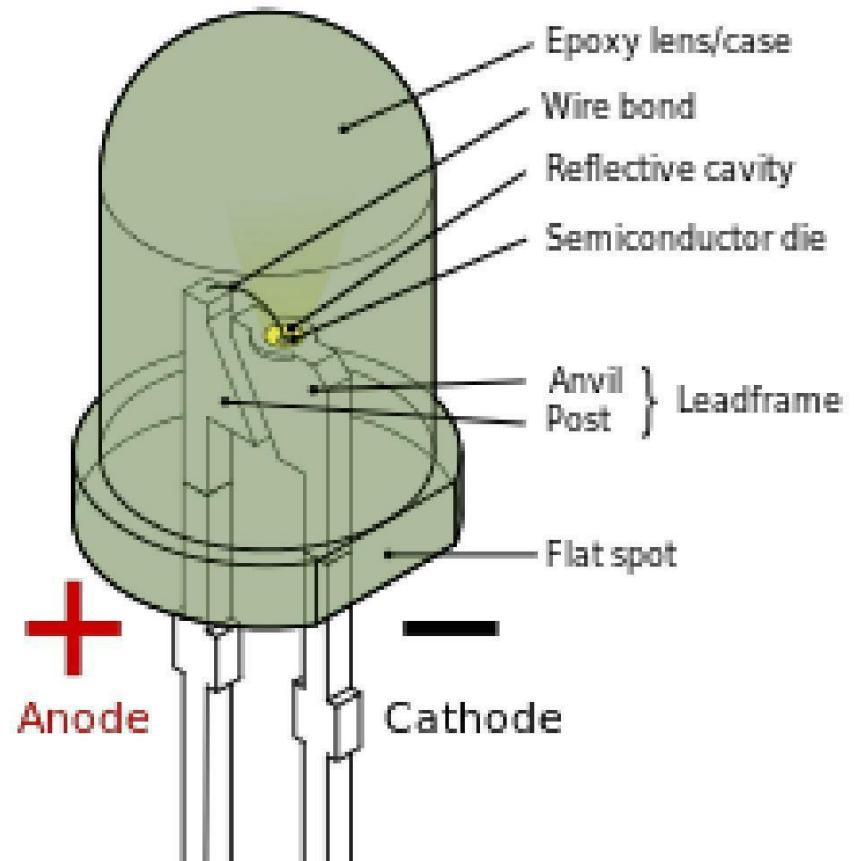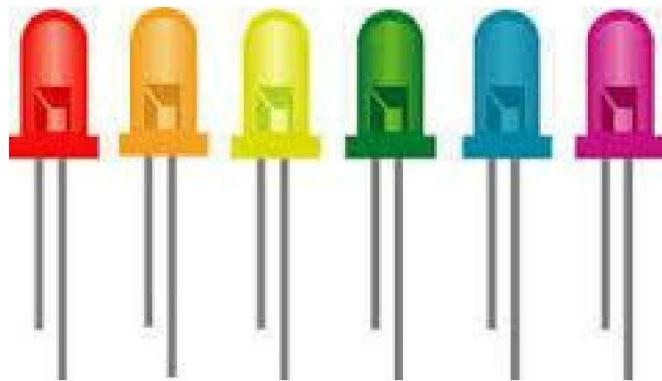






LED

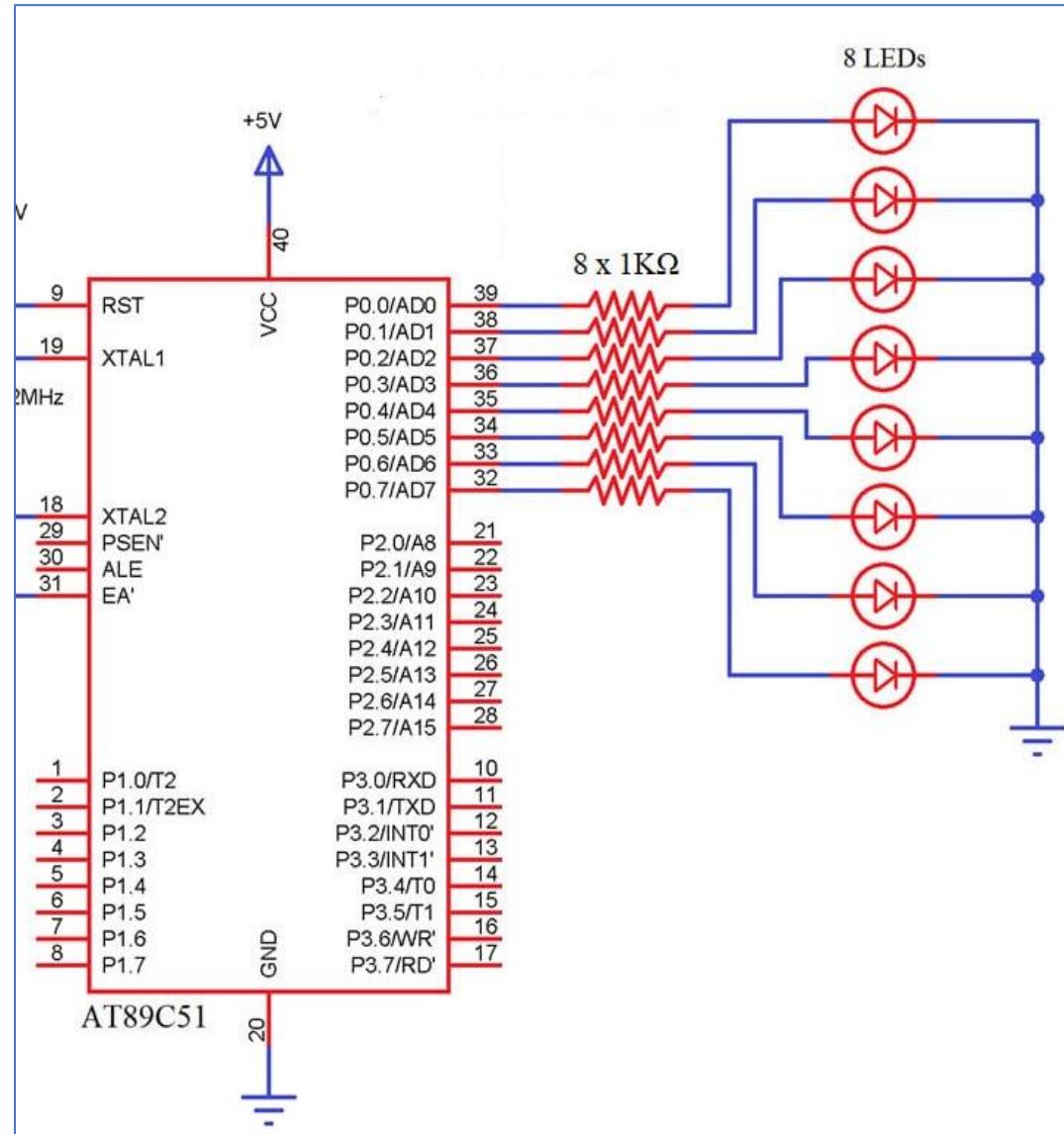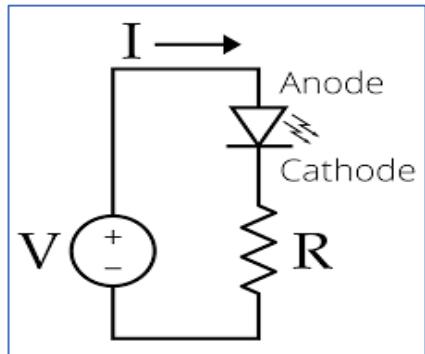


LED Multiplexing

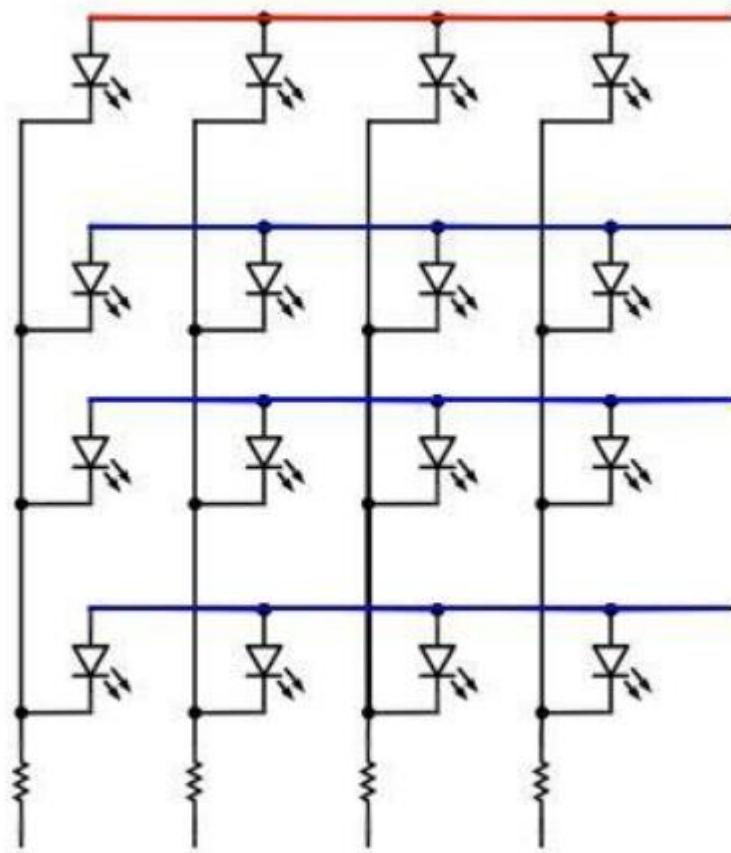

LED Multiplexing

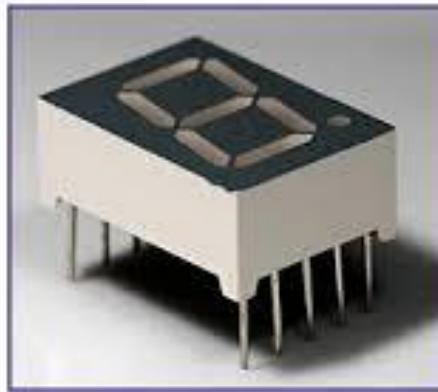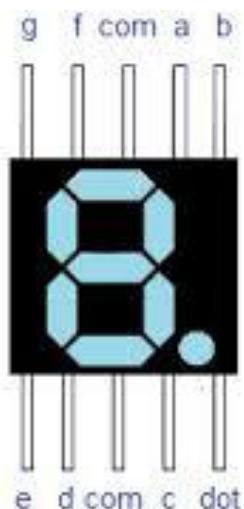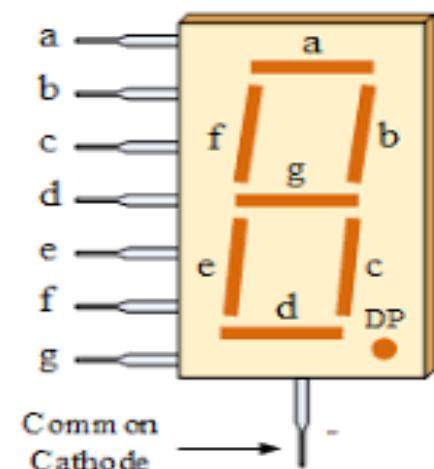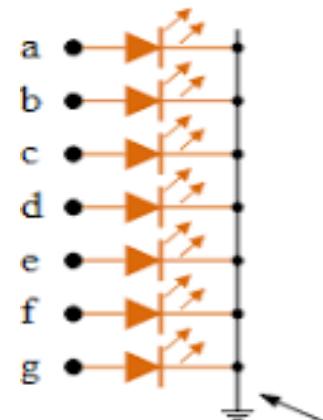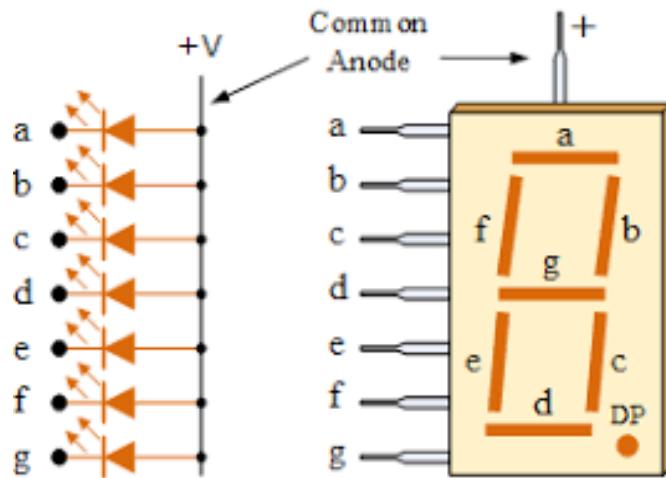

LED Multiplexing

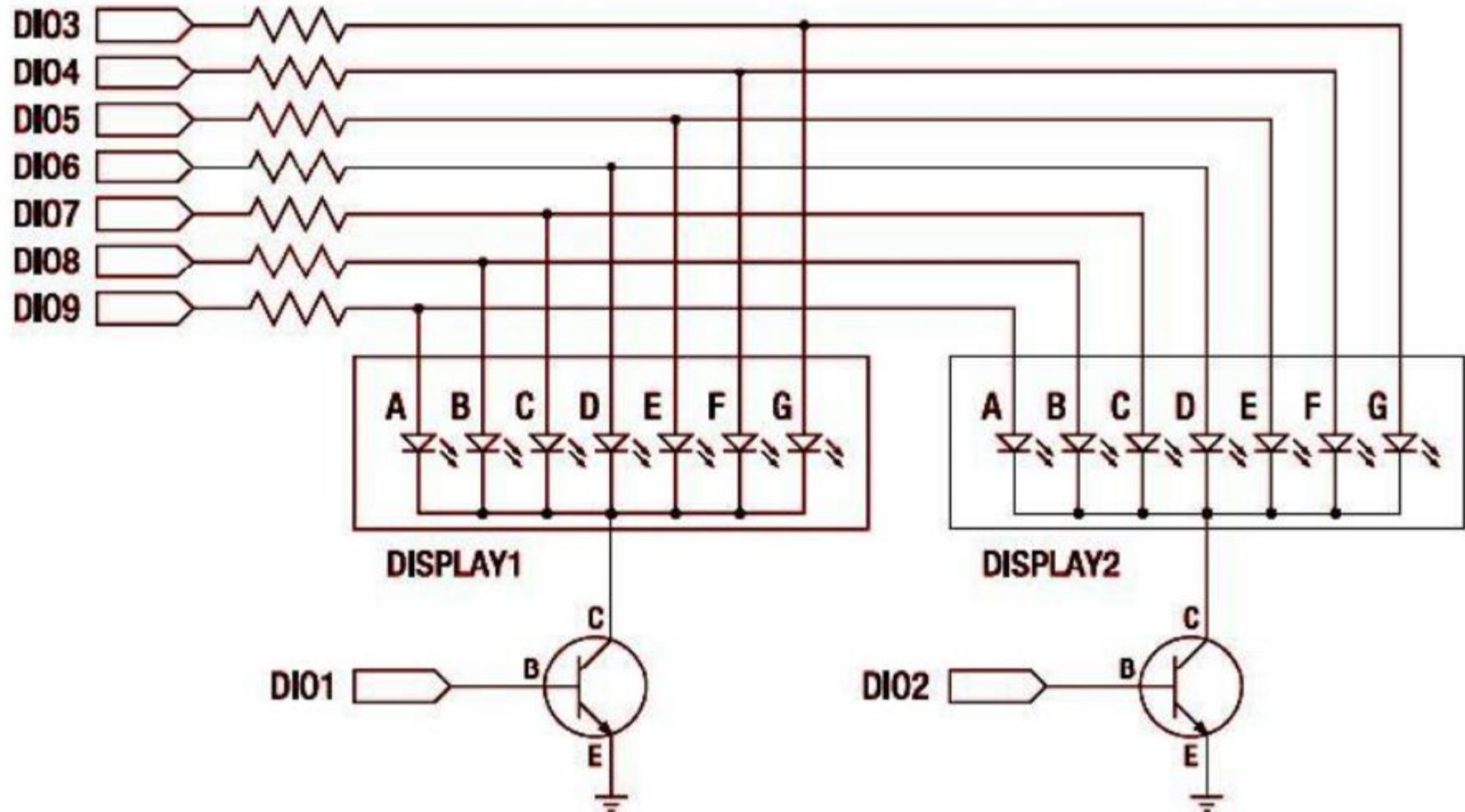


LED Multiplexing Demo



LCD

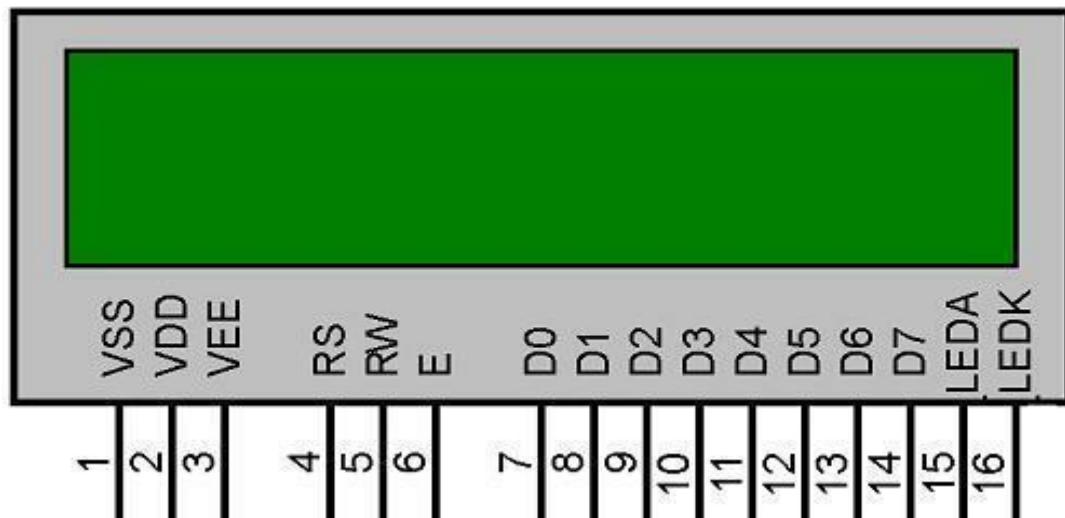
- Operating Voltage is 4.7V to 5.3V
- Current consumption is 1mA without backlight
- Alphanumeric LCD can display alphabets and numbers
- Consists of two rows and each row can print 16 characters.
- Each character is build by a 5x8 pixel box
- Can work on both 8-bit and 4-bit mode




LCD

Pin No:	Pin Name:	Description
1	Vss (Ground)	Ground pin connected to system ground
2	Vdd (+5 Volt)	Powers the LCD with +5V (4.7V – 5.3V)
3	VE (Contrast V)	Decides the contrast level of display. Grounded to get maximum contrast.
4	Register Select	Connected to Microcontroller to shift between command/data register
5	Read/Write	Used to read or write data. Normally grounded to write data to LCD
6	Enable	Connected to Microcontroller Pin and toggled between 1 and 0 for data acknowledgement
7 -14	Data Pin 0 - 7	Data pins 0 to 7 forms a 8-bit data line. They can be connected to Microcontroller to send 8-bit data. These LCD's can also operate on 4-bit mode in such case Data pin 4,5,6 and 7 will be left free.
15	LED Positive	Backlight LED pin positive terminal
16	LED Negative	Backlight LED pin negative terminal

LCD Interfacing

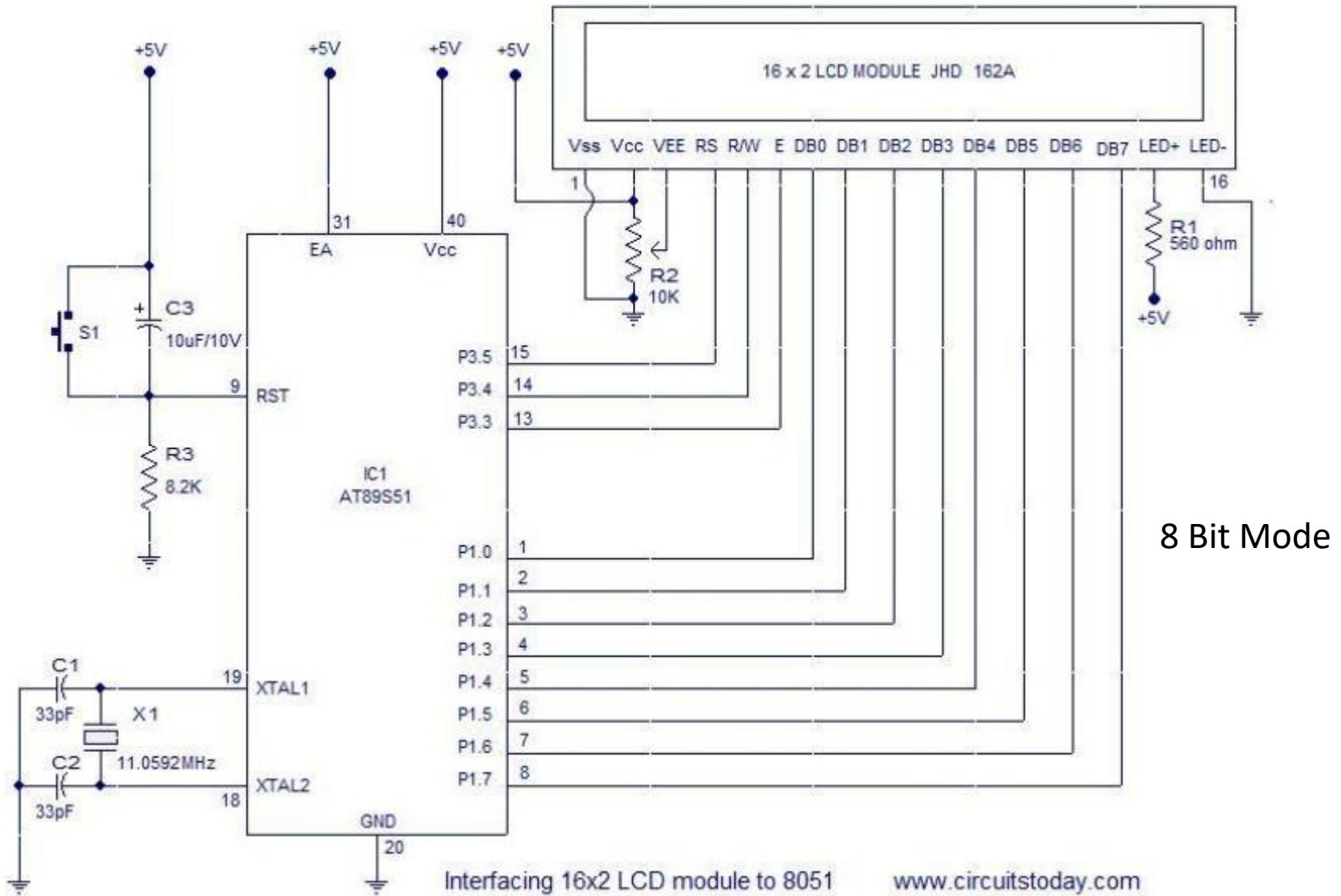


LCD Interfacing

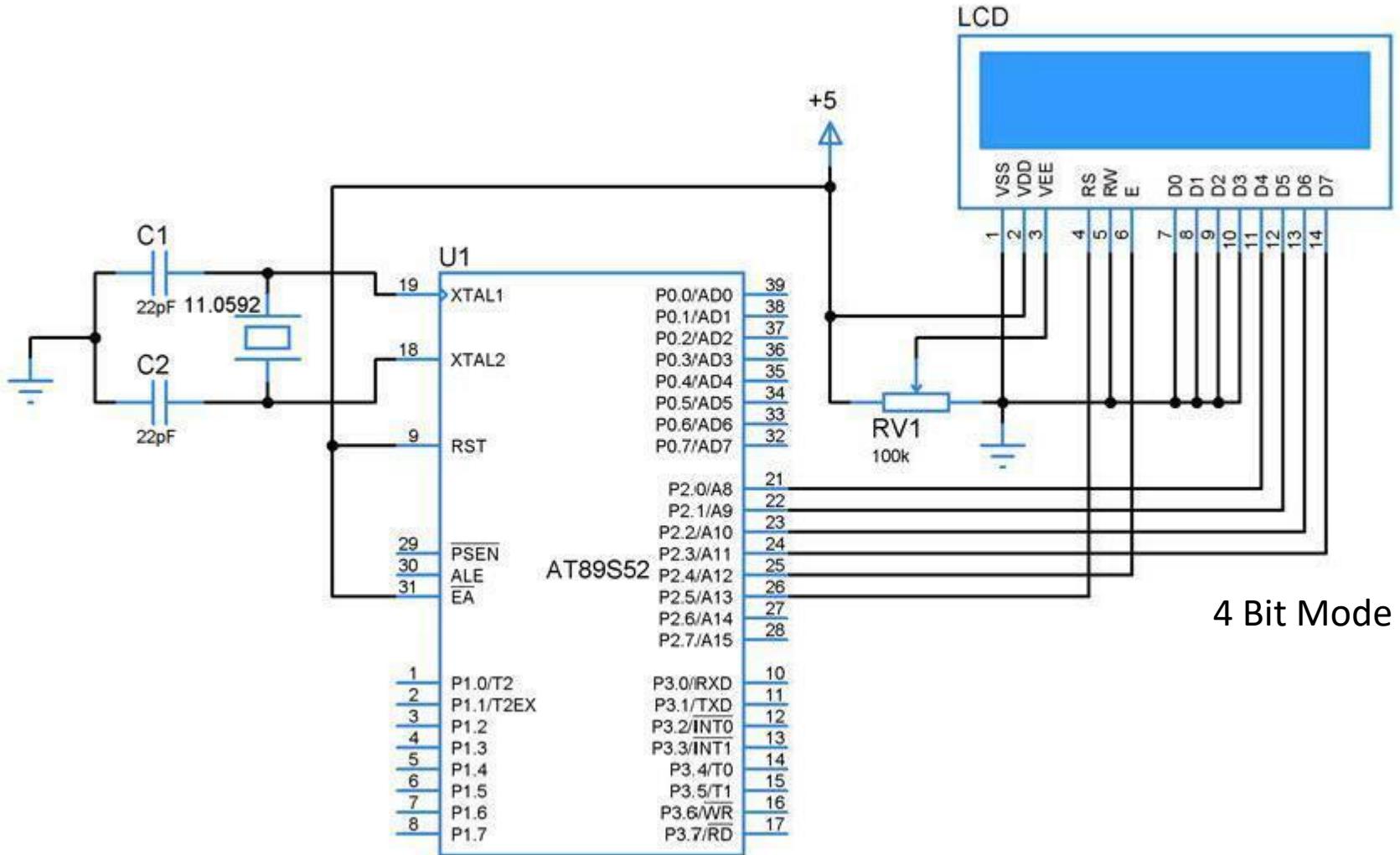

Buzzer



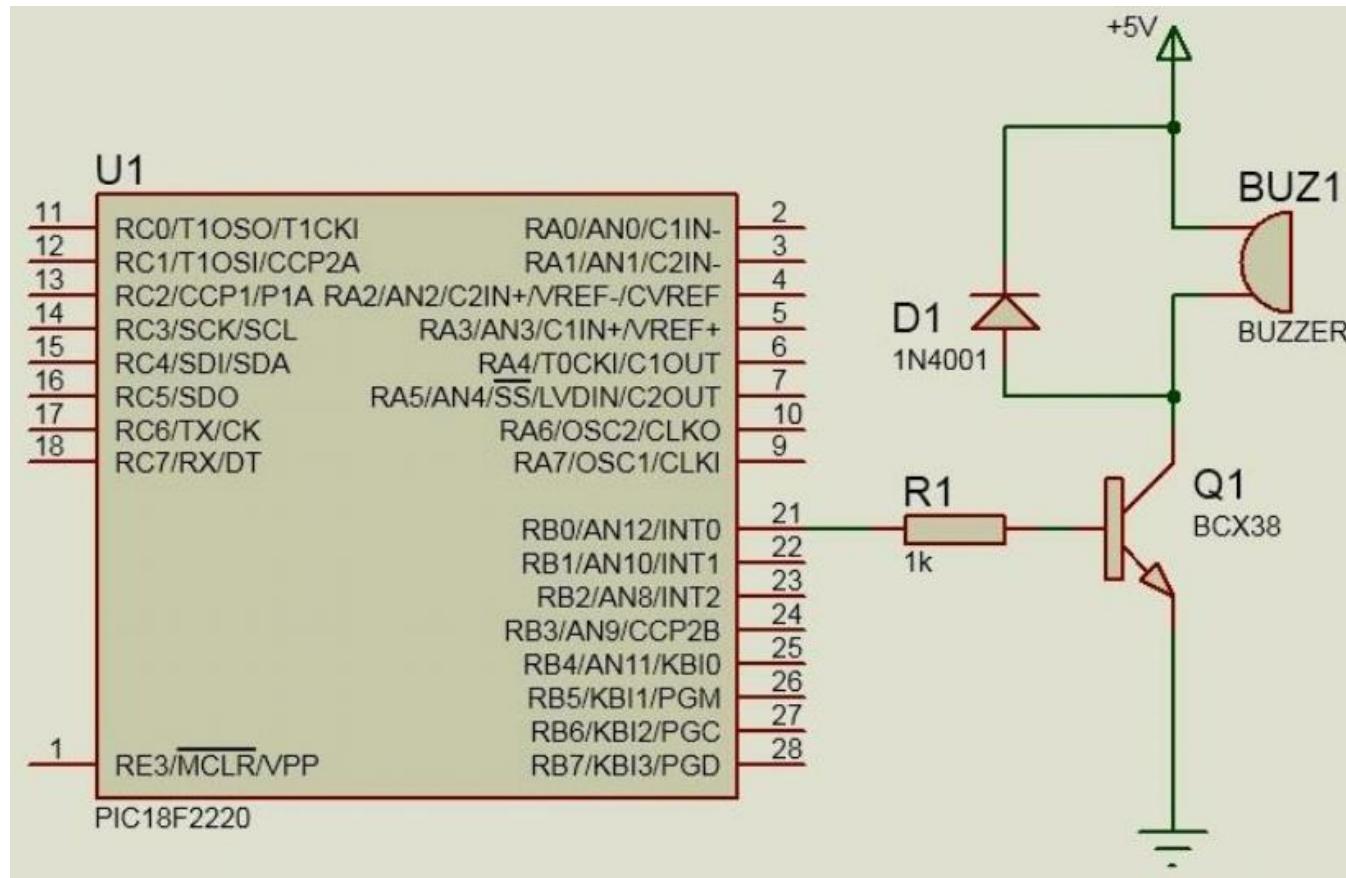
A **buzzer** or **beeper** is an audio signaling device




Motor

There are basically three types of conventional electrical motor available:

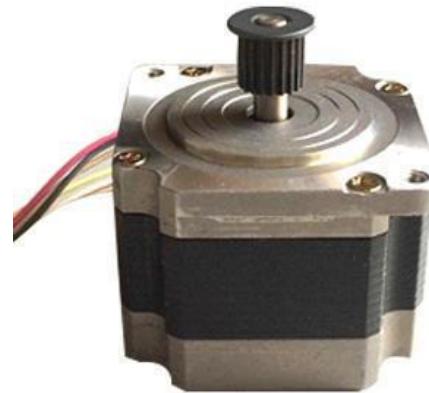
- A Typical Small DC Motor.
- Servo Motor.
- Stepper Motor.




Motor Interfacing

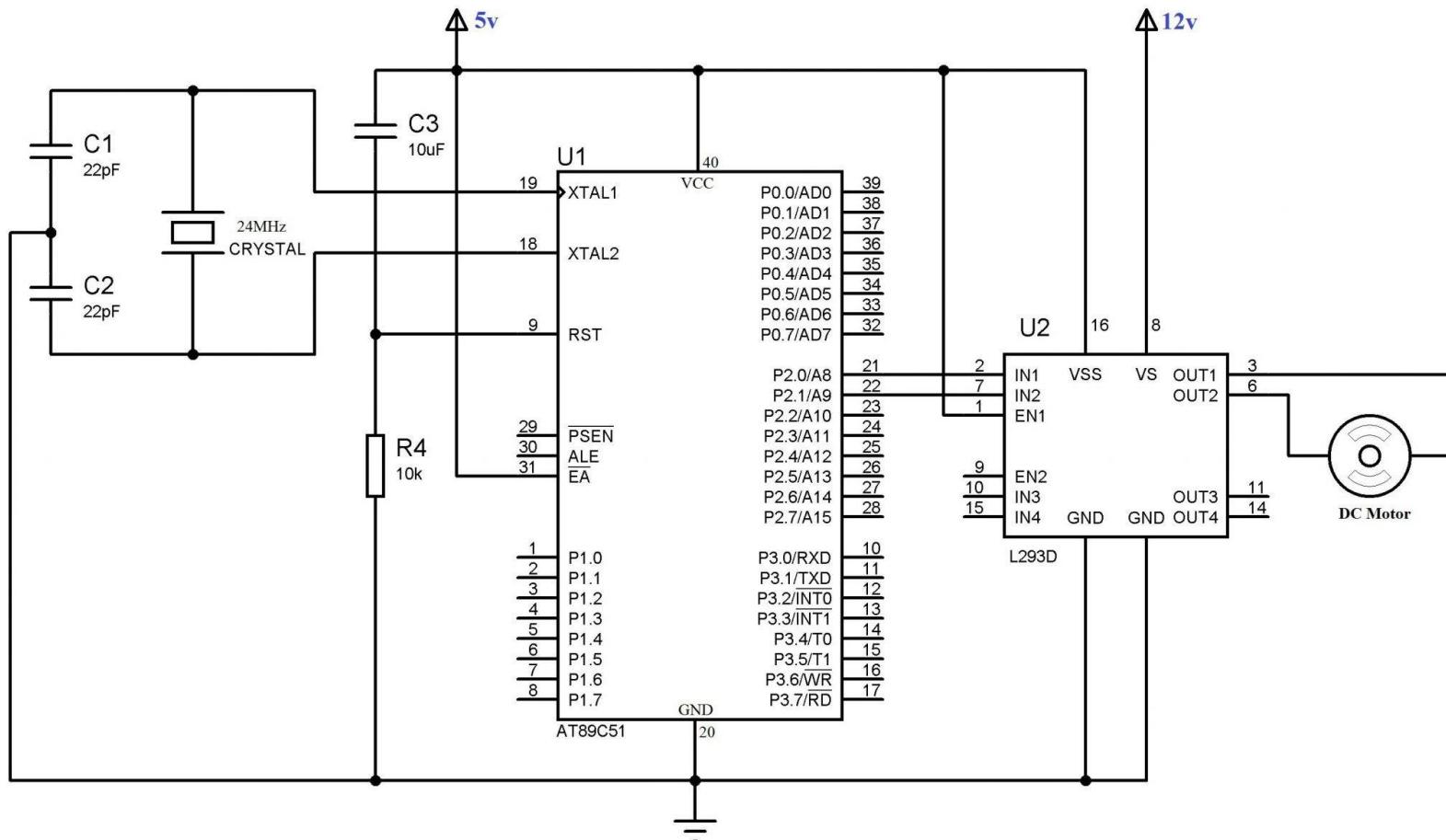


Motor Demonstration

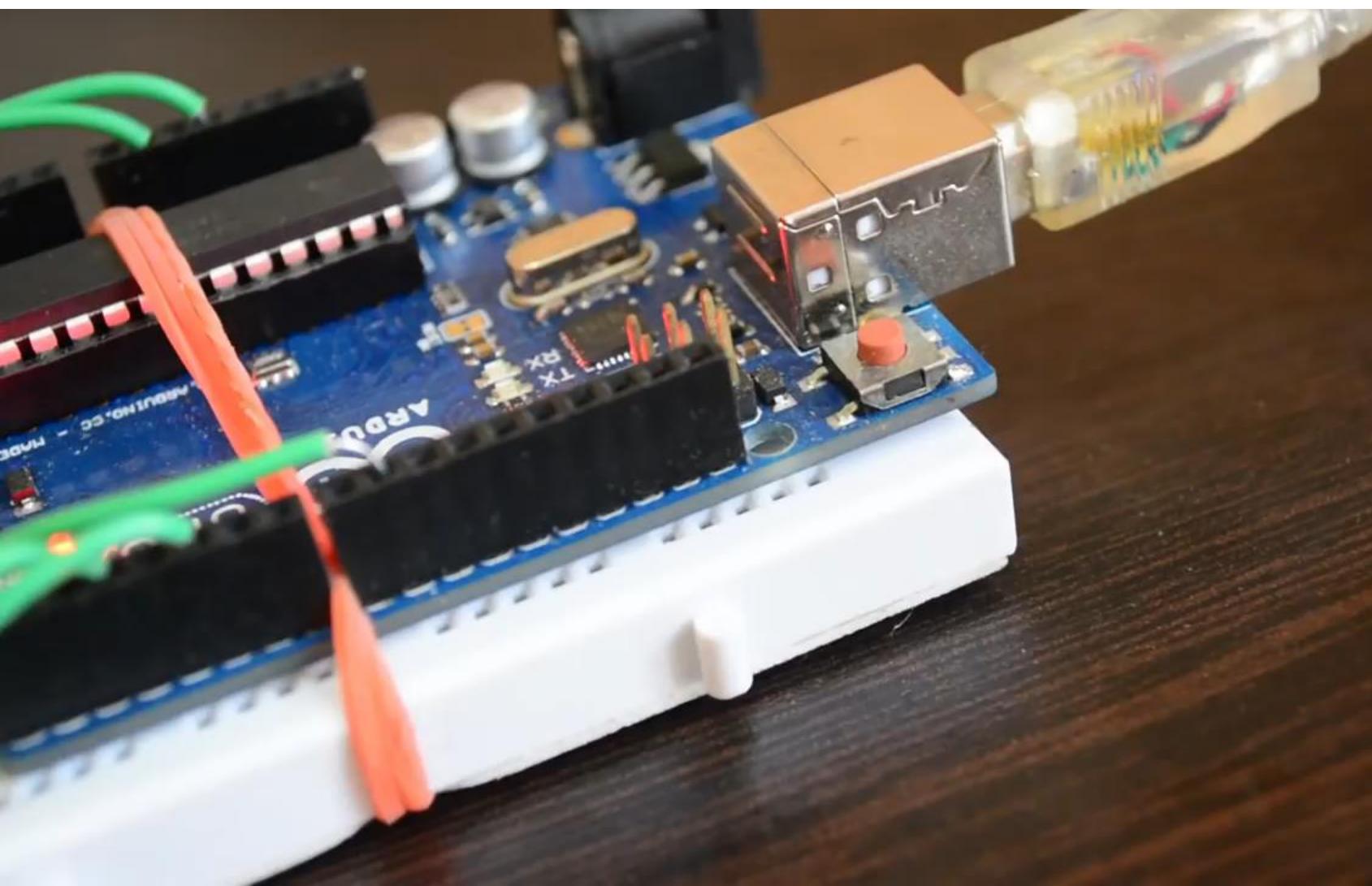

Data Communication Devices

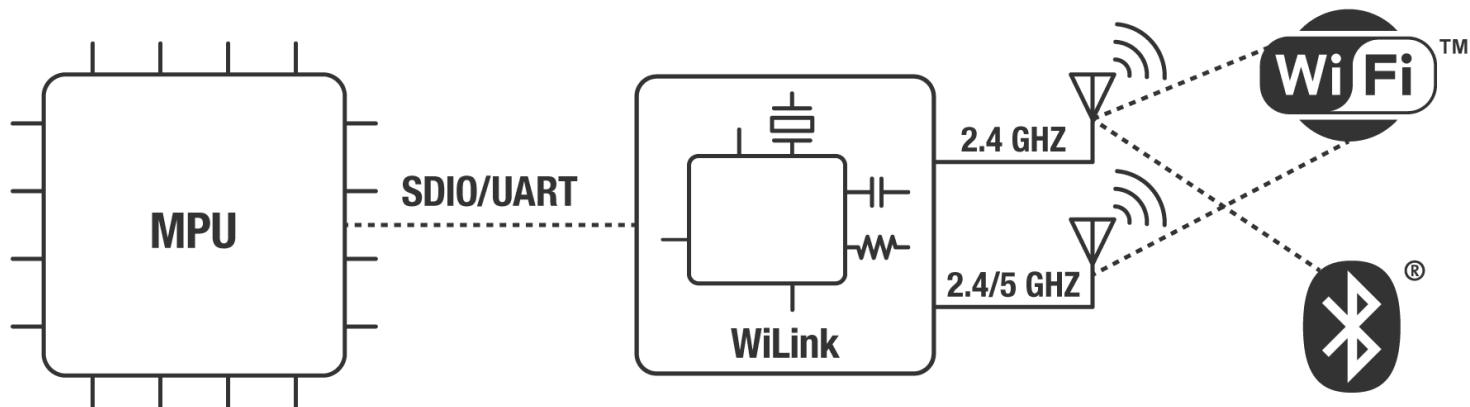


Data Communication Devices

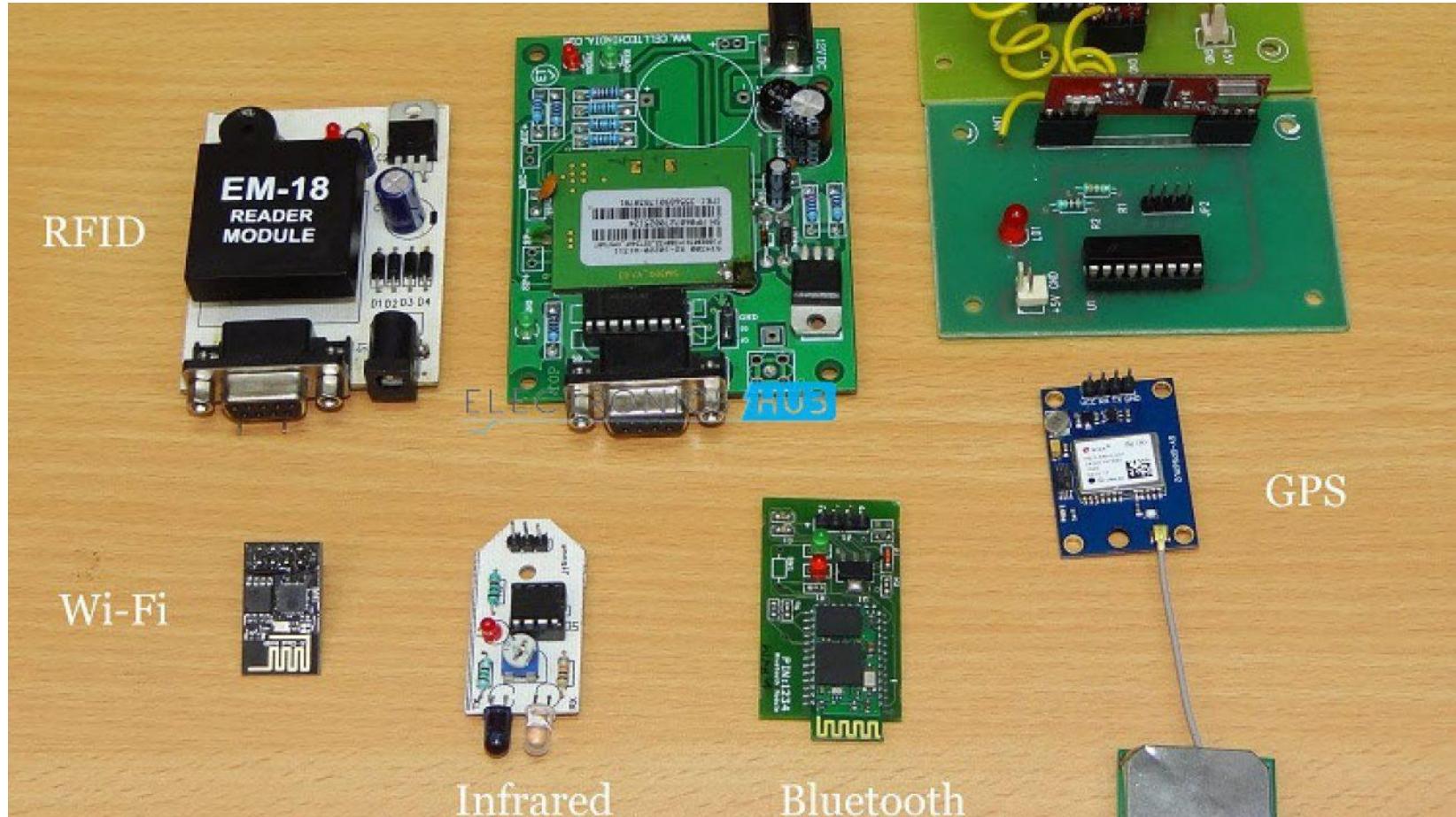


WIRELESS TECHNOLOGIES AT A GLANCE					
Technology	Frequency	Data rate	Range	Power	Cost
2G/3G	Cellular bands	10 Mb/s	Several km	High	High
802.15.4	2.4 GHz	250 kb/s	100 m	Low	Low
Bluetooth	2.4 GHz	1, 2.1, 3 Mb/s	100 m	Low	Low
LoRa	< 1 GHz	<50 kb/s	2-5 km	Low	Medium
LTE Cat 0/1	Cellular bands	1-10 Mb/s	Several km	Medium	High
NB-IoT	Cellular bands	0.1-1 Mb/s	Several km	Medium	High
SIGFOX	<1 GHz	Very low	Several km	Low	Medium
Weightless	<1 GHz	0.1-24 Mb/s	Several km	Low	Low
Wi-Fi (11f/h)	2.4, 5, <1 GHz	0.1-1 Mb/s	Several km	Medium	Low
WirelessHART	2.4 GHz	250 kb/s	100 m	Medium	Medium
ZigBee	2.4 GHz	250 kb/s	100 m	Low	Medium
Z-Wave	908.42 MHz	40 kb/s	30 m	Low	Medium

Data Interfaces

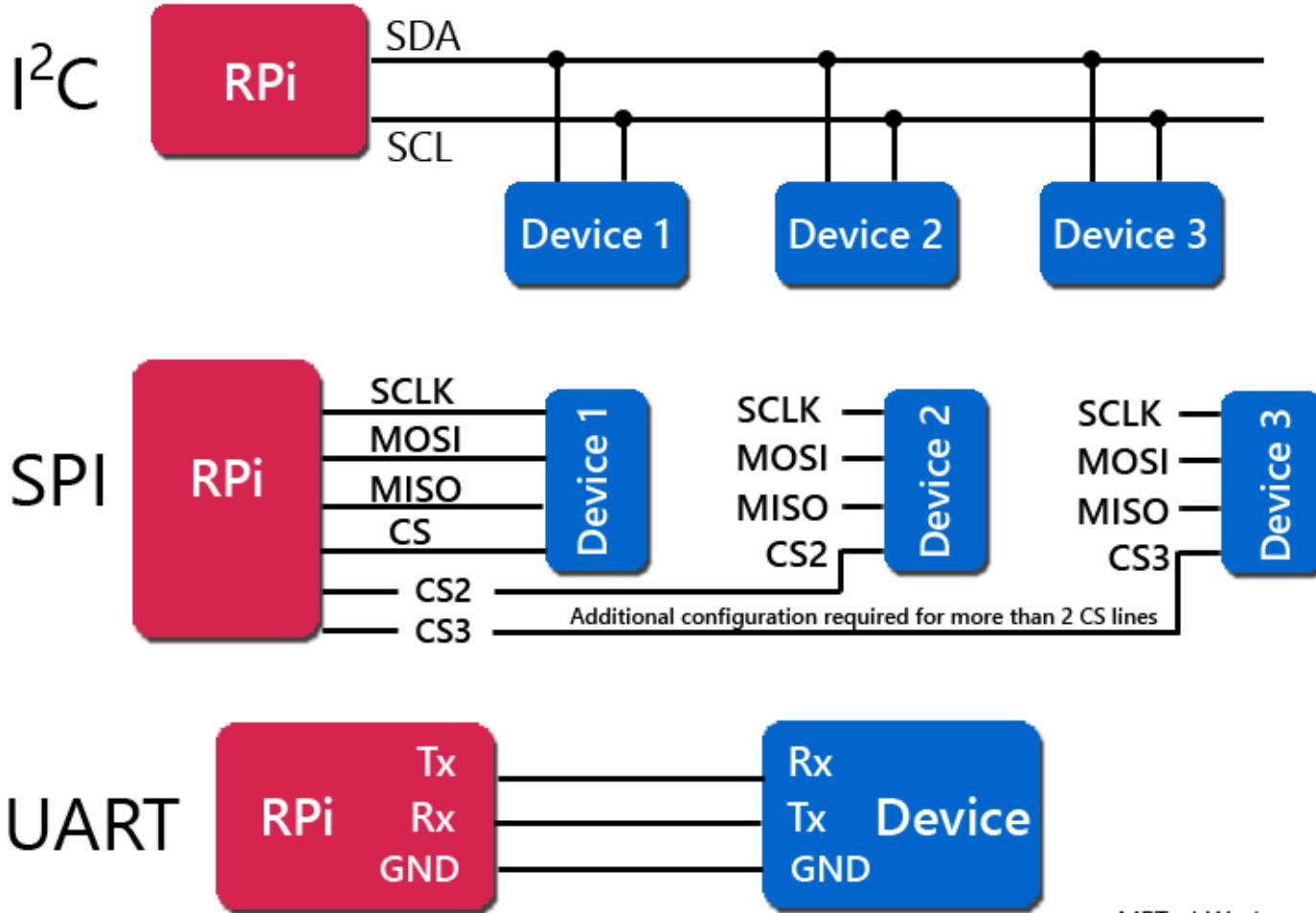

Wifi Module interfacing

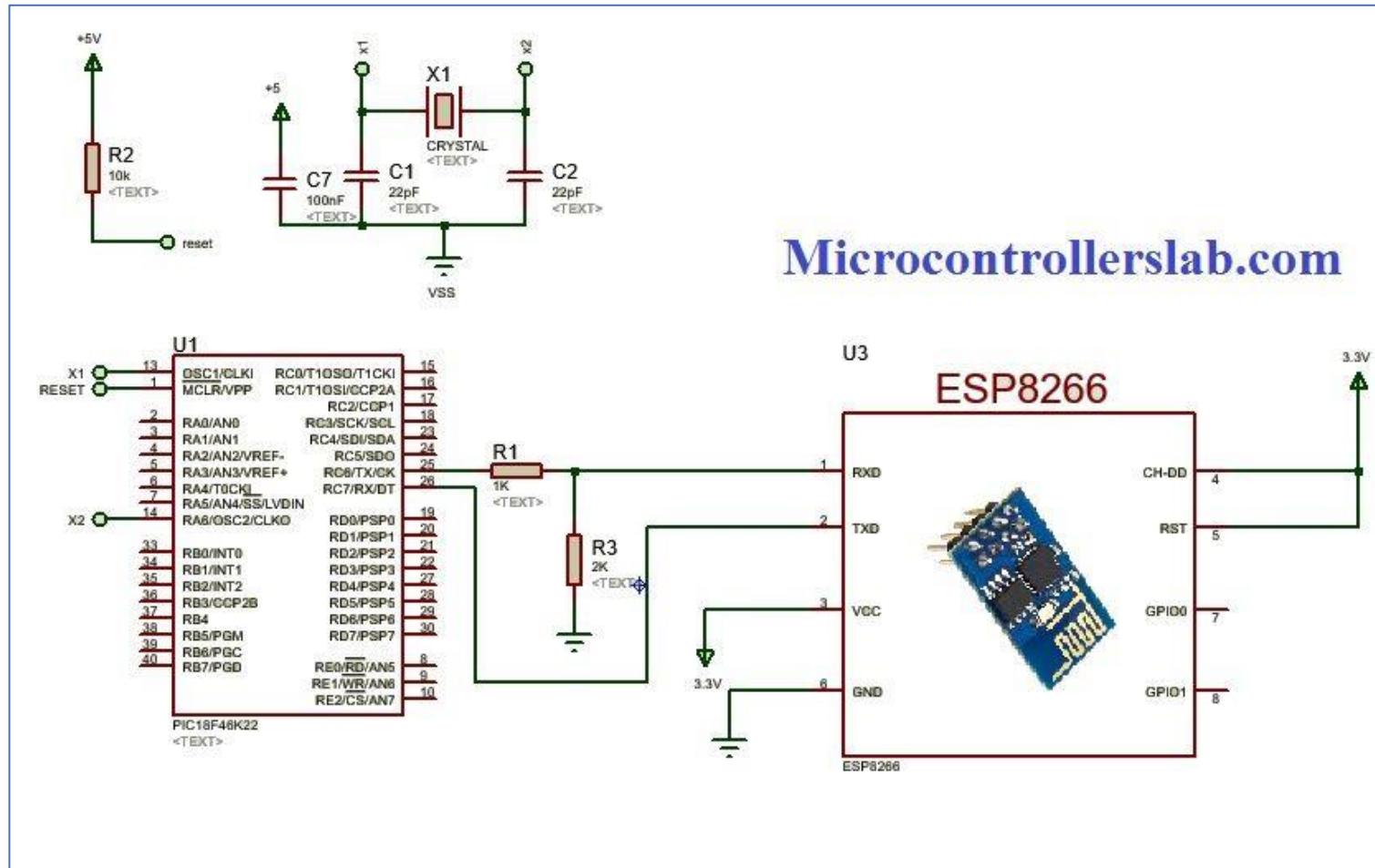

Embedded System Demo



Electronics | Software & Mechanical Kits

Embedded System Demo

System Components

Input Devices

Output Devices